

第7章 软开关谐振功率变换技术

- ◆什么是 软开关技术 (soft switching) ?
- ◆为什么要使用 soft switching ?
- ◆如何实现 soft switching ?

课程教材：徐德鸿、马皓、汪樾生主编 电力电子技术

软开关的概念 Concept of soft switching






(1) 理想开关 (Ideal switch)

◆ Static characteristics

- ON state $R=0$
- Off state $R=\text{infinite}$



◆ Dynamic characteristics

- Turn on time=0
- Turn off time=0

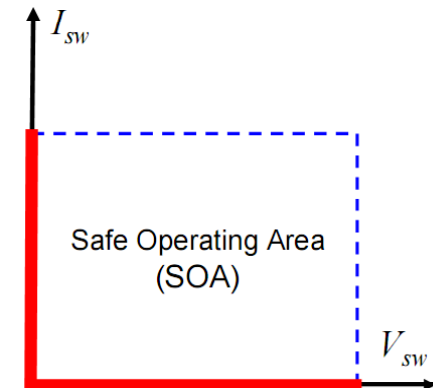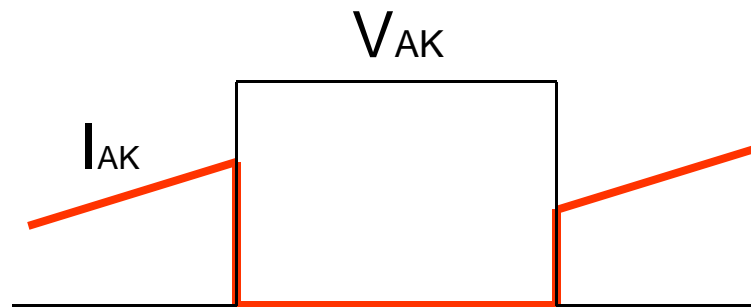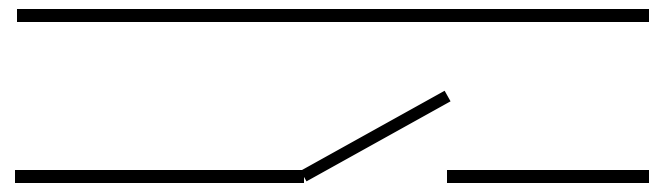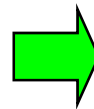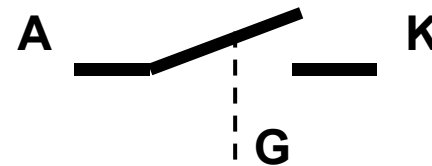

(2) 实际的功率器件的开关过程


◆ 特性：拖拉、动作不干脆

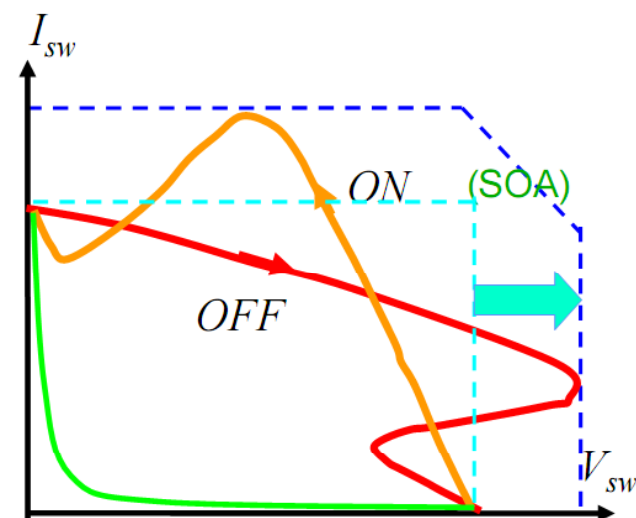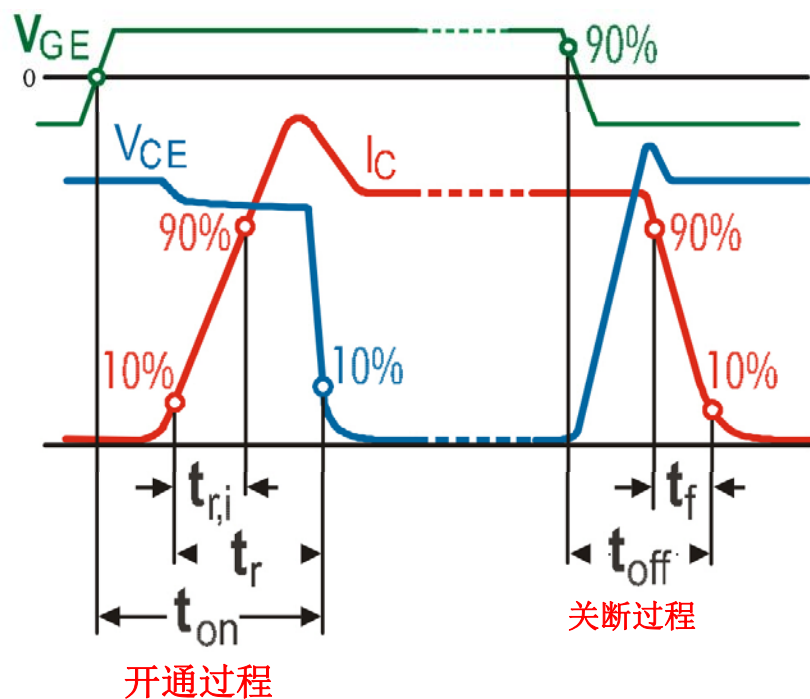


此外,存在通态压降

比较

Ideal Switching

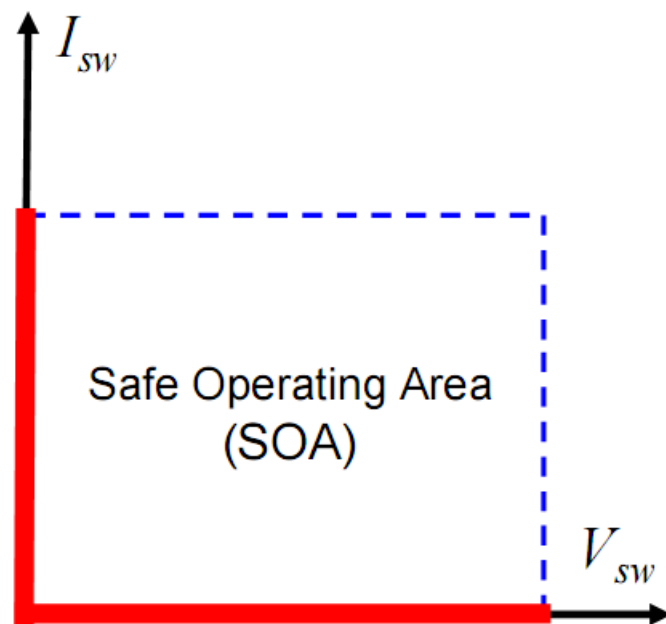


Actual Switching

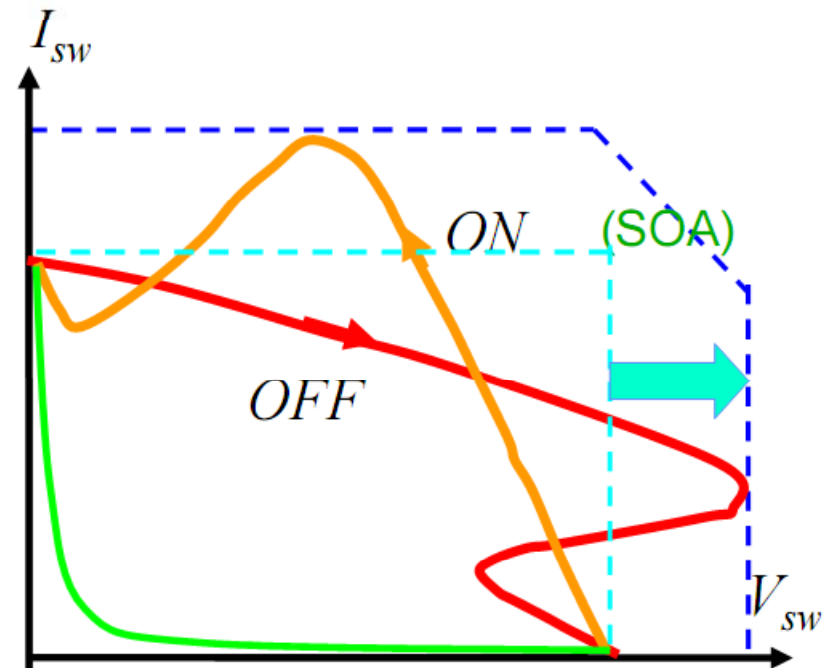


IGBT开关过程

器件: U-Series IGBT+Si FWD (2MBI150U4B)
IGBT: 150A/1200V Si diode: 150A/1200V


@Vce=600V Ic=40A Rg=2.2Ω

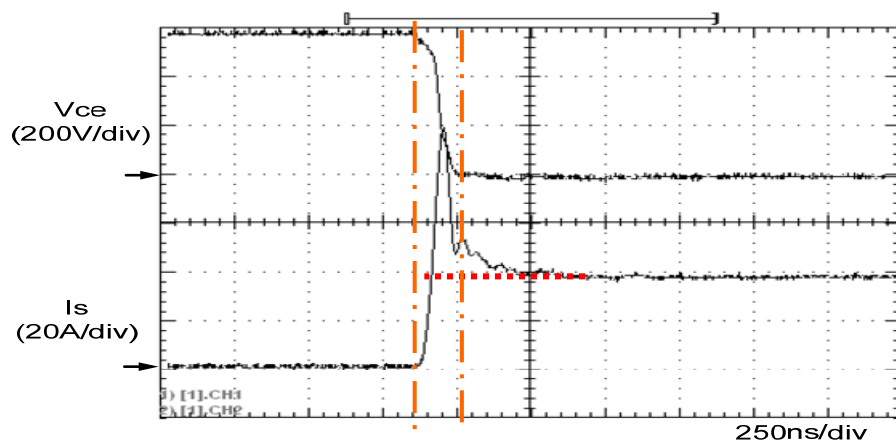


Switch-on

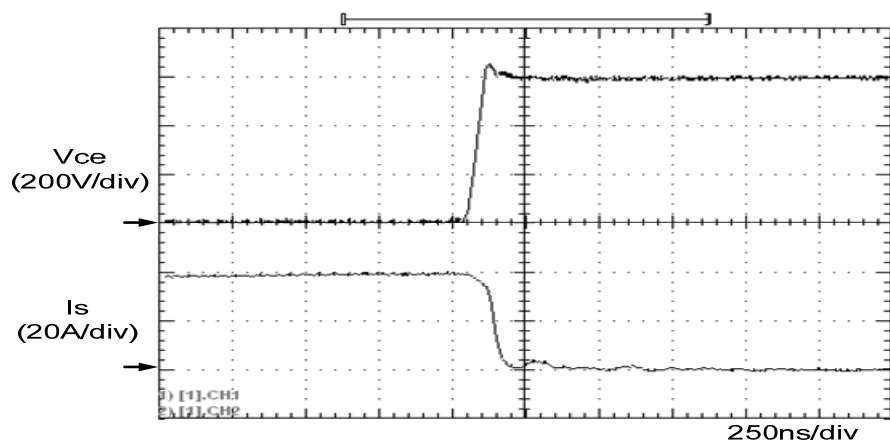

2018/9/3 Switch-off

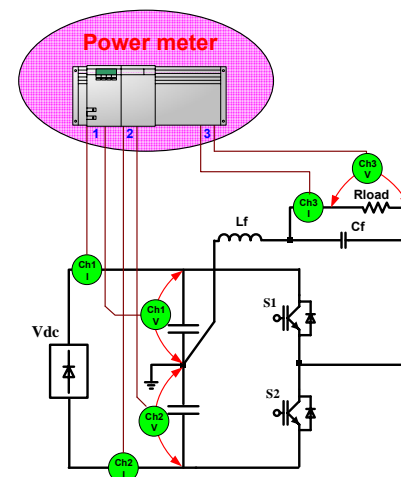

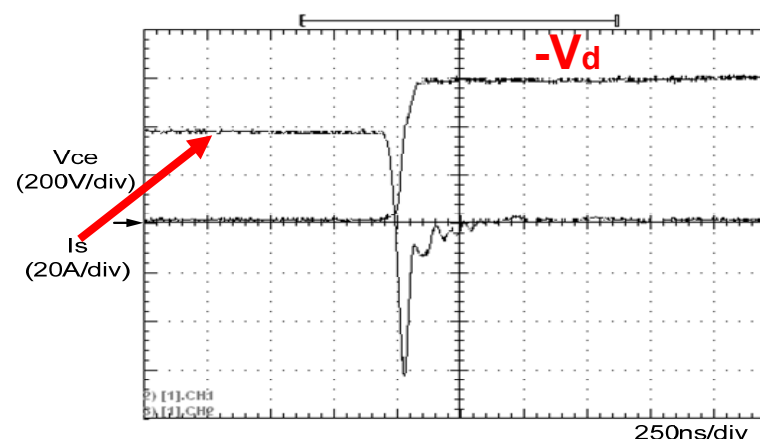
$$P_{sw} = f \cdot \sum_{n=1}^N [E_{off}(i_o(n)) + E_{on}(i_o(n)) + E_{rr}(i_o(n))]$$



电力电子技术


Reverse recovery

二极管反向恢复过程 (Diode reverse recovery)


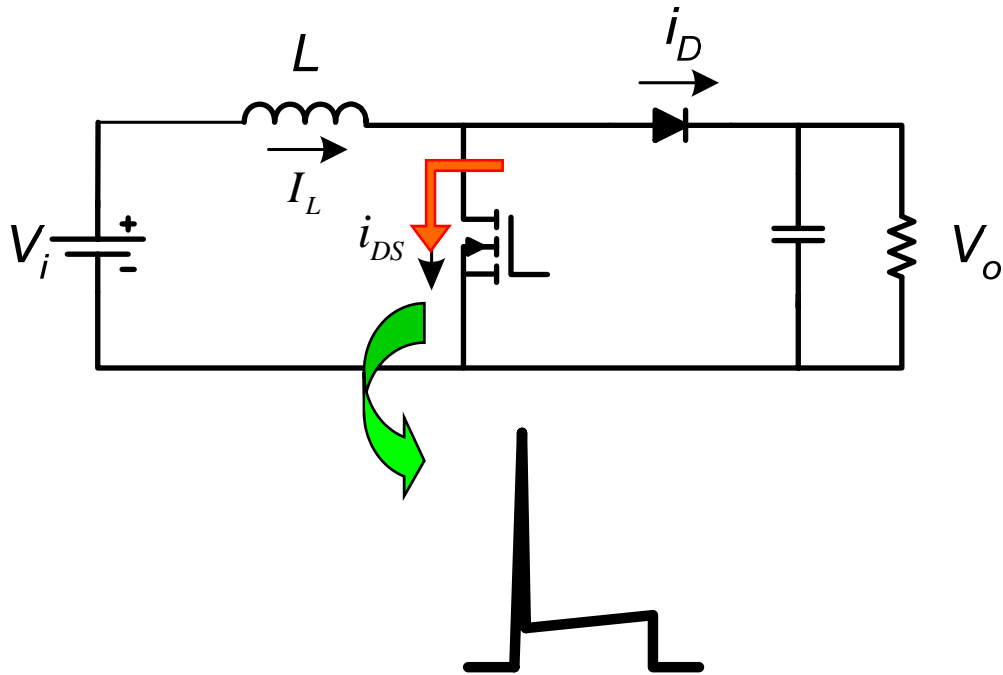


- High di/dt , EMI problem
- High loss on switch and diode

In the future SiC Schottky diode

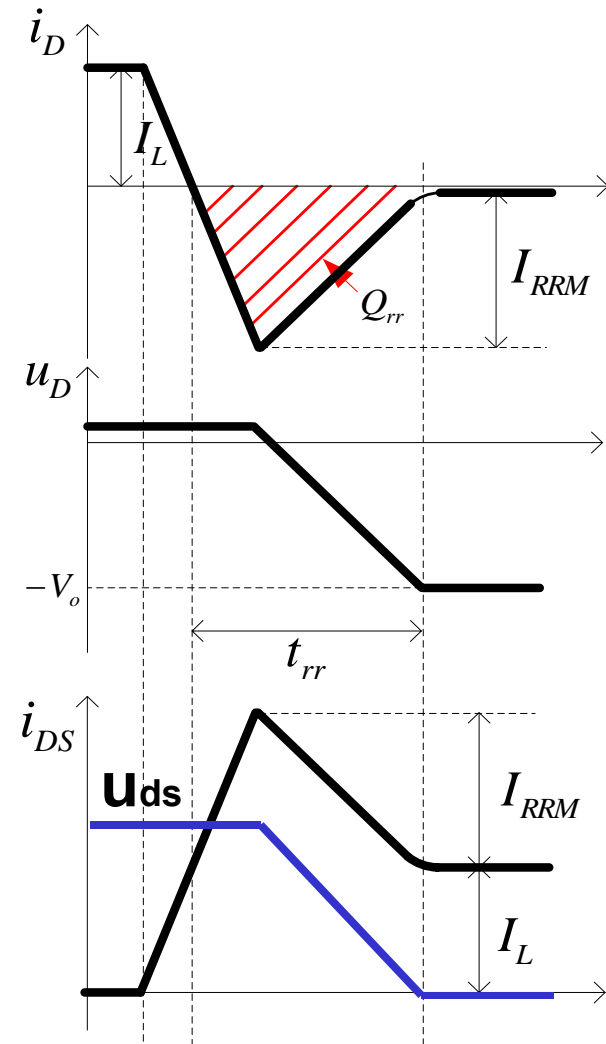

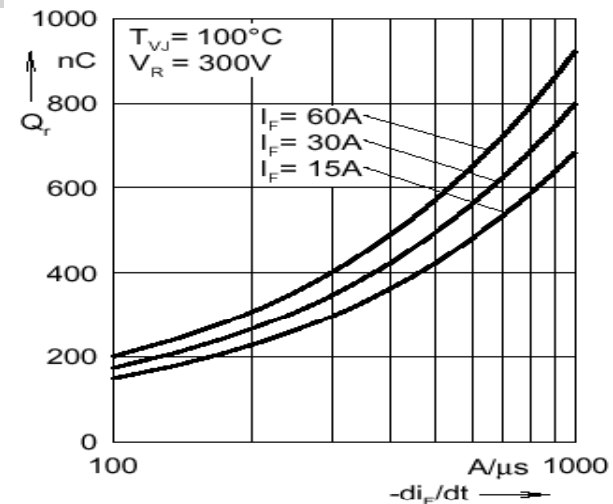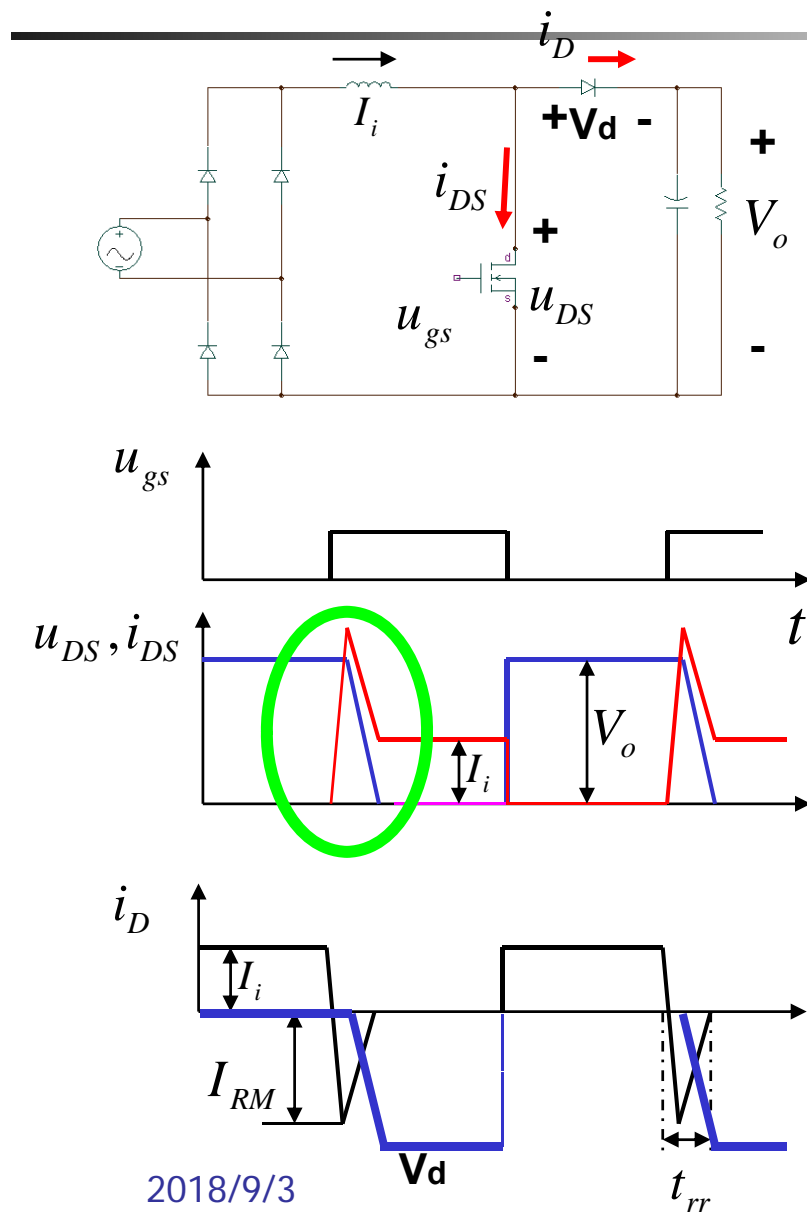反向恢复过程引起的损耗 (Switching loss resulting from reverse recovery)



Reverse recovery charge Q_{rr} vs. $\frac{dI_F}{dt}$

➤ Turn-on loss in switch and boost diode

$$A_{\text{turn_on}} = Q_{rr} V_o + I_i \int_0^{t_{rr}} u_{DS} dt + \frac{1}{2} C_{oss} V_o^2$$

寄生电容 (Parasitic capacitance)

Power MOSFET

Diode

Layout stray capacitance

Transformer winding capacitance


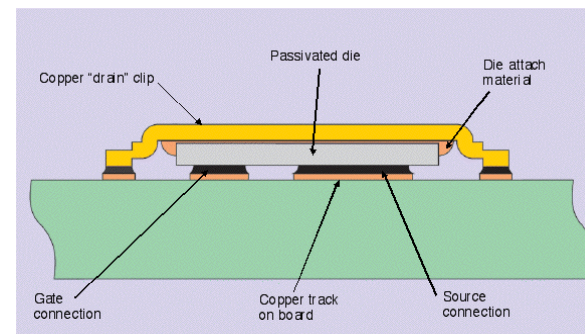
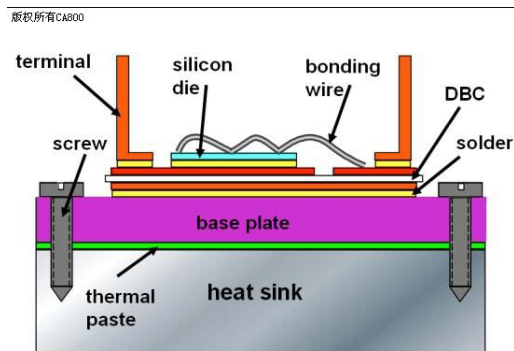
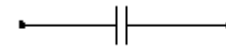
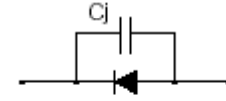
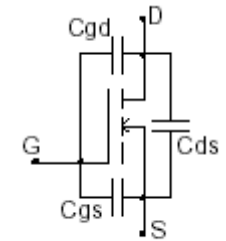



Fig 1 Cross-Section of a DirectFET MOSFET Soldered to PCB

寄生电感 (Parasitic inductance)

Leakage inductance of the transformer

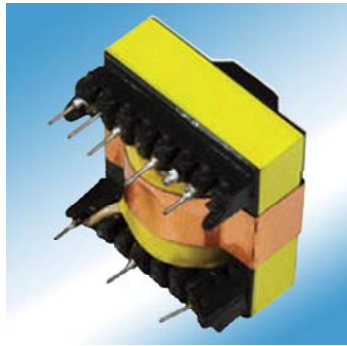


Equivalent circuit for a transformer


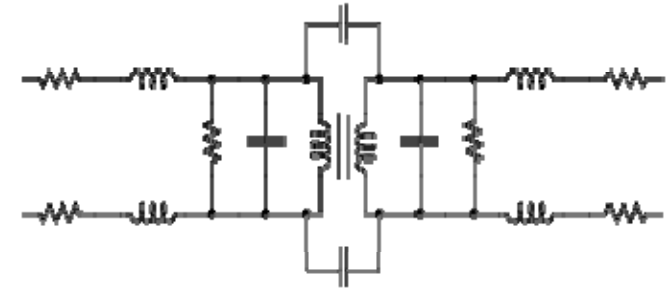


Stray inductance

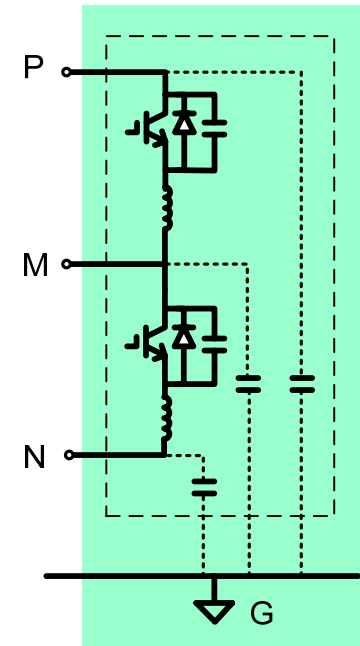
- Layout
- Wire bonds in device packages
- Leads of devices




理想元件构成的Buck变换器 (Ideal Buck converter)

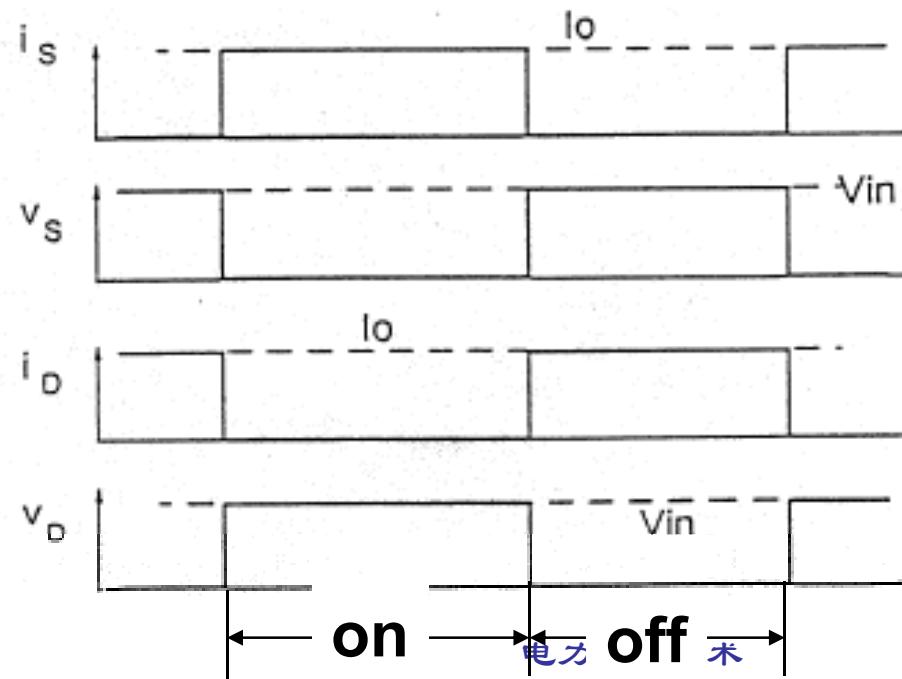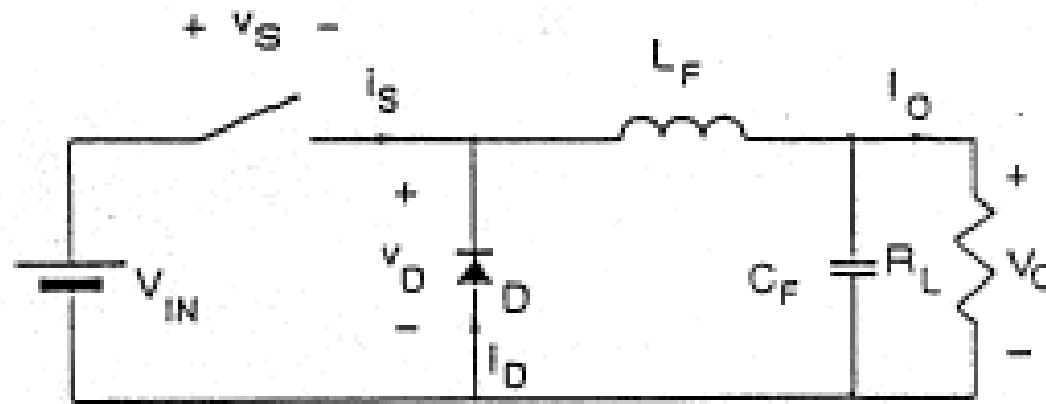

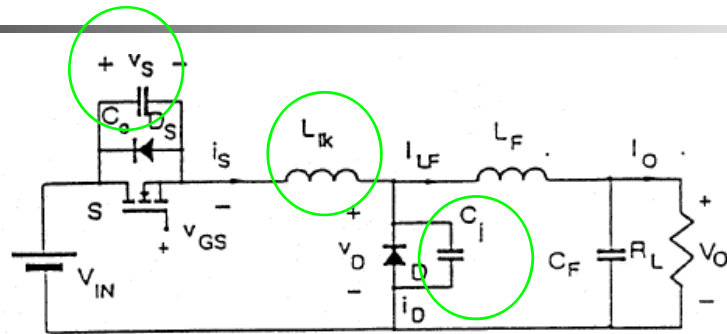实际元件构成的Buck变换器 (Practical Buck converter)




Ideal

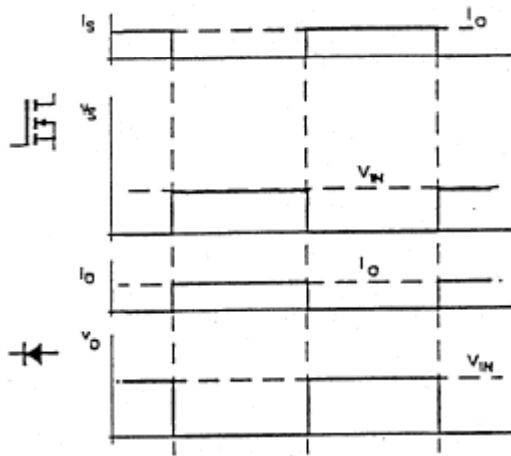

Square Waveforms

No Switching Loss

Practice

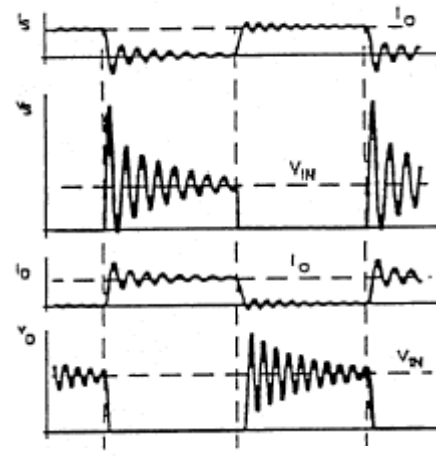

Parasitic Oscillations

Switching Loss



Snubber Loss

Gate-Drive Miller Effect

Low Efficiency at HF



反激变换器 (Flyback converter)

without parasitic

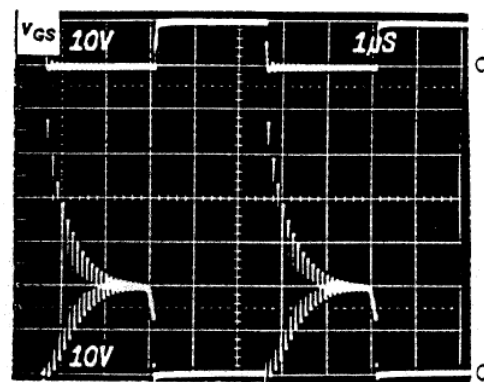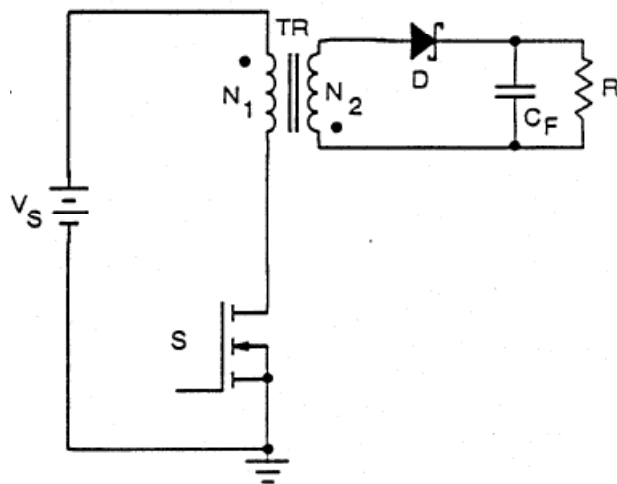


Gate-to-source (v_{GS}) and drain-to-source (v_{DS}) voltage waveforms of a PWM flyback converter without snubbers.
scales: 10 V/div ; 1 μ/div

with parasitic

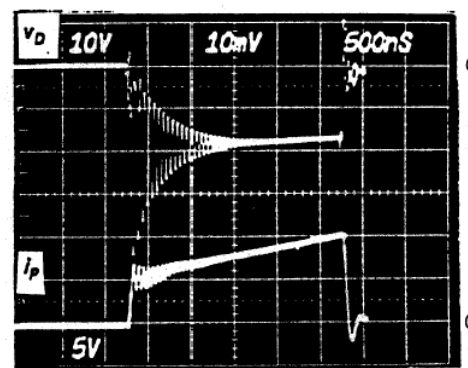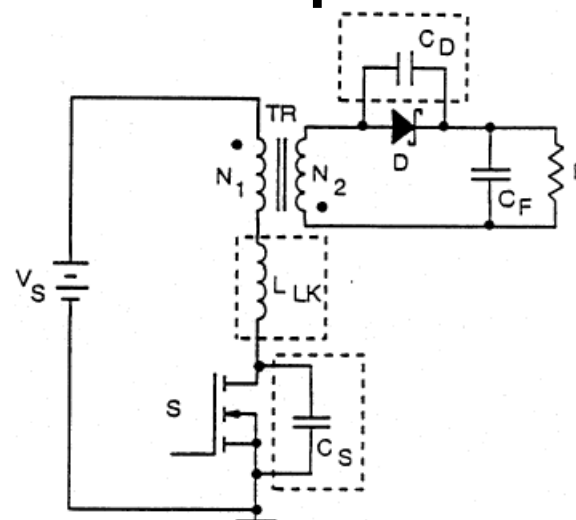


Rectifier voltage (v_D) waveform and primary current (I_P) waveform of a PWM flyback converter without snubbers.
scales: 10 V/div ; 1 A/div ; 500 ns/div.

吸收电路

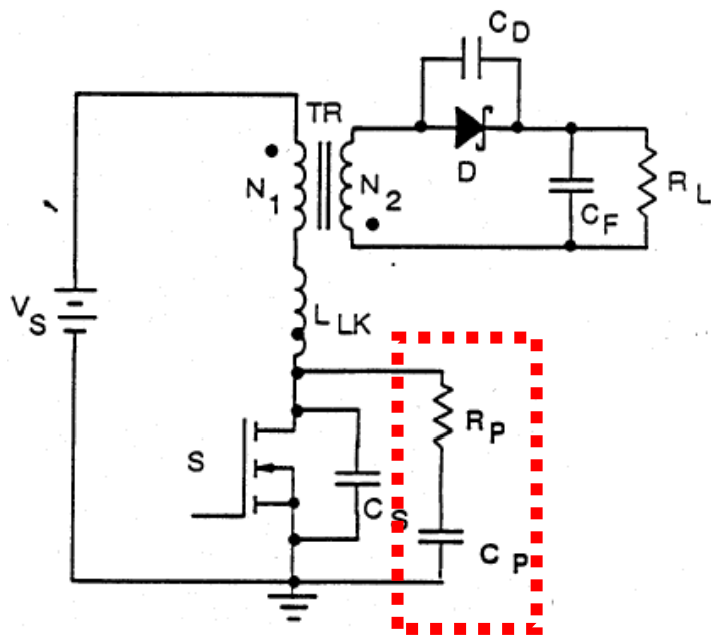


Primary switch RC snubber

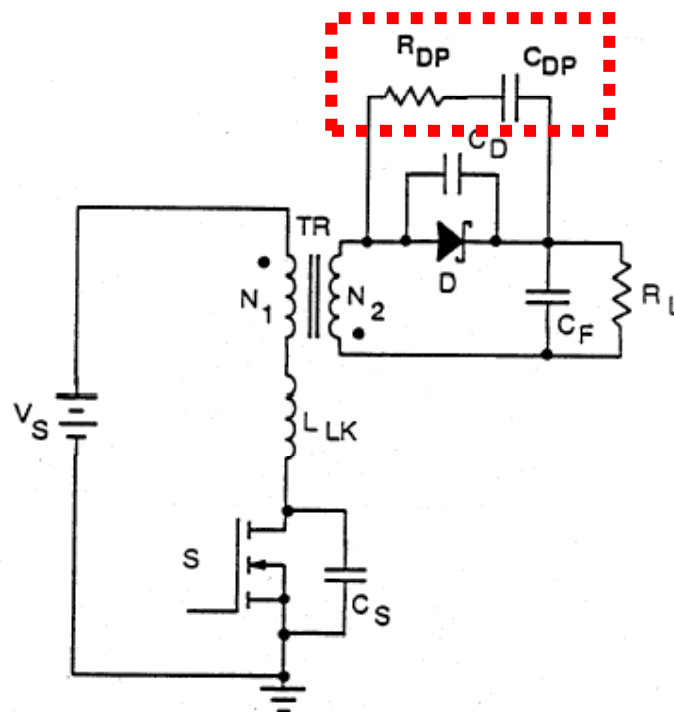

Rectifier snubber

振荡被抑制,但造成能量的损耗

开关过程和开关损耗（Hard switching operation）

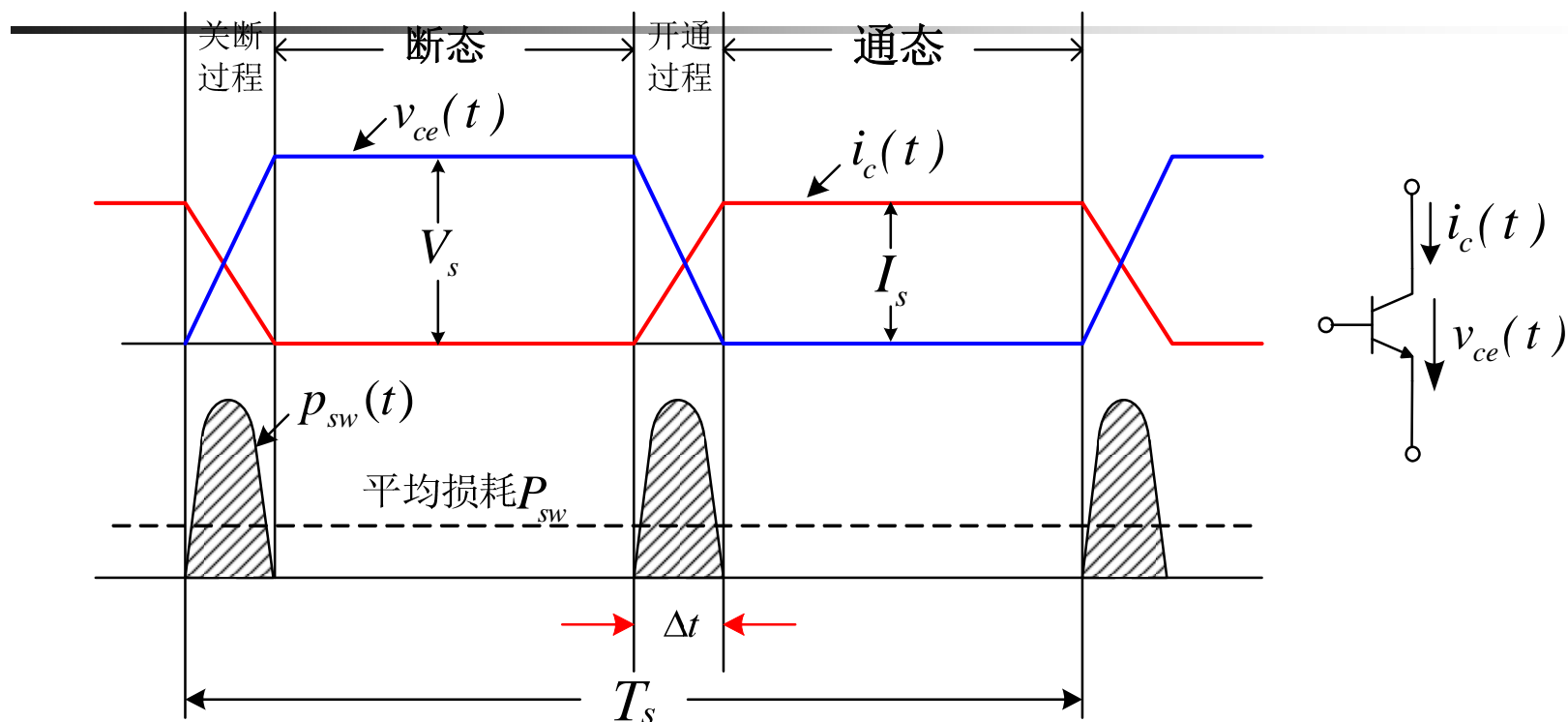

$$P_{sw} = \frac{1}{T_s} \int_0^{T_s} v_{ce}(t) \cdot i_c(t) dt = \frac{2}{T_s} \int_0^{\Delta t} v_{ce}(t) \cdot i_c(t) dt$$

$$= \frac{2}{T_s} \int_0^{\Delta t} \left(-\frac{V_s}{\Delta t} t + V_s \right) \frac{I_s}{\Delta t} t dt = \frac{1}{3} V_s I_s f_s \Delta t$$

开关频率 $f_s = \frac{1}{T_s}$

开关损耗 (Switching loss)

$$\begin{aligned} P_{sw} &= \frac{1}{T_s} \int_0^{T_s} v_{ce}(t) \cdot i_c(t) dt = \frac{2}{T_s} \int_0^{\Delta t} v_{ce}(t) \cdot i_c(t) dt \\ &= \frac{2}{T_s} \int_0^{\Delta t} \left(-\frac{V_s}{\Delta t} t + V_s \right) \frac{I_s}{\Delta t} t dt = \frac{1}{3} V_s I_s f_s \Delta t \end{aligned}$$

平均开关损耗功率与开关频率 f_s 和重叠时间 Δt 之积成正比



在高频应用场合为抑制开关损耗，需选用开关速度快的器件

减少重叠时间 (Reduce overlapping time)

◆ 电力电子电路的高频化

- 可以减小滤波器、变压器的体积和重量，电力电子装置小型化、轻量化。
- 开关损耗增加，电路效率严重下降，电磁干扰增大。


◆ 软开关技术

- 降低开关损耗和开关噪声。
- 使开关频率可以大幅度提高。


软开关的分类 (Types of soft switching)

◆ Cut down turn-on loss:

- ZCS on
- ZVS on

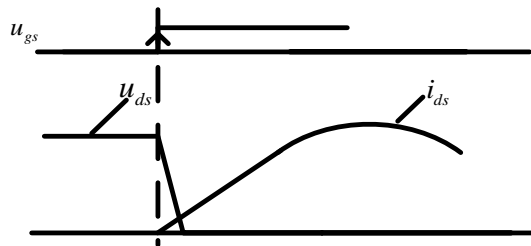


ZCS on

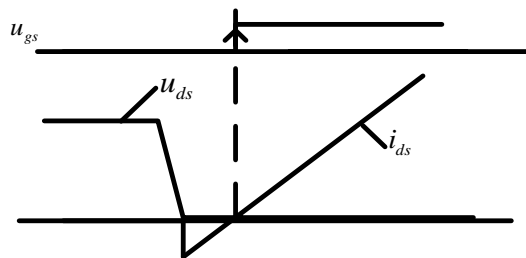


ZVS on

◆ Cut down turn-off loss:

- ZCS off
- ZVS off

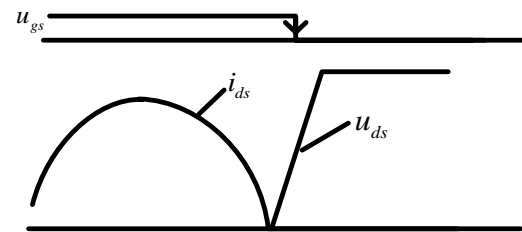


ZCS off

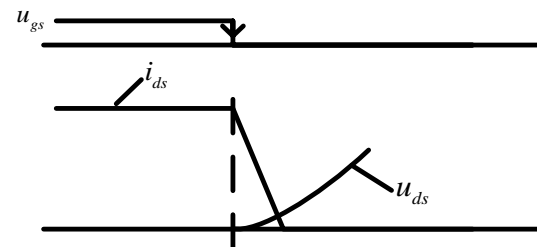

ZVS off

零电流开通Zero current switch on(ZCS on)

Turn on with zero current

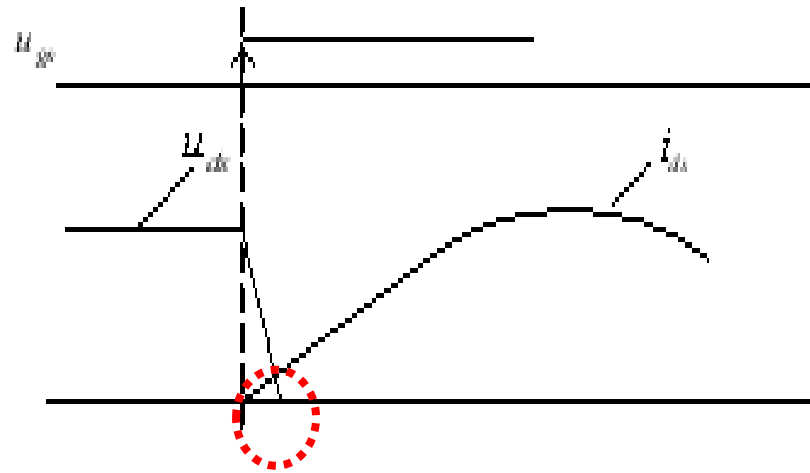


Overlap time still exist

But integral of multiplication of u_{ds} and i_{ds} is reduced

Turn-on switching loss is reduced

零电压开通Zero voltage switch on(ZVS on)

Turn on with zero voltage

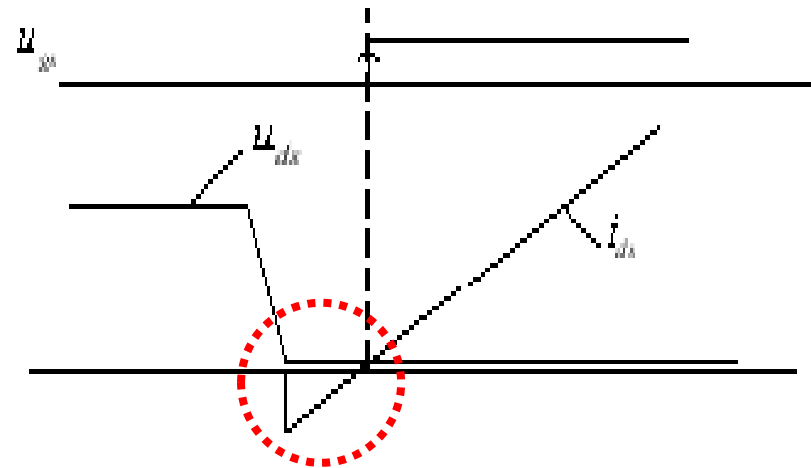


Overlap time is zero

integral of multiplication of u_{ds} and i_{ds} is 0

Turn-on switching loss is 0

零电流关断Zero current switch off(ZCS off)

Turn off with zero current

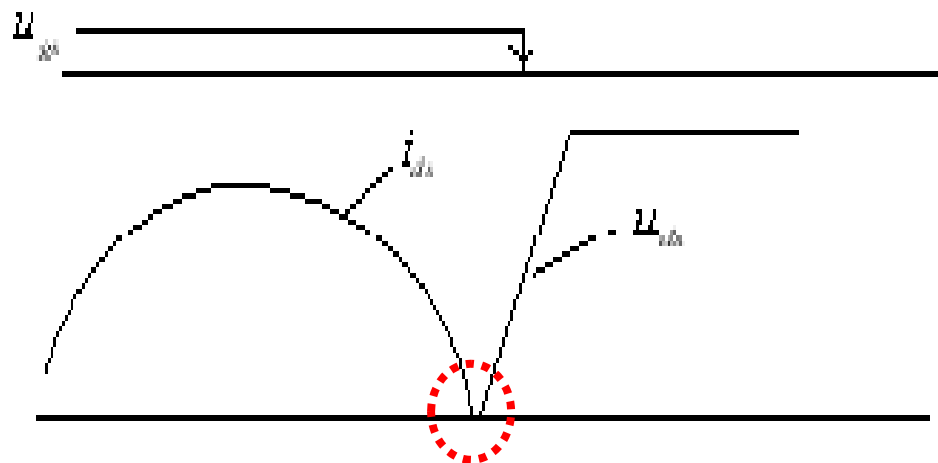


Overlap time is zero

integral of multiplication of u_{ds} and i_{ds} is 0

Turn-off switching loss is 0

零电压关断Zero voltage switch off(ZVS off)

Turn off with zero voltage

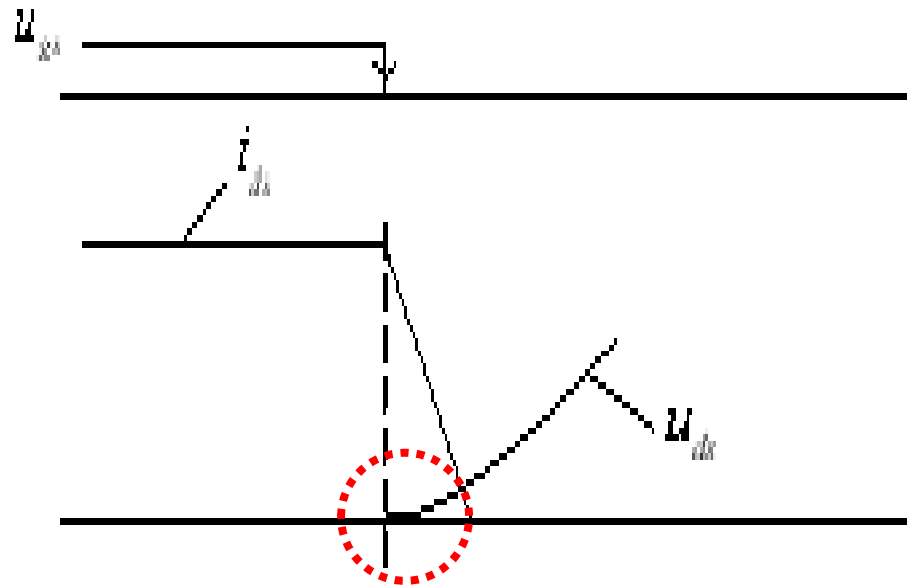


Overlap time still exist

But integral of multiplication of u_{ds} and i_{ds} is reduced

Turn-off switching loss is reduced

串联谐振逆变器 (Series resonant inverter)

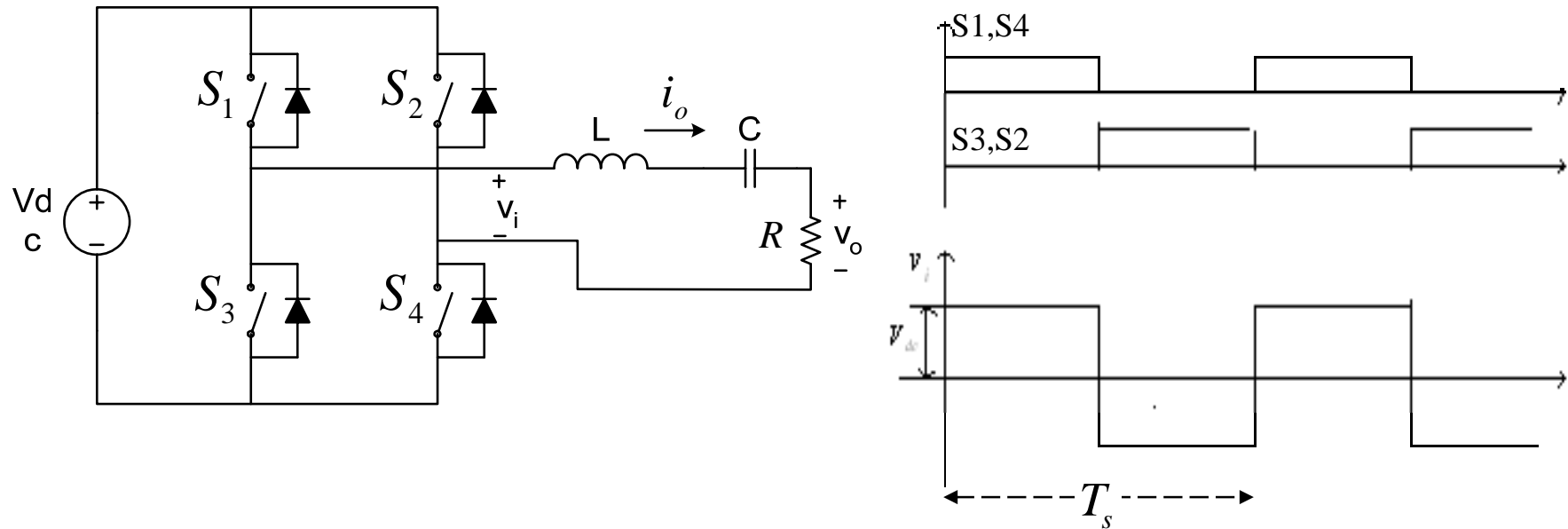


- ❑ Gate signal for S_1 and S_4 are the same
- ❑ Gate signal for S_2 and S_3 are the same
- ❑ Duty ratio of all the switches is 50%
- ✓ S_1 and S_3 operate complementally
- ✓ S_2 and S_4 also operate complementally
- ✓ V_i is square wave, freq: $f_s=1/T_s$

基波等效电路 (Equivalent circuit)

简化:分析基波分量之间的关系, 而忽略谐波分量的作用

- ◆ V_i : square waveform Amplitude: $\pm V_{dc}$ freq: f_s
- ◆ Amplitude of fundamental component

$$V_1 = \frac{4V_{dc}}{\pi}$$

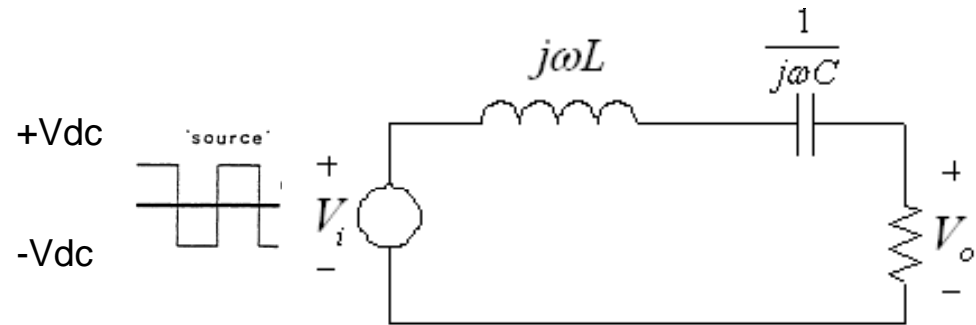

- ◆ In-out ratio:

$$\frac{V_o}{V_i} = \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = \frac{1}{\sqrt{1 + (\frac{\omega L}{R} - \frac{1}{\omega RC})^2}}$$

$$\omega = 2\pi f_s$$

f_s : Switching frequency

输入输出比 (Input-output ratio)

$$\frac{V_o}{V_i} = \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = \frac{1}{\sqrt{1 + \frac{L}{R^2 C} (\omega \sqrt{L} \sqrt{C} - \frac{1}{\omega \sqrt{L} \sqrt{C}})^2}}$$


◆ Quality factor

$$Q = \frac{\omega_o L}{R} = \frac{1}{\omega_o R C} = \frac{\sqrt{\frac{L}{C}}}{R}$$

- Natural resonant frequency $\omega_o = 2\pi f_o = \frac{1}{\sqrt{LC}}$


$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + Q^2 (\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega})^2}} = \frac{1}{\sqrt{1 + Q^2 (\frac{f}{f_o} - \frac{f_o}{f})^2}}$$

输入输出比 (Input-output ratio)

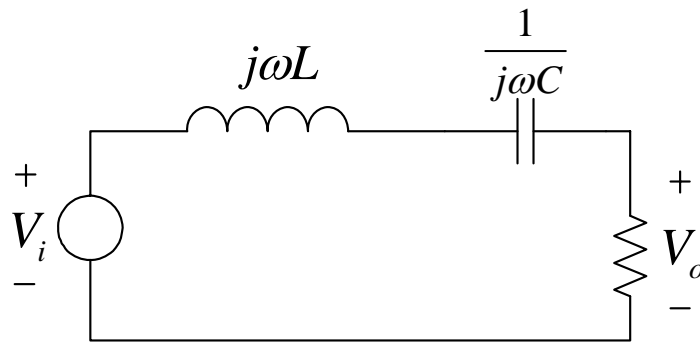

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + Q^2 \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega} \right)^2}}$$

$$Q = \frac{\sqrt{L/C}}{R}$$

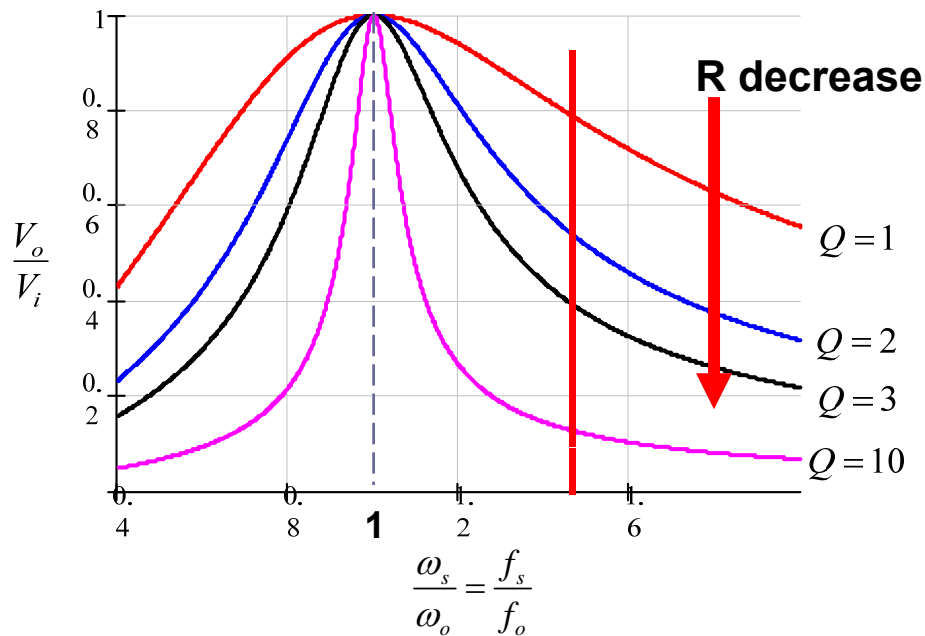


- Common point: ($f^*=1$, $V_o/V_i=1$)
- Q increases, then V_o decrease w/ fixed f_s
- $f^*>1$, inductive load, delayed phase
- $f^*<1$, capacitive load, leading phase

V_o vs. f^* curve w/ constant Q

- $f^*>1$, decrement function
- $f^*<1$, increment function
- V_o can be regulated by changing f_s


$$f^* = f_s / f_o$$

Inverter stage analysis

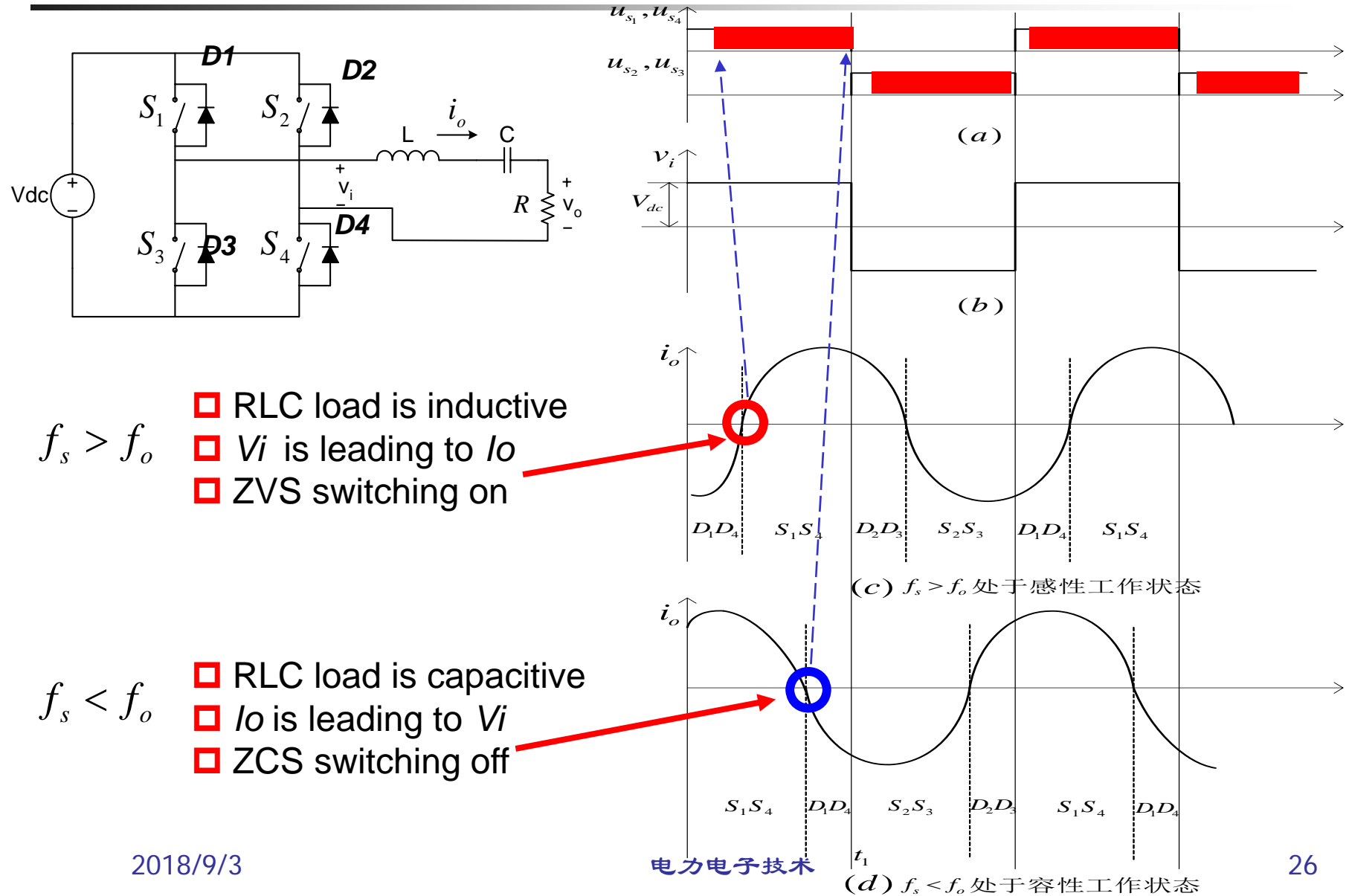


Inverter bridge variations

● Full bridge

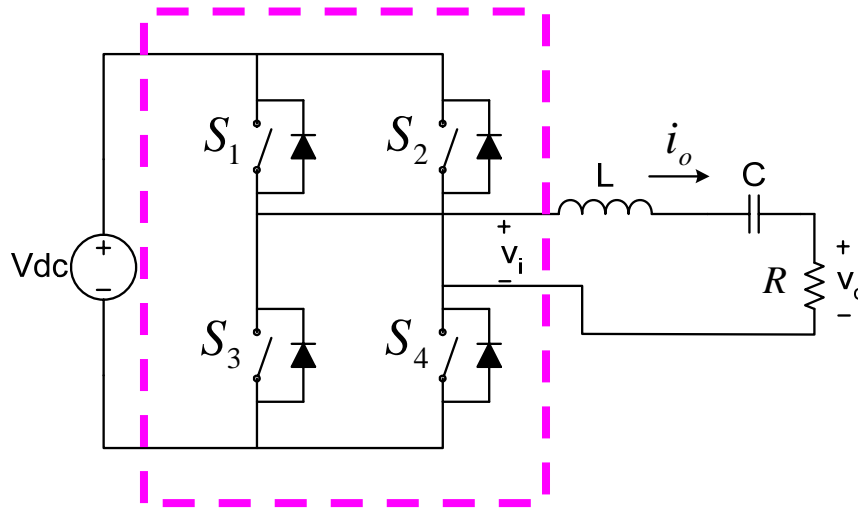


● Half bridge

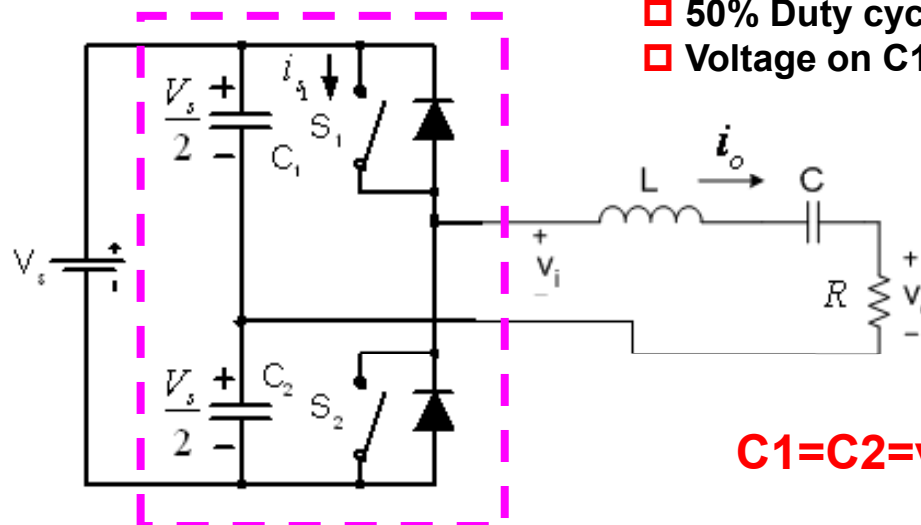

- S1 and S2 gate signal are complement
- 50% Duty cycle
- Voltage on C1 and C2 are constant, $=V_s/2$


C1=C2=very large

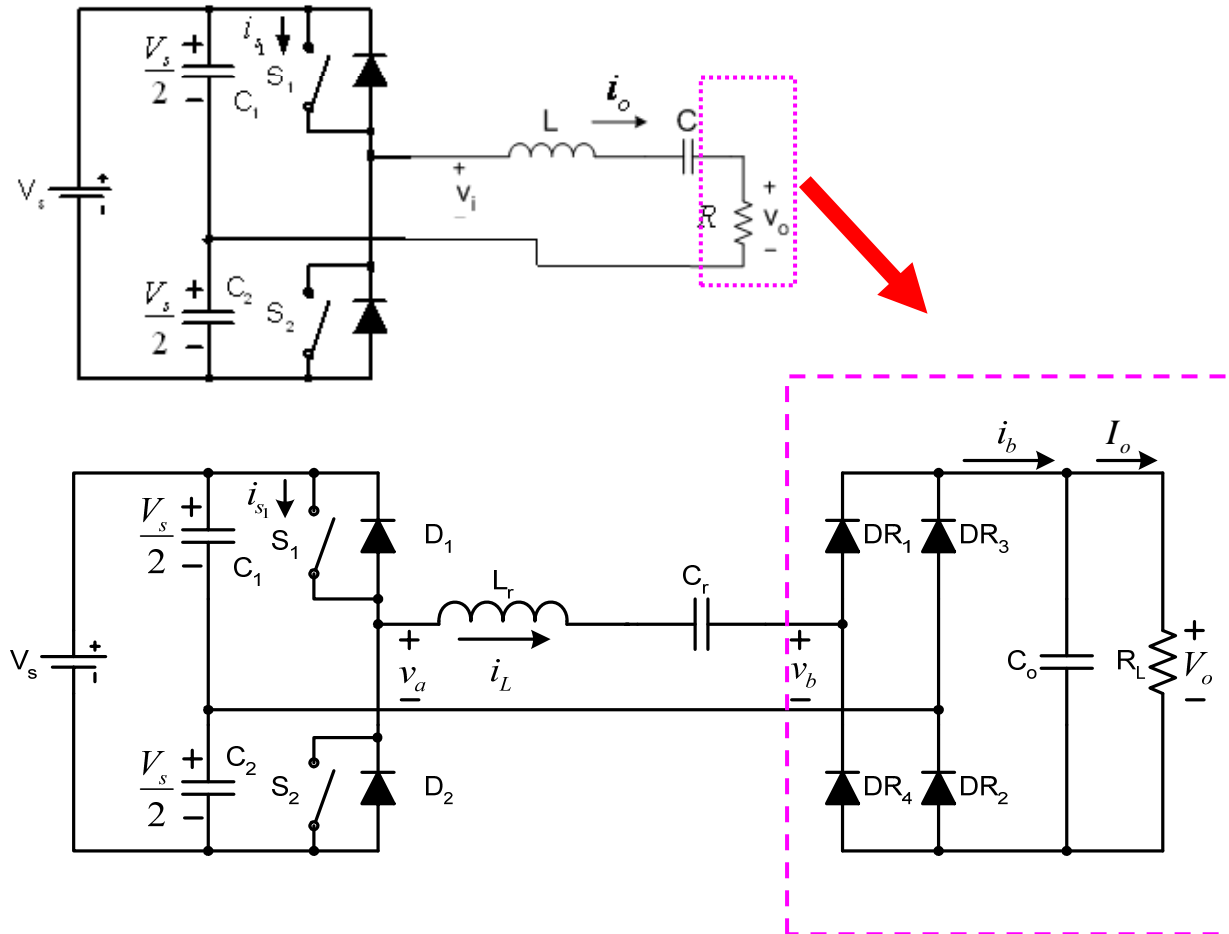串联谐振变换器 (Series resonant DC/DC converter)




R in the resonant inverter is replaced by a full bridge rectifier


感性方式 (Inductive operation)

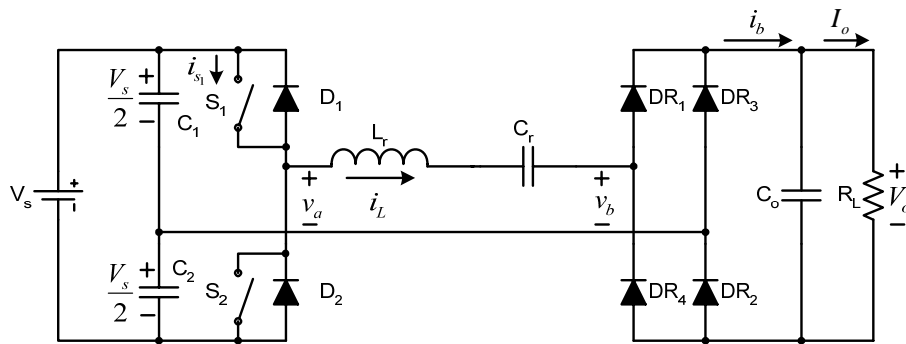


- ◆ Resonant current is lagging
- ◆ S1 and S2: ZVS switching on
- ◆ S1 and S2 turn off loss reduction: Parallel capacitor on switches

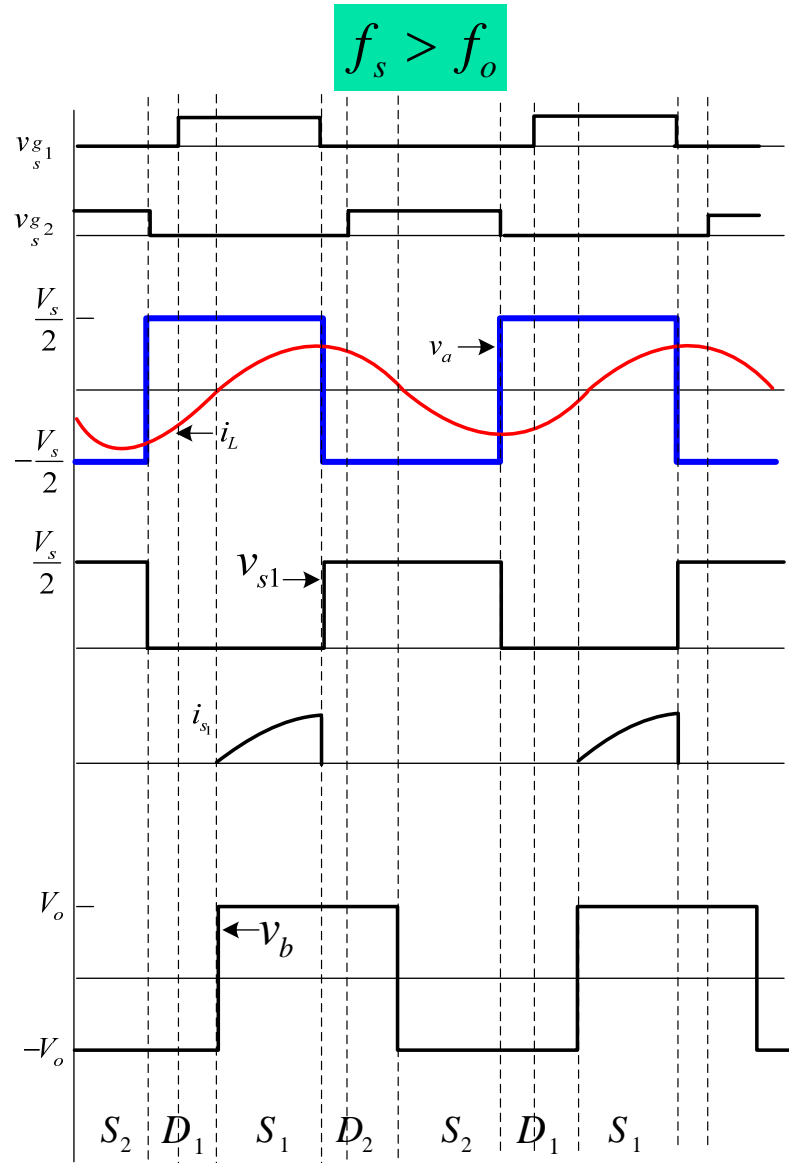

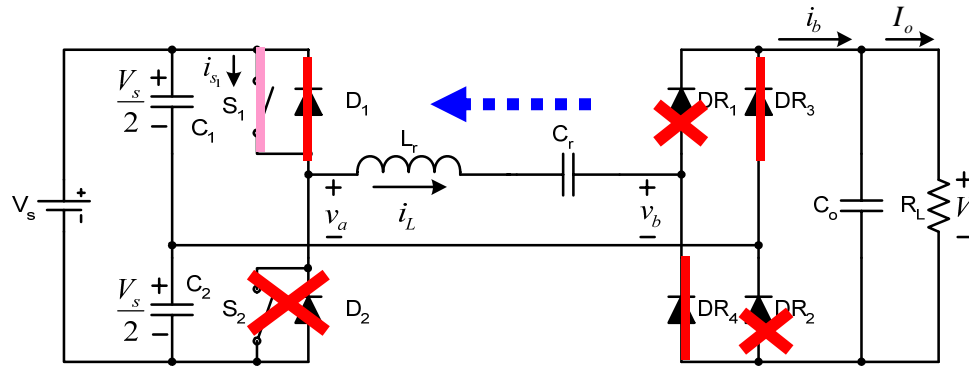
stage 1:[t1,t2] Reactive power flow stage



- ◆ Half bridge:
 - D1 is on, S1 is ready to turn on
 - S2(D2) is off
- ◆ Rectifier:
 - DR3, DR4 are on
 - DR1,DR2 are off
- ◆ Since $v_a > 0$ & $i_L < 0$, power flow is reverse
- ◆ Stage end condition: i_L increases to zero
 - D1 is conducting
 - S1 is ready to be turned on with ZVS

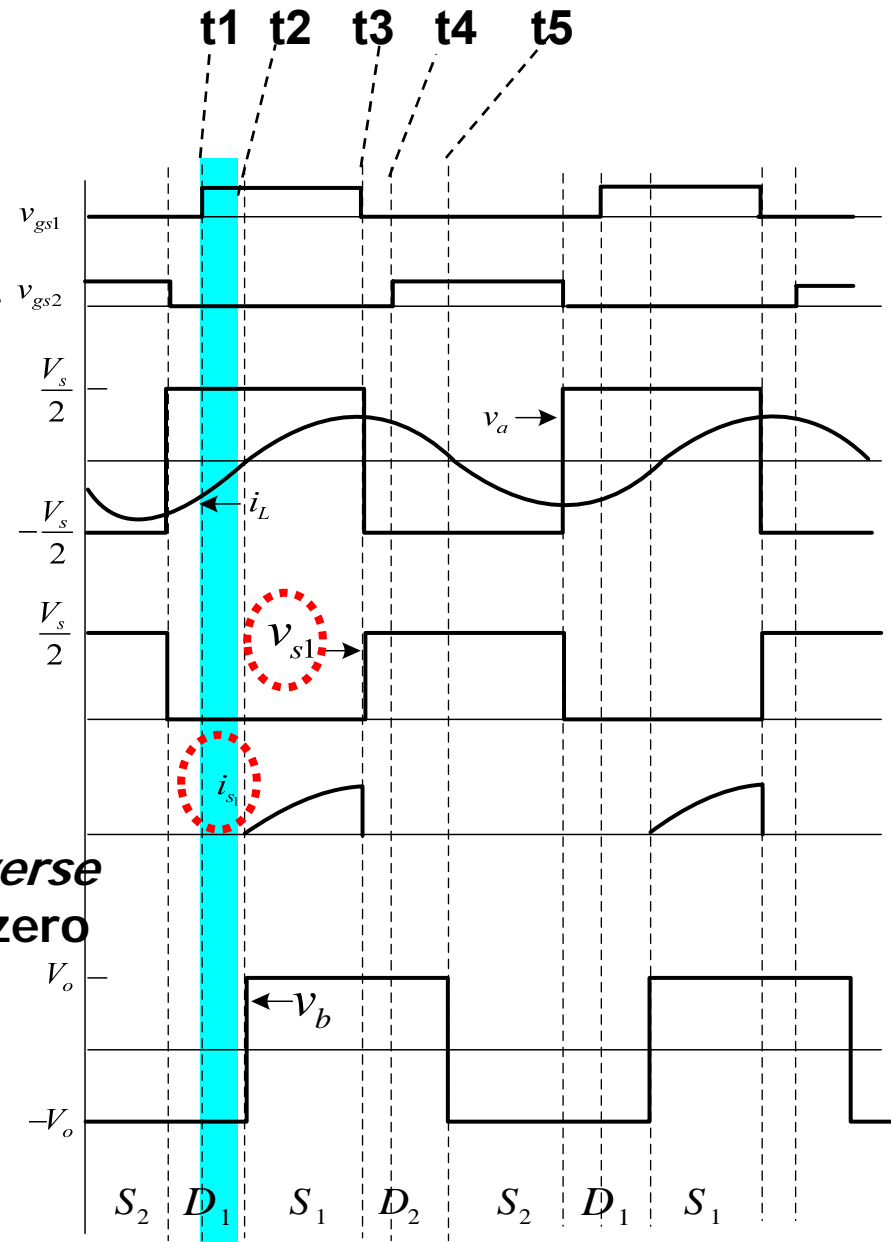

stage 2:[t2,t3] Active power flow stage

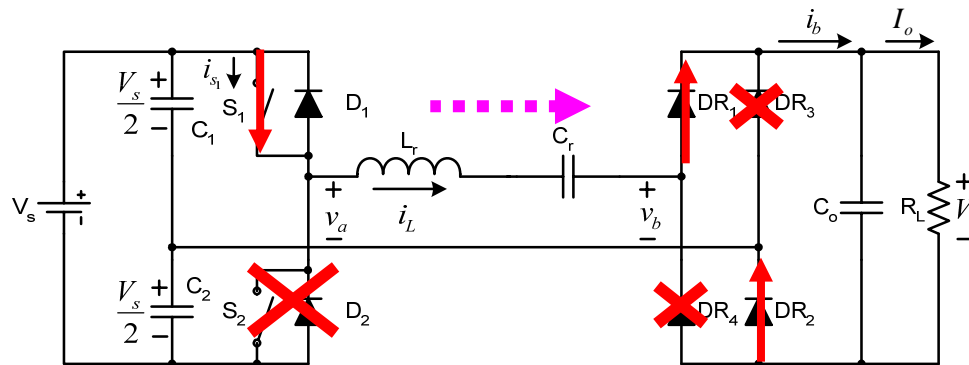


Half bridge: **S1 is on, D1 is off**
S2(D2) is off


Rectifier: **DR3, DR4 are off**
DR1, DR2 are on

Since $V_a > 0$ & $I_L > 0$, power flow is forward

Stage end condition: V_{gs1} steps down

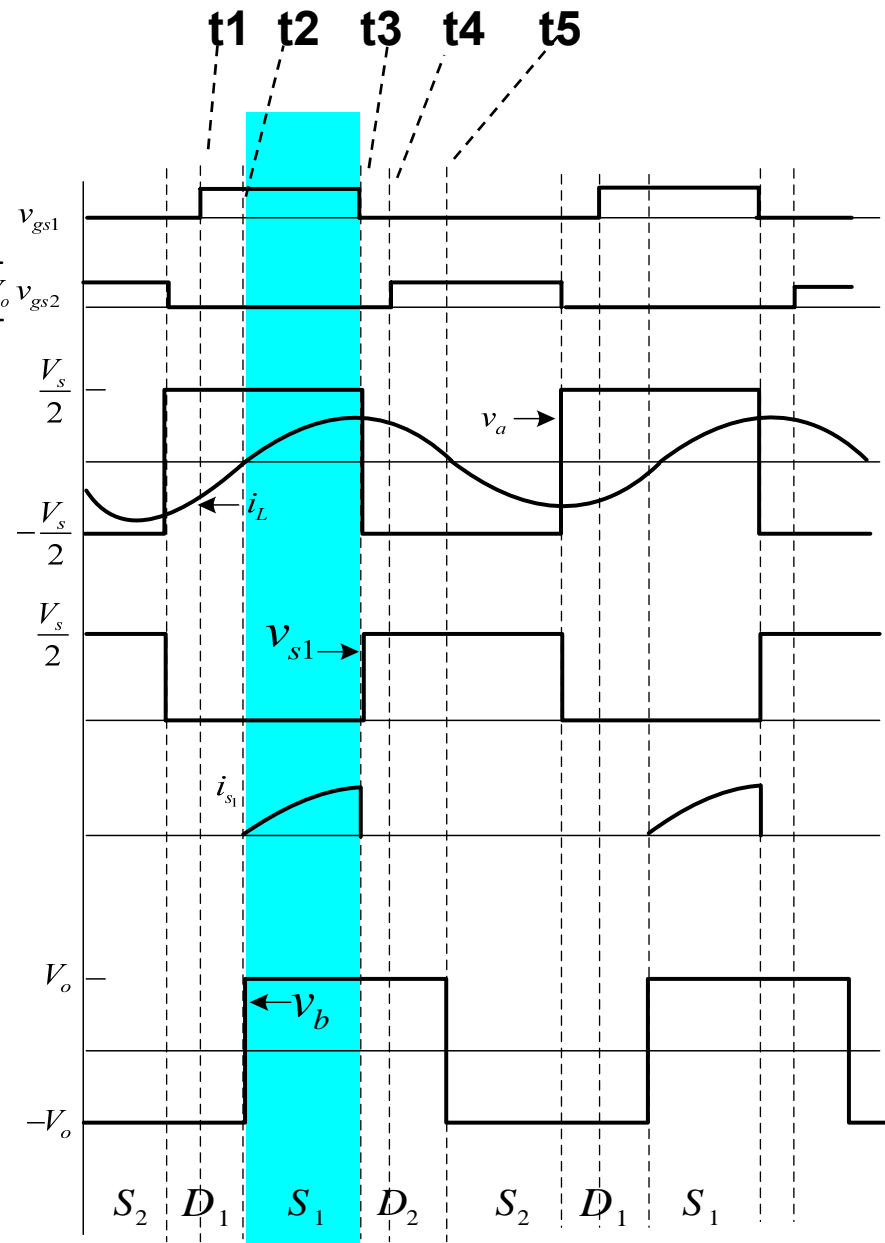

Capacitance of MOSFETs

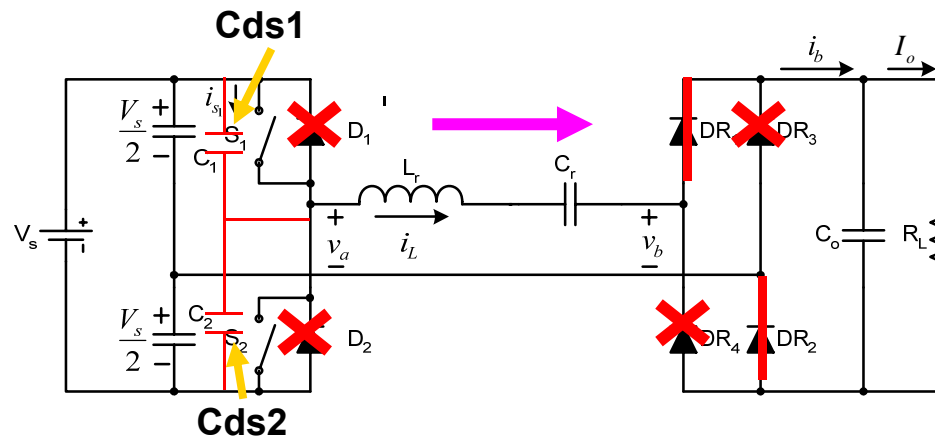

Since t_3 to t_4 is short, i_L is taken to be constant


$$v_{Cds1} + v_{Cds2} = V_s$$

v_{Cds1} Linearly increases from 0 to V_s


V_{Cds2} Linearly decreases from V_s to 0

Stage end condition:


$V_{c ds2}=0$, then D2 is turned on

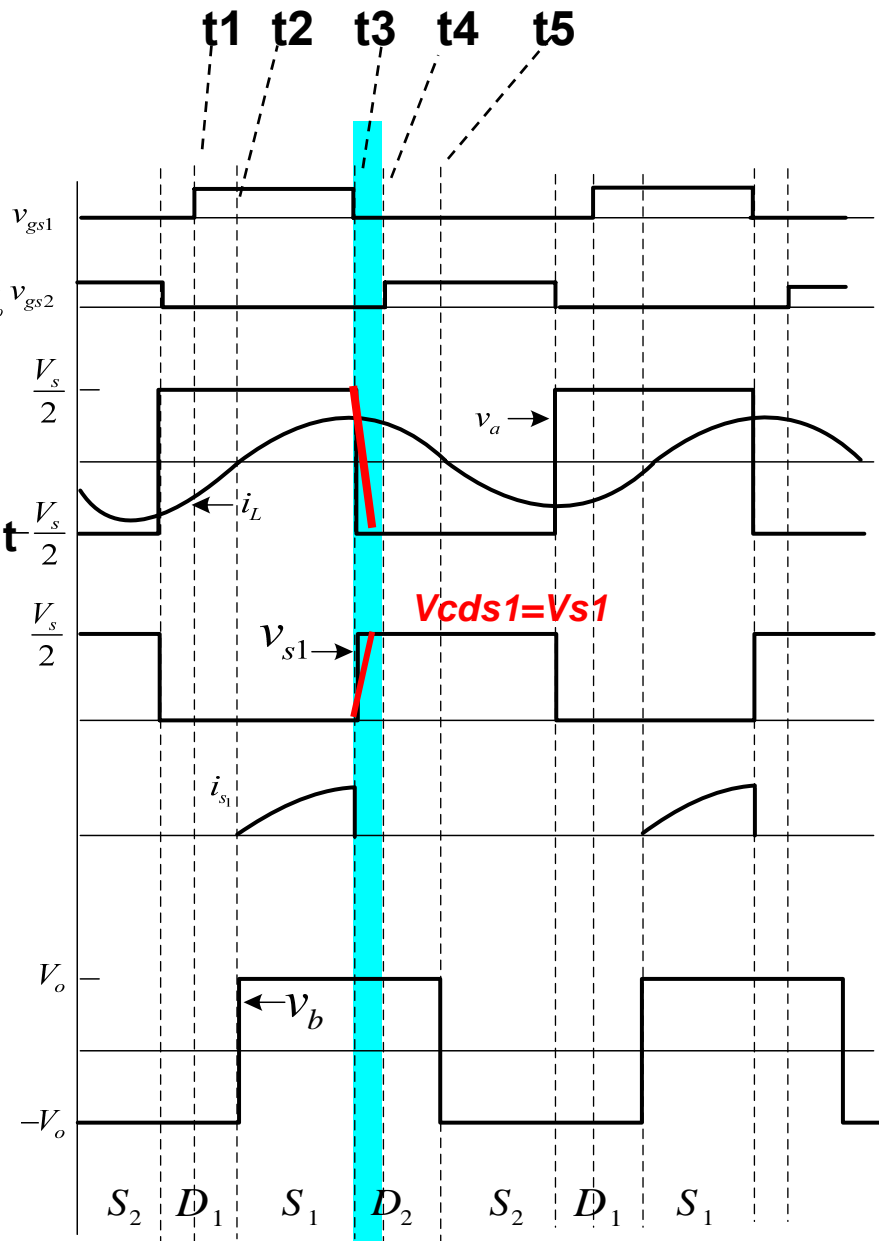

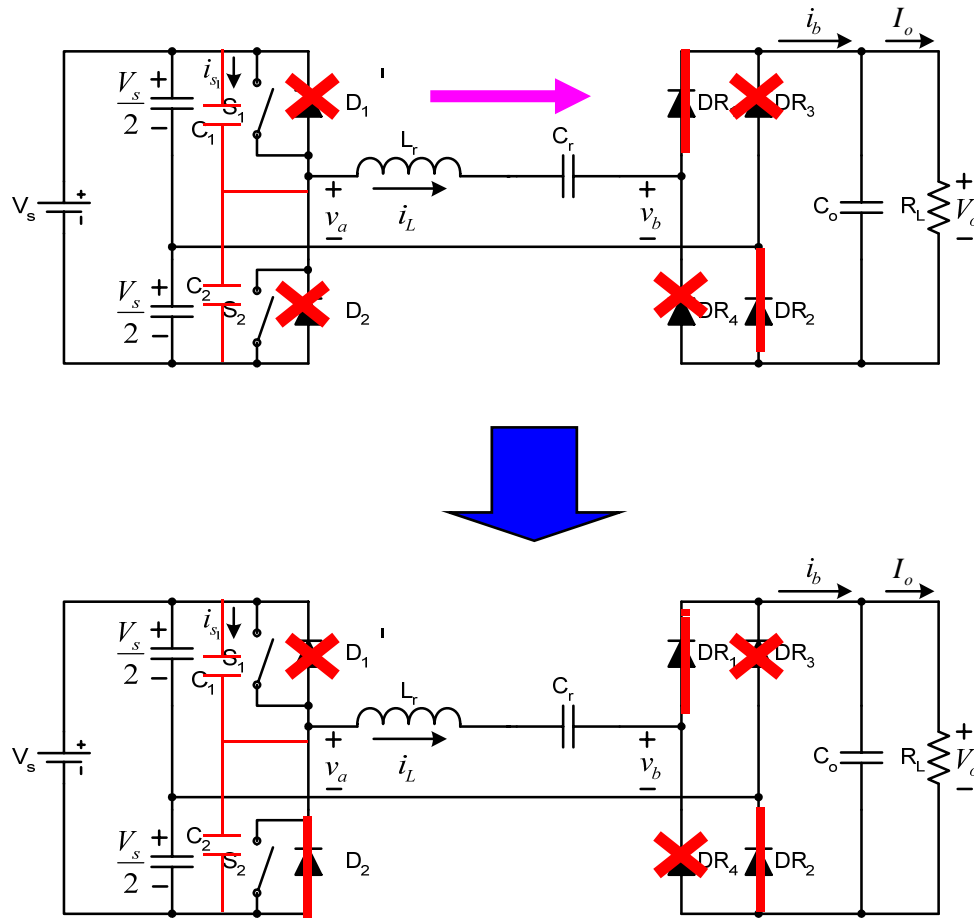
stage 3: [t3,t4] Resonant stage (continued)



- D2 is conducting
- S2 is ready to be turned on with ZVS

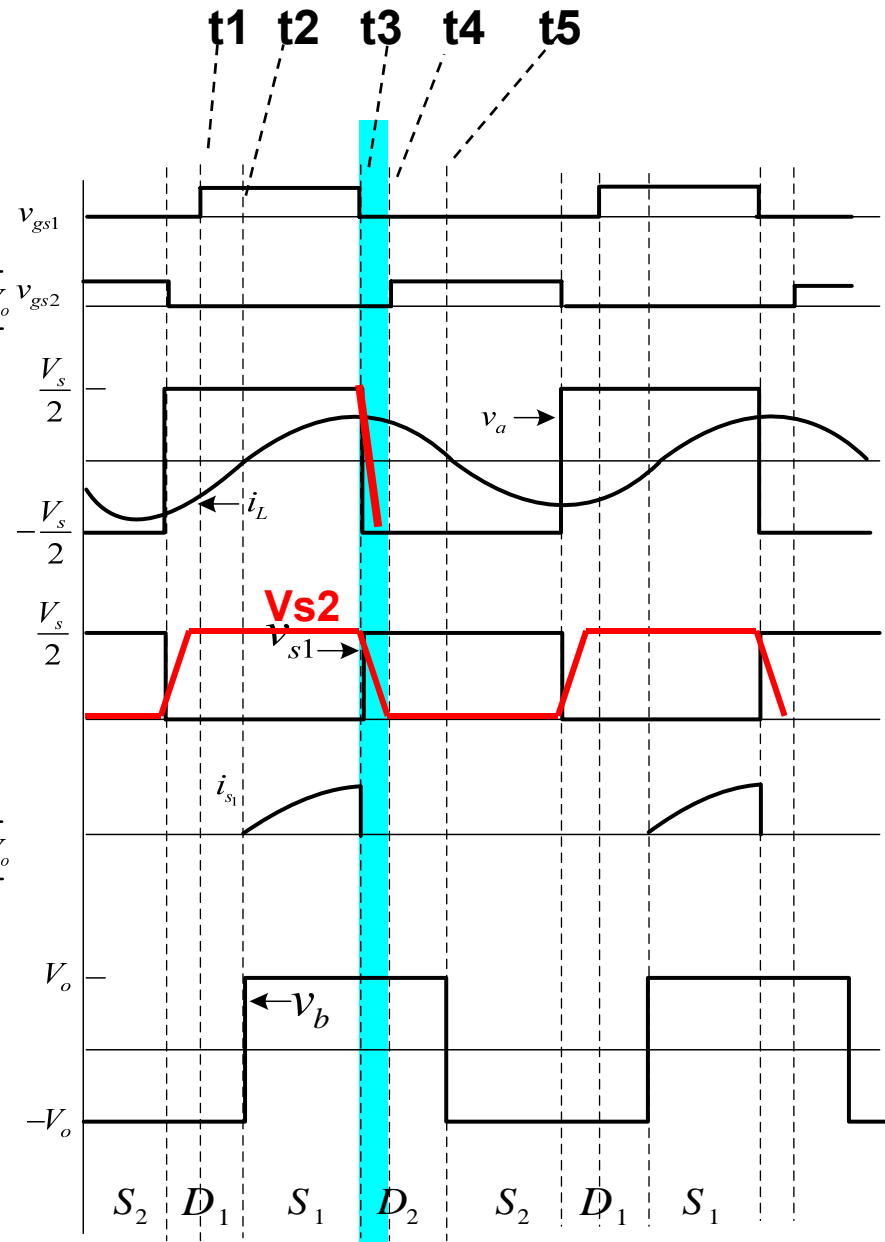

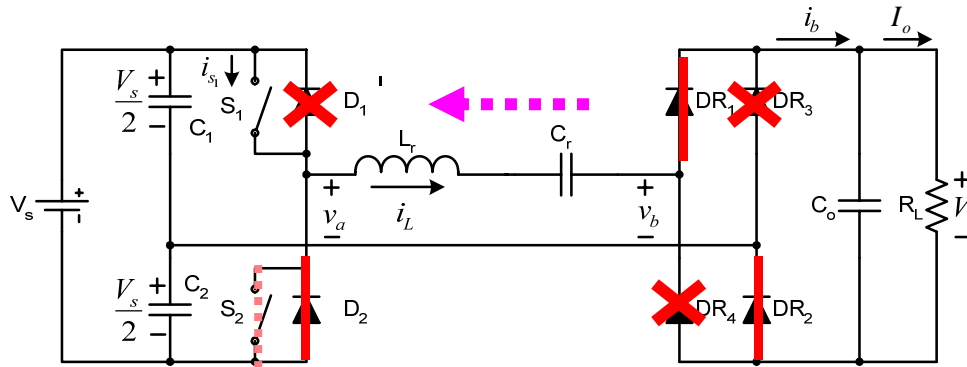stage 4:[t4,t5] reactive power flow stage



Half bridge:

S1(D1) is off
D2 is on, S2 ?


Rectifier:

DR3, DR4 are off
DR1, DR2 are on


Since $V_a < 0$ & $I_L > 0$, power flow is reverse

Stage end condition: l_L decreases to zero

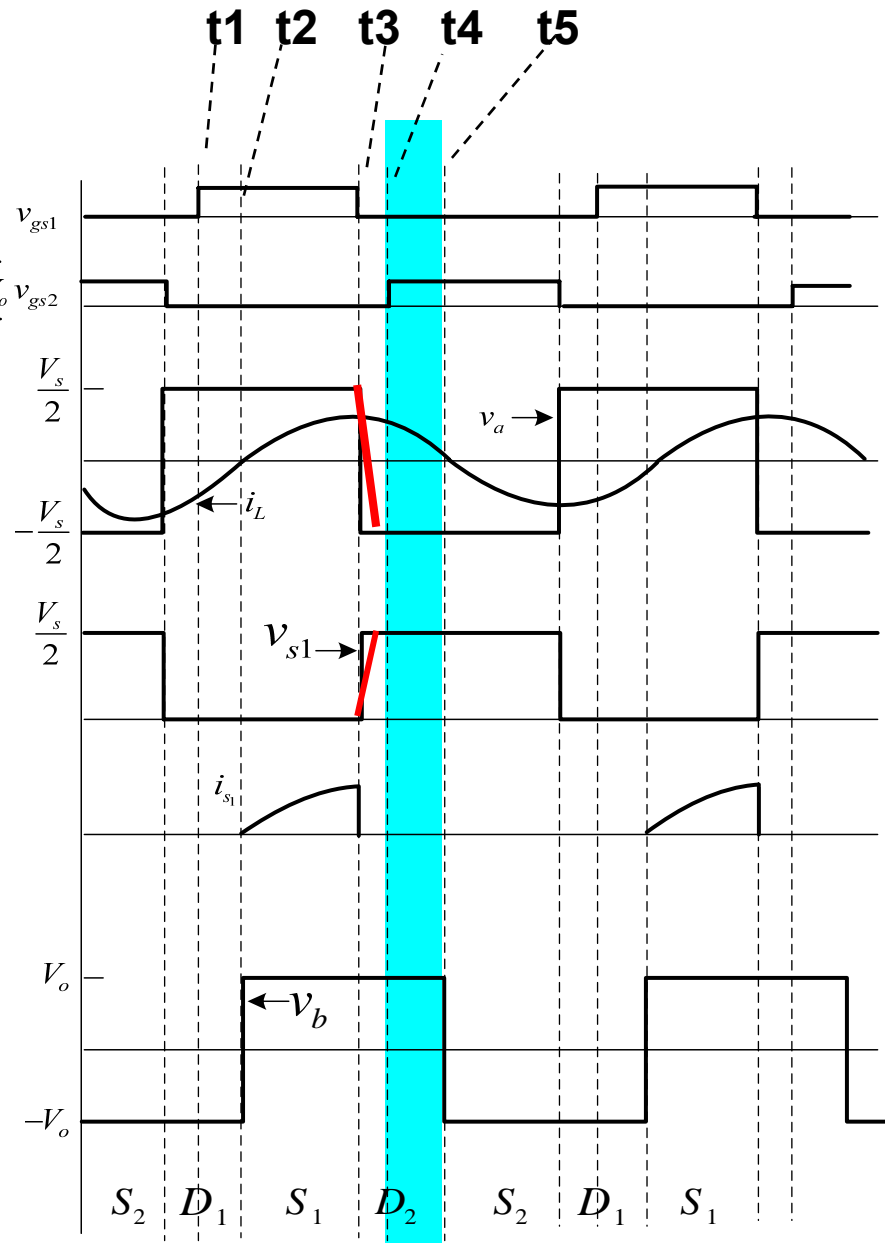D2 is conducting and create the condition of zero voltage turn-on for S2




半桥逆变器的输出基波 (Half bridge inverter)

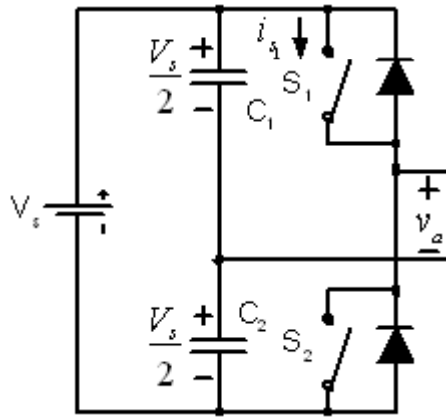

- ◆ v_a Square wave with amplitude $v_s/2$
- ◆ Amplitude of the fundamental component
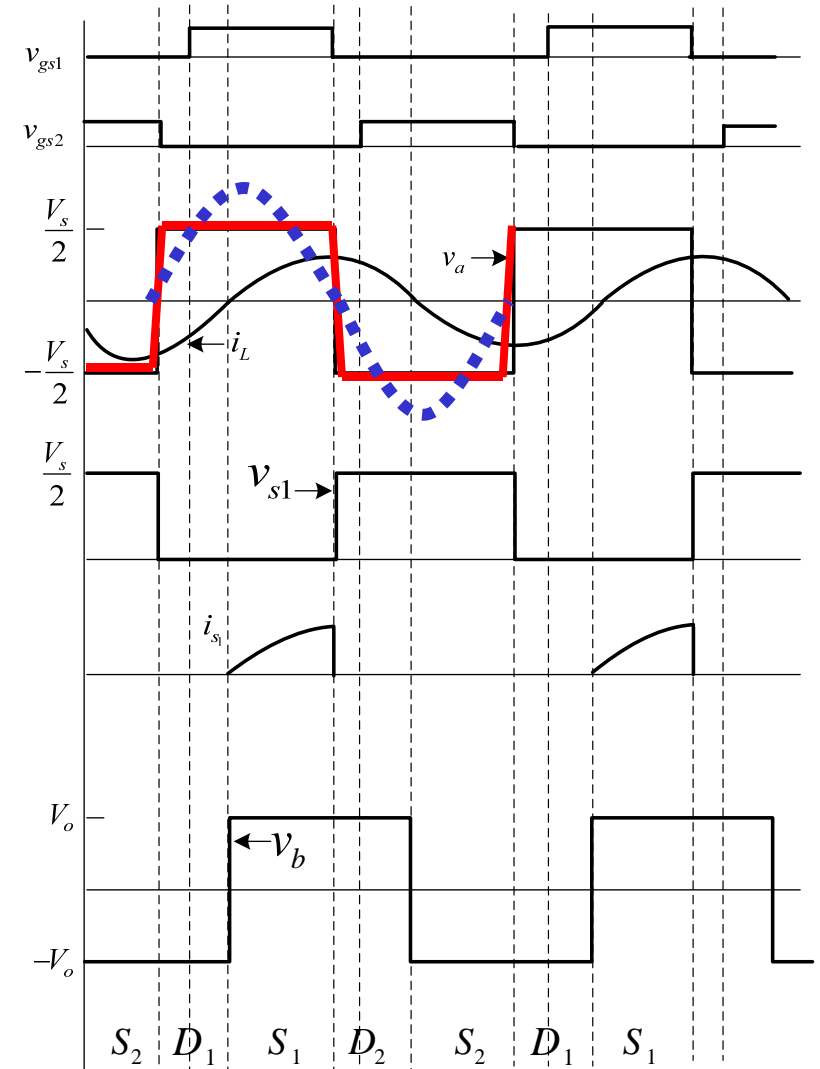
$$V_{a1} = \frac{4(V_s / 2)}{\pi} = \frac{2V_s}{\pi}$$



容性输出整流器 (Capacitor filtered rectifier)



- ◆ Assumption: output V_o is constant
- ◆ Input voltage v_b is square wave. Amplitude of the fundamental component

$$V_{b1} = \frac{4V_o}{\pi}$$

- ◆ Since resonant circuit has filter property, its current can be seen as Sine wave.

- ◆ i_L Amplitude: I_{L1}
- ◆ I_b is rectified current of Averaged value of i_b

$$I_b = \frac{2I_{L1}}{\pi}$$

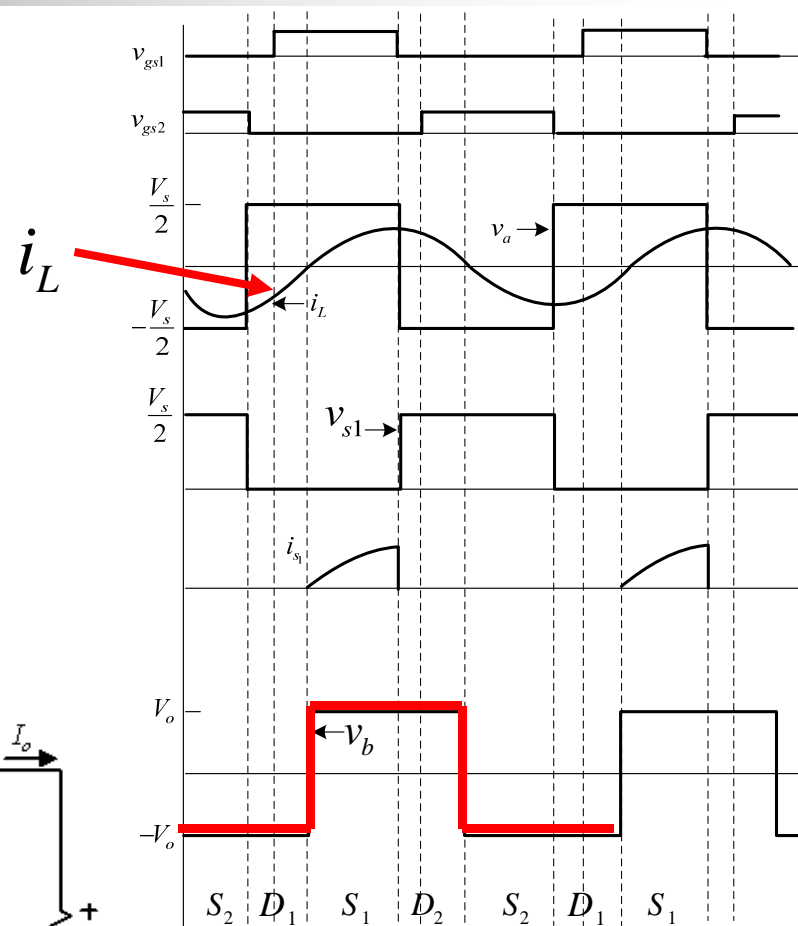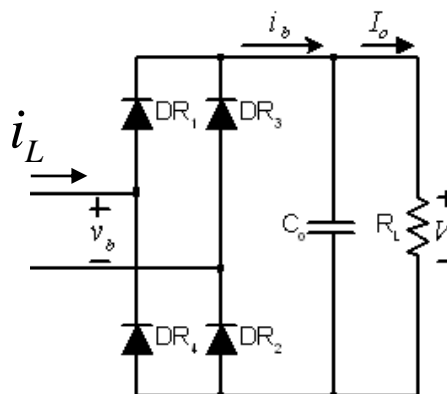

Capacitor filtered rectifier (continued)


$$I_b = I_o$$

- Output current
- ◆ Resonant circuit current amplitude


$$I_{L1} = \frac{\pi}{2} I_o$$

- ◆ Capacitor filtered rectifier can be replaced by an equivalent resistor
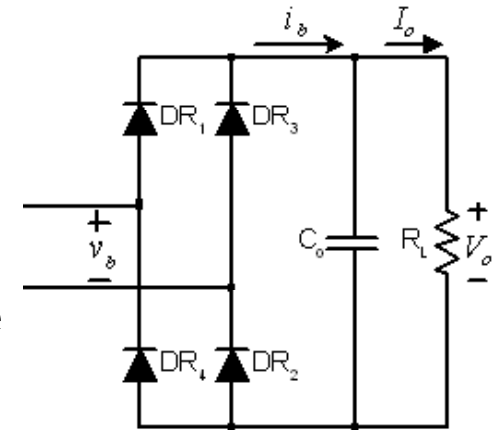
$$R_e = \frac{V_{b1}}{I_{L1}} = \frac{\frac{4V_o}{\pi}}{\frac{\pi I_o}{2}} = \frac{8}{\pi^2} \frac{V_o}{I_o} = \frac{8}{\pi^2} R_L$$




基波等效电路 (Fundamental equivalent circuit)

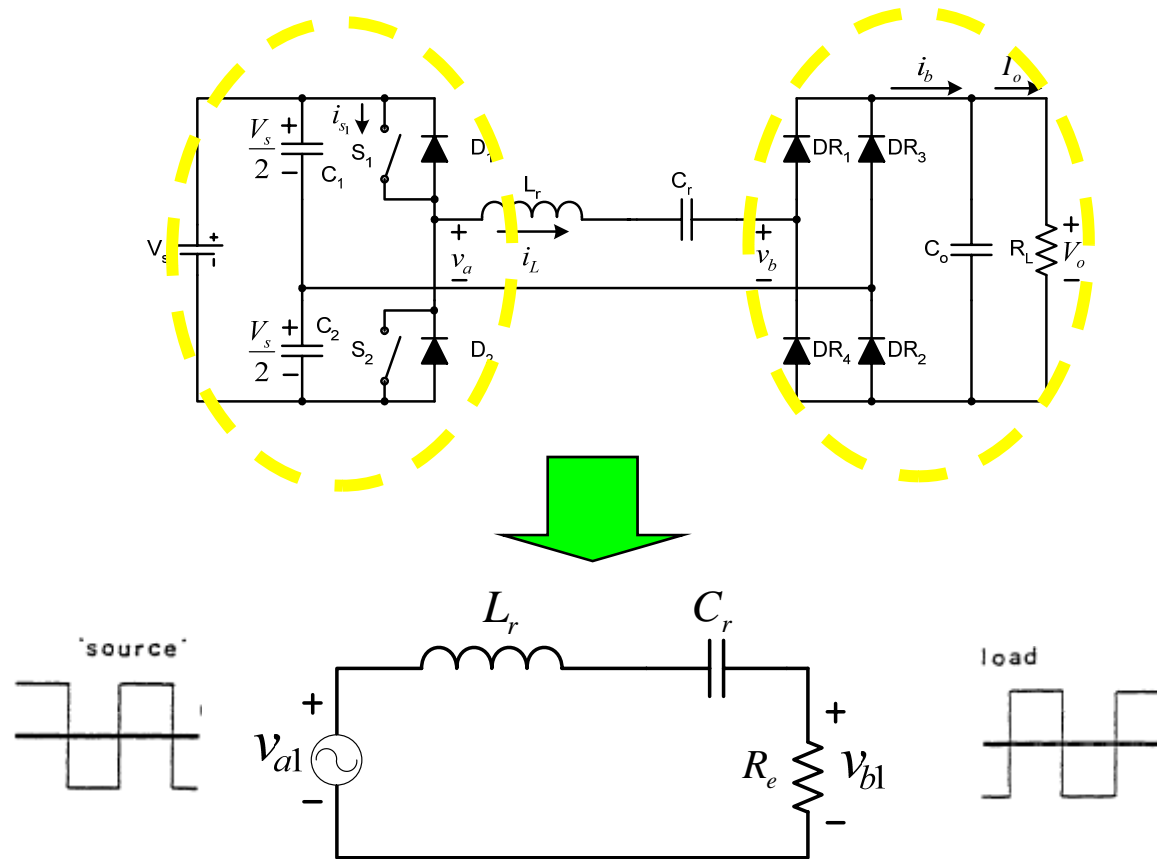

$$\frac{V_{b1}}{V_{a1}} = \frac{\frac{4V_o}{\pi}}{\frac{2V_s}{\pi}} = \left| \frac{R_e}{R_e + j(\omega_s L_r - \frac{1}{\omega_s C_r})} \right|$$

直流电压比 (DC/DC conversion ratio)
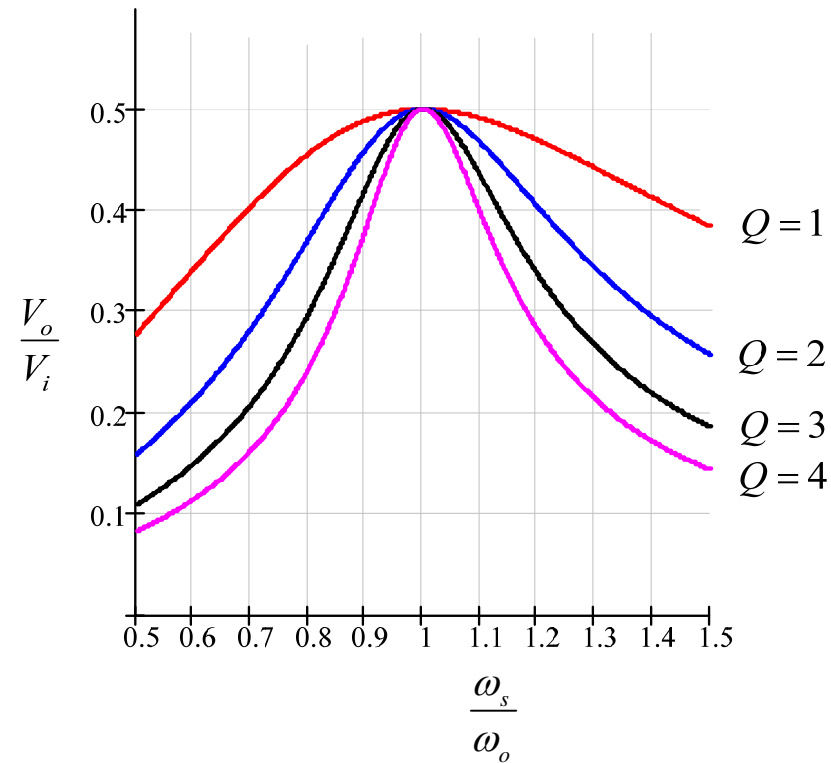
$$\frac{V_o}{V_s} = \frac{1}{2\sqrt{1 + Q^2\left(\frac{\omega_s}{\omega_o} - \frac{\omega_o}{\omega_s}\right)^2}} \quad Q = \frac{\omega_o L_r}{R_e}$$




Output V_o can be controlled by changing switching frequency f_s

Capacitive operation


$$\frac{f_o}{2} < f_s < f_o$$

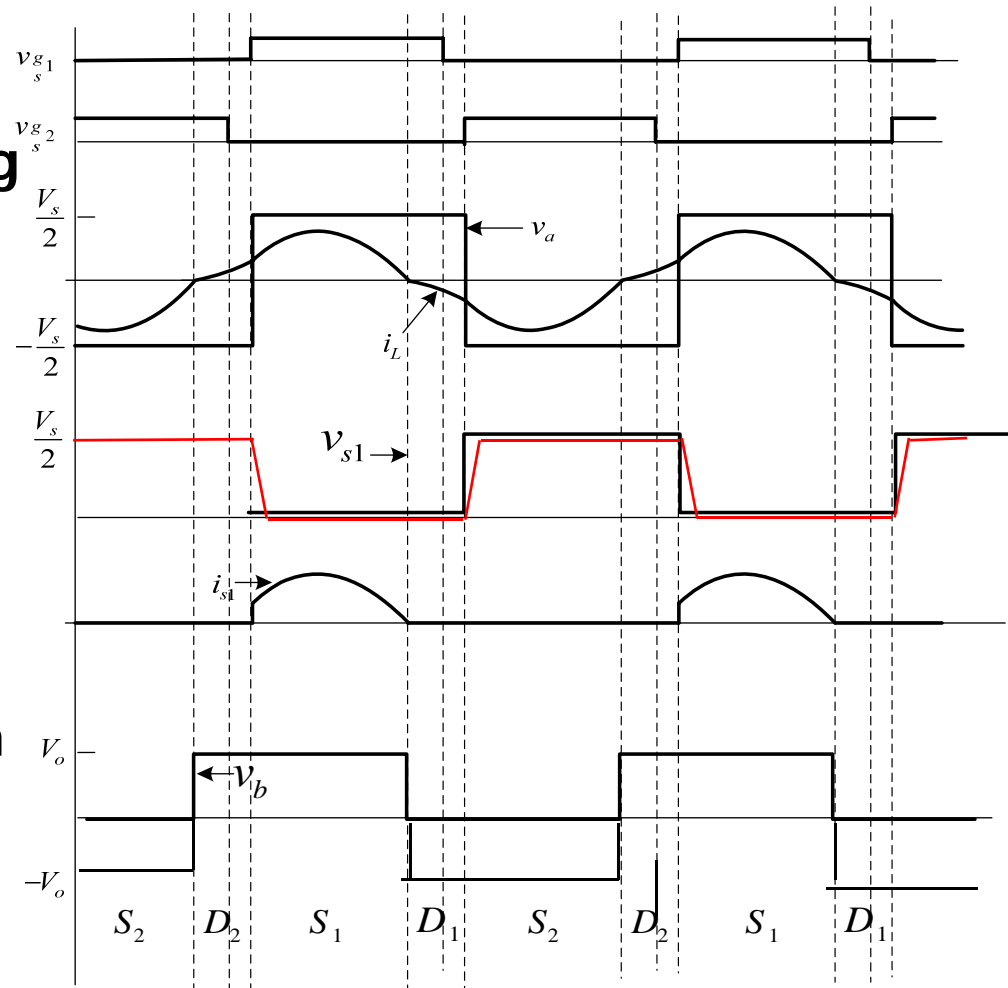- ◆ Resonant current is leading
- ◆ S1 and S2: ZCS switching off
- ◆ Suited to thyristor converter
- ◆ Larger turn-on loss:
- ◆ Body diode reverse recovery
- ◆ There is larger distortion in resonant current




零电流关断与零电压开通 (ZCS and ZVS switching)

Zero Current Switching

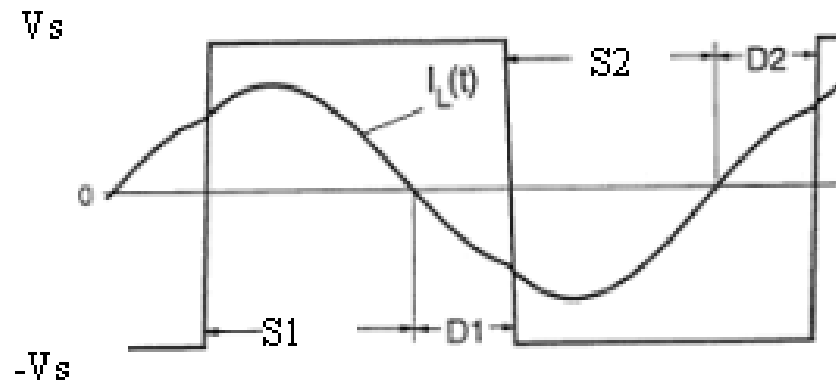

$f_s < f_0$, Capacitive load

Zero Voltage Switching


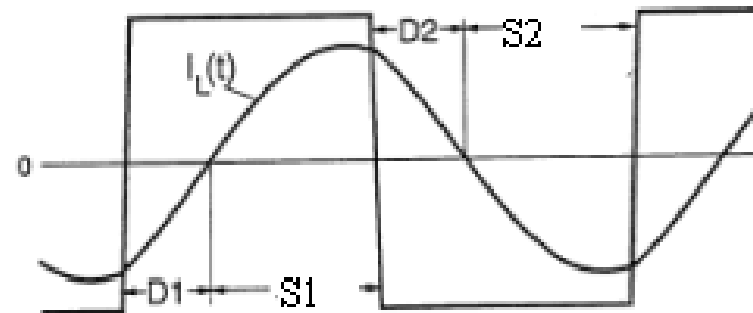


$f_s > f_0$, Inductive load


感性方式的优势 (Advantages of inductive mode)

- ◆ No turn-on loss in the power switches due to ZVS turn-on
- ◆ Lossless snubber during turn-off due to ZVS turn-off
- ◆ High speed anti-parallel diodes are not necessary, body diode of MOSFETs are ok
- ◆ Smaller transformer due to higher frequency operation
- ◆ Smaller output filter

Topology variations

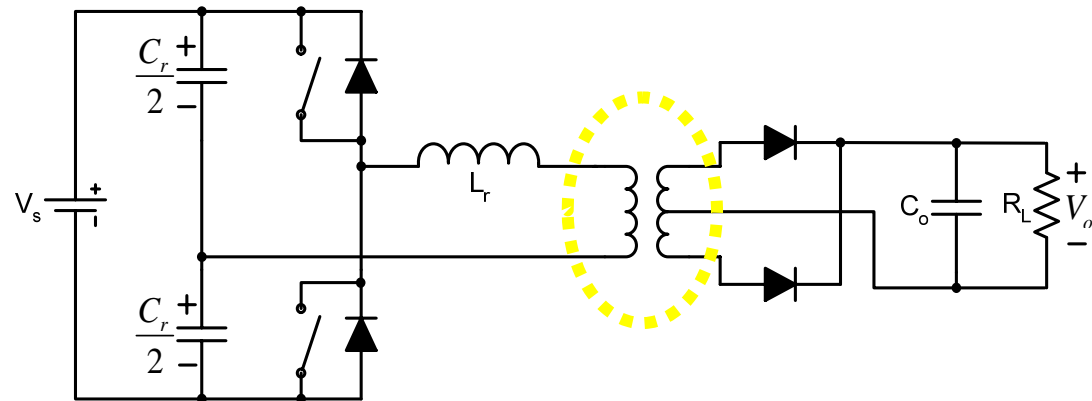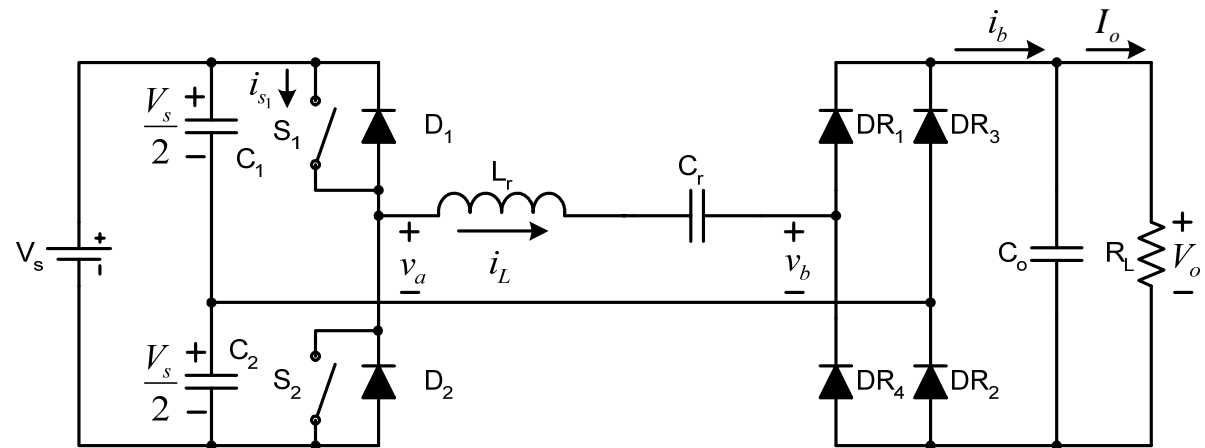


Zero Current quasi resonant converter

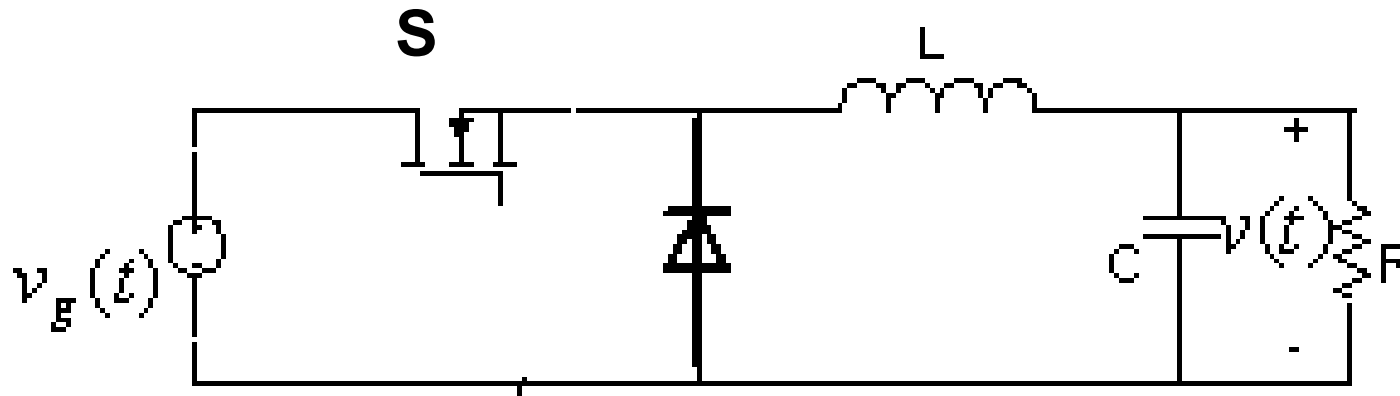


ZCS: How can the current through the switch naturally decrease to zero ?

Resonant switching concept

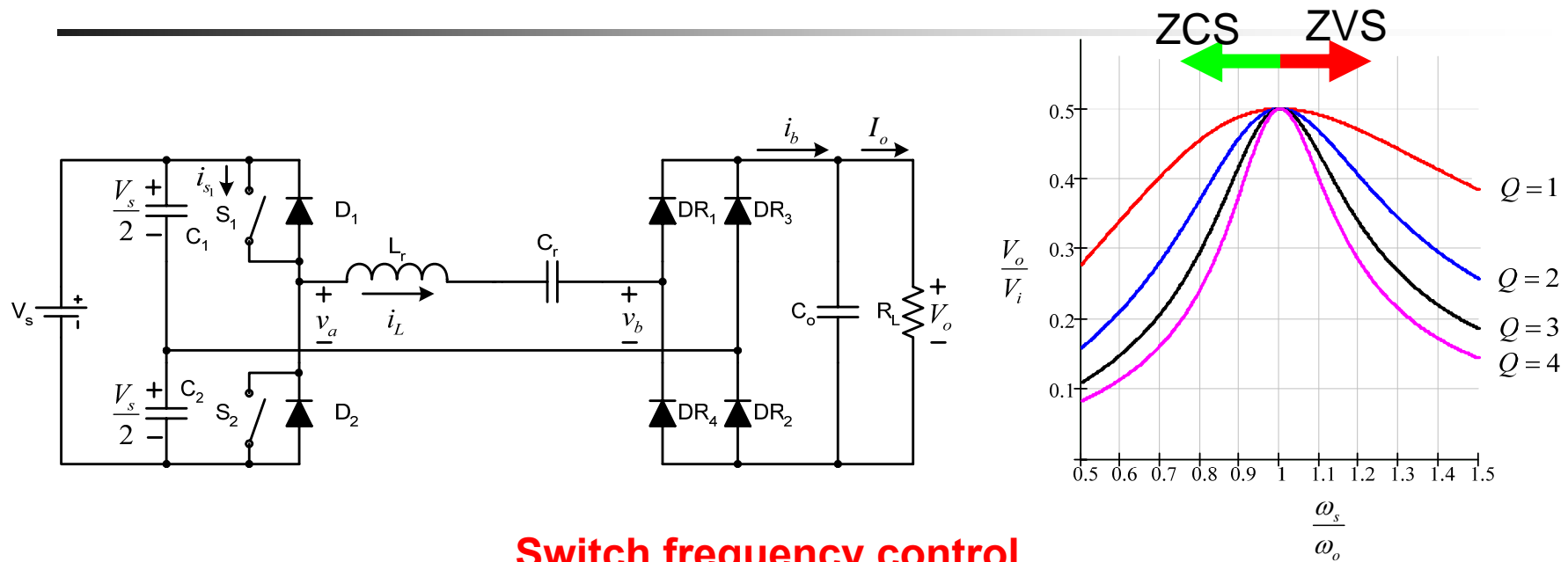


Switch frequency control

Zero Current Switching


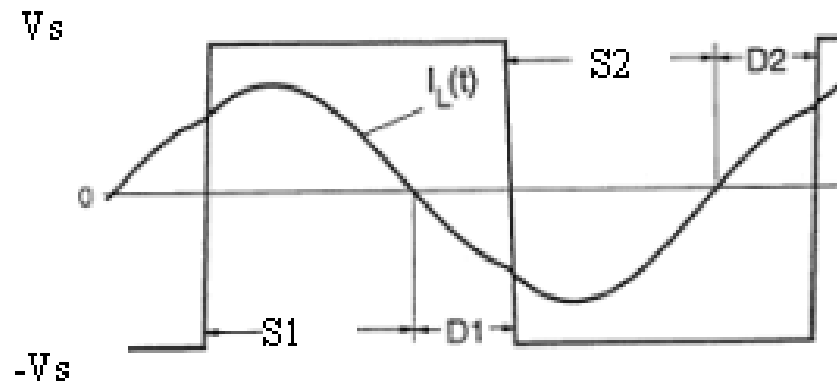


Zero Voltage Switching

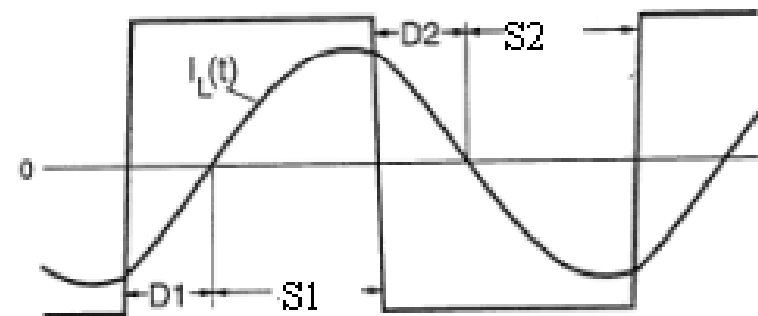


Introduce resonant switching concept to DC/DC converters

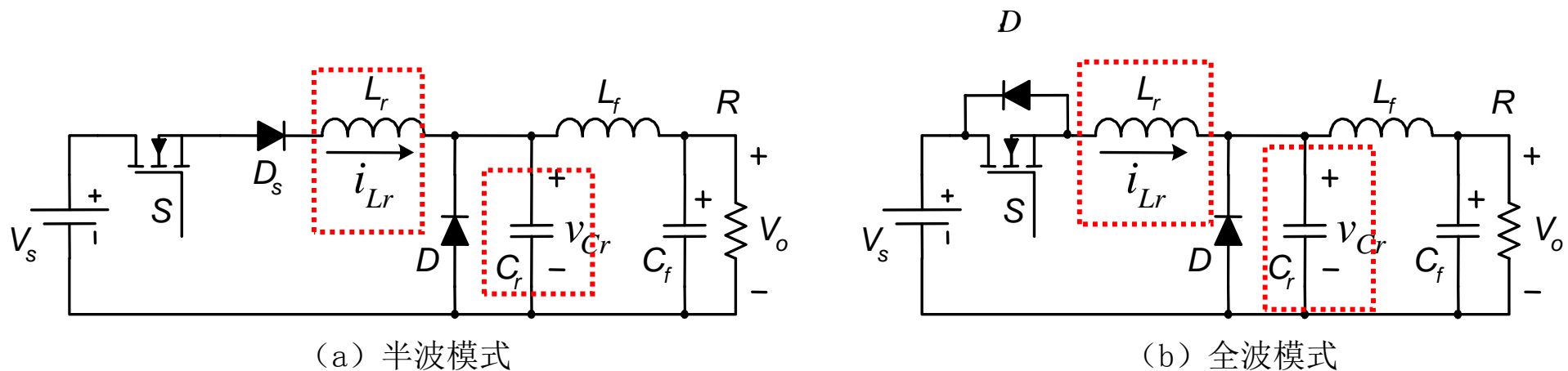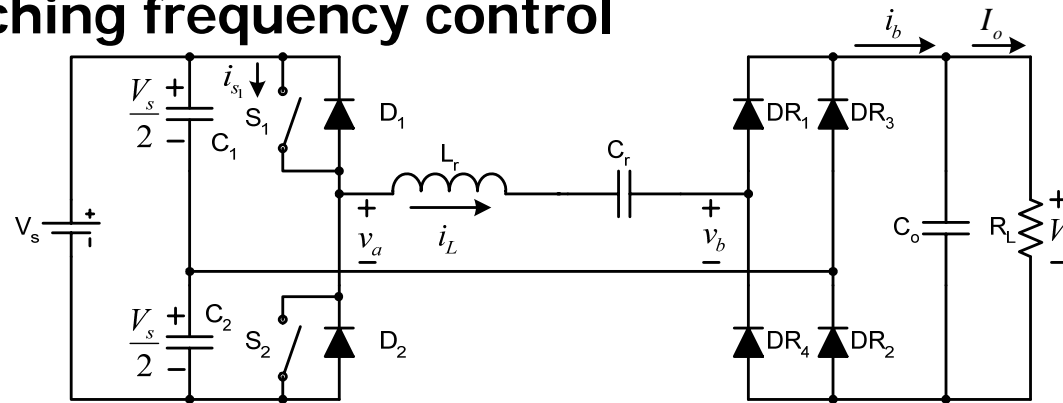- ◆ There is a LC resonant circuit, and the current is able to resonance to zero
- ◆ Switching frequency control



ZCS resonant switch

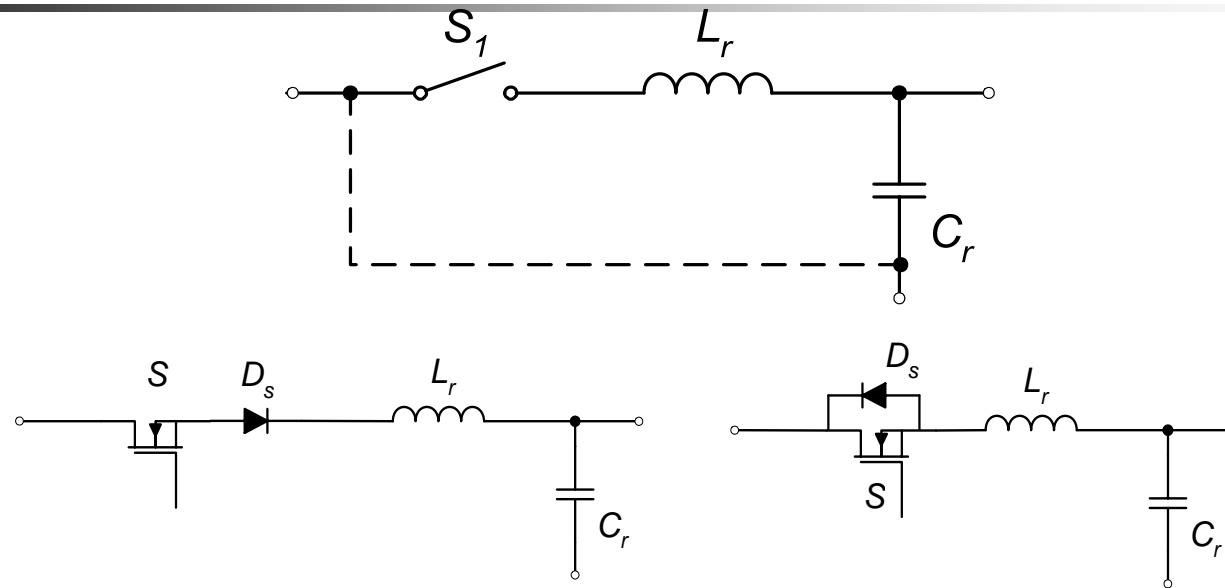


(a) 半波模式

(b) 全波模式


Half wave: Resonant inductor current is one directional

Full wave: Resonant inductor current is bi-directional

ZCS quasi-resonant Buck converter

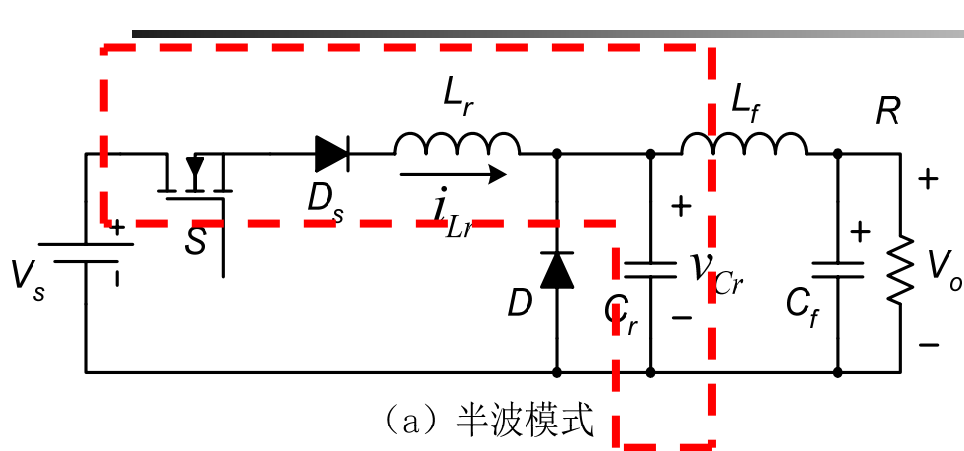

Half wave

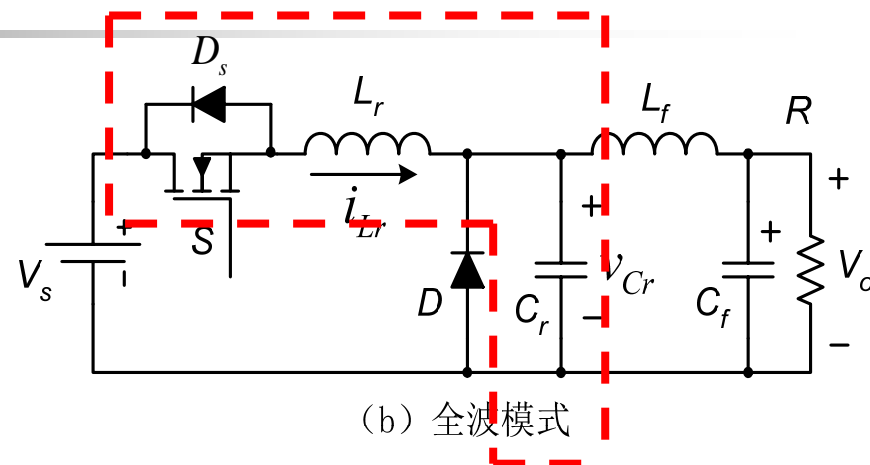


Full wave

Assumption:

- All switches and diodes are ideal
- L and C are ideal
- L_f is larger enough and its current to be seen as current source

Stage 1: inductor charging (t_0, t_1)

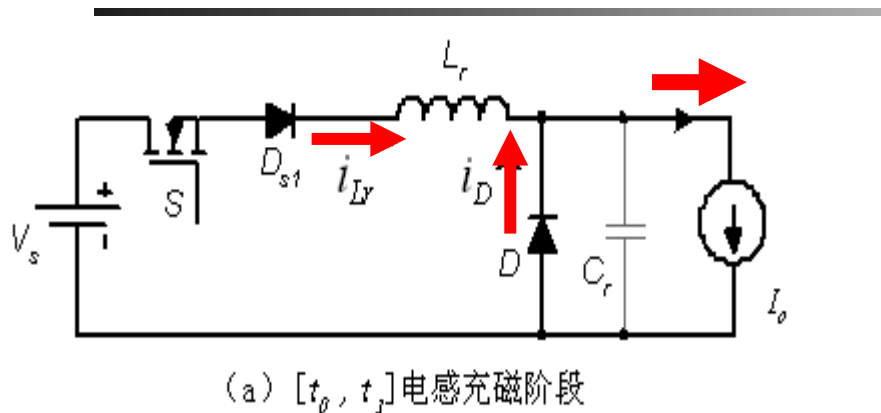

Current in diode is transfer to the switch

$$i_{Lr}(t_0) = 0$$


$$i_{Lr}(t) = \frac{1}{L_r} \int_0^t V_s dt = \frac{V_s}{L_r} t$$

Duration:


$$T_1 = t_1 - t_0 = \frac{L_r I_o}{V_s}$$

Stage 1 ends when i_D reduced to zero

2018/9/3

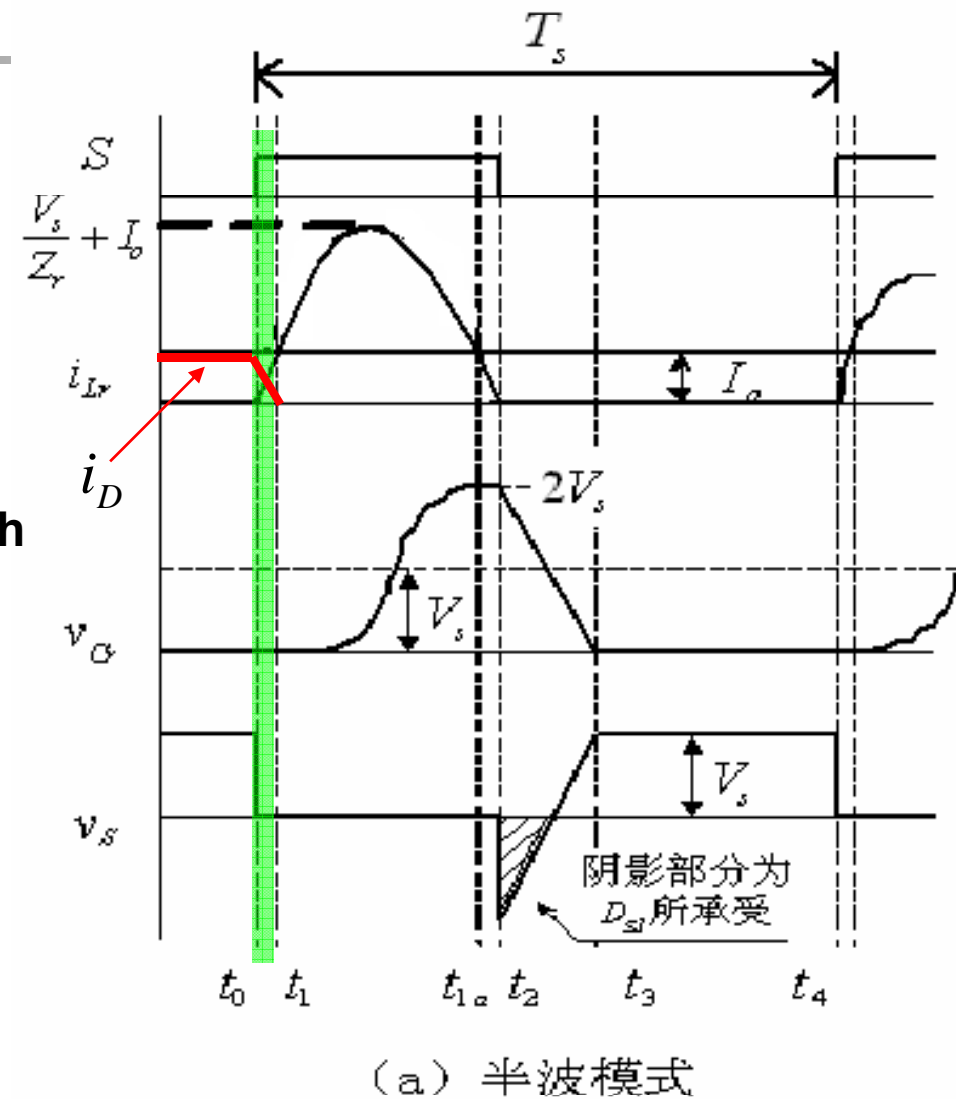

Stage 2: resonant stage (t1,t2)

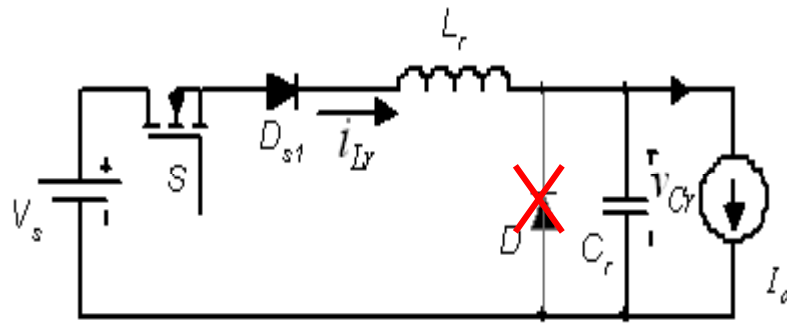

(b) $[t_1, t_2]$ 谐振阶段


L_r and C_r is in resonance

$$\begin{cases} C_r \frac{dv_{Cr}}{dt} = i_{Lr} - I_o & \text{KCL law} \\ L_r \frac{di_{Lr}}{dt} = V_s - v_{Cr} & \text{KVL law} \end{cases}$$

$$i_{Lr}(t) = I_o + \frac{V_s}{Z_r} \sin \omega_r (t - t_1)$$

$$v_{Cr}(t) = V_s [1 - \cos \omega_r (t - t_1)]$$
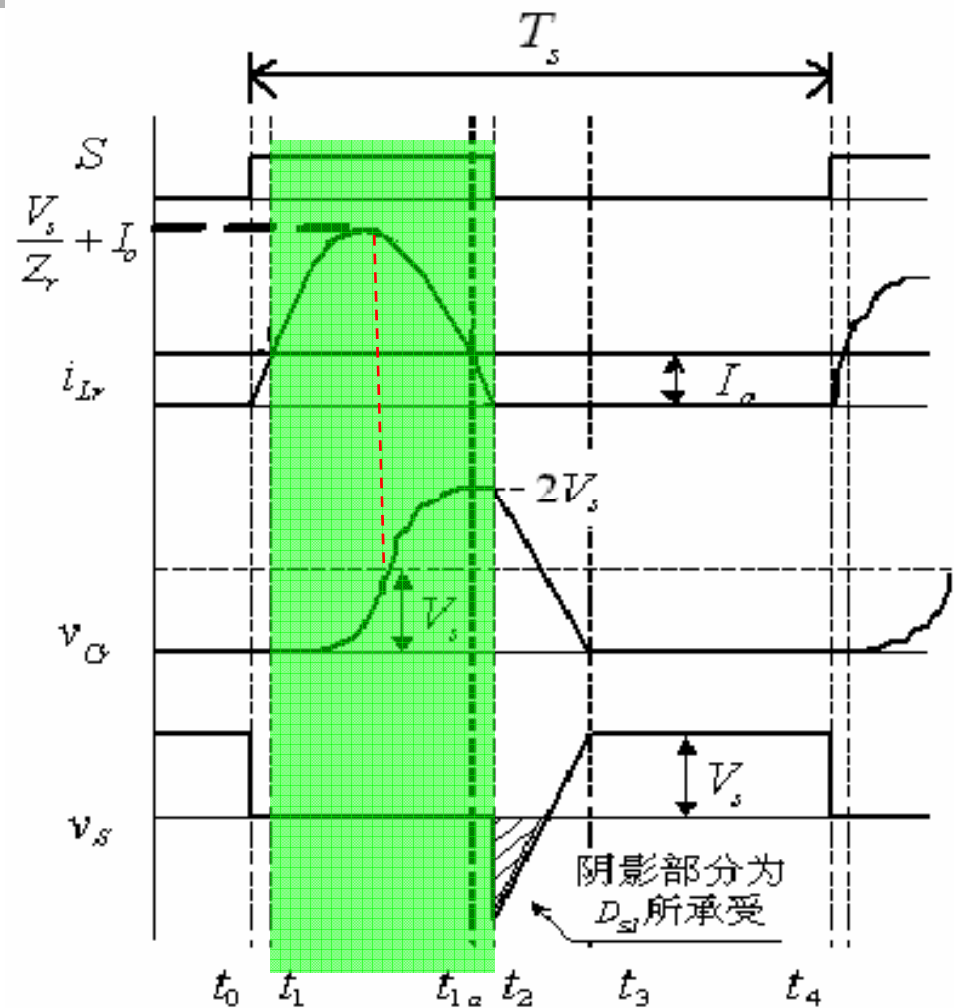
$$\omega_r = 2\pi f_r = \frac{1}{\sqrt{L_r C_r}} \quad Z_r = \sqrt{\frac{L_r}{C_r}}$$



(a) 半波模式

Stage 2: resonant stage (cont'd)

$$\omega_r(t - t_1) = \frac{\pi}{2}$$

Resonant inductor peak current $i_{Lr\max} = i_{Lr}[\omega_r(t - t_1) = \frac{\pi}{2}] = \frac{V_s}{Z_r} + I_o$

Resonant cap voltage $v_{Cr}[\omega_r(t - t_1) = \frac{\pi}{2}] = V_s$

$$\omega_r(t - t_1) = \pi$$

Resonant cap peak voltage: $v_{Cr\max} = v_{Cr}[\omega_r(t - t_1) = \pi] = 2V_s$

Resonant inductor current $i_{Lr}[\omega_r(t - t_1) = \pi] = I_o$

At time t_2 , switch naturally turns off when switch current resonant to 0  ZCS is realized

2018/9/1 Stage 2 ends when S is turned off with ZCS

Stage 3: capacitor discharge (t2,t3)




(c) $[t_2, t_3]$ 电容放电阶段

Cap. voltage linearly is decreasing

$$v_{Cr}(t) = \frac{1}{C_r} \int_{t_2}^t (-I_o) dt + V_{Cr}(t_2) = V_{Cr}(t_2) - \frac{I_o}{C_r} (t - t_2)$$

Duration:
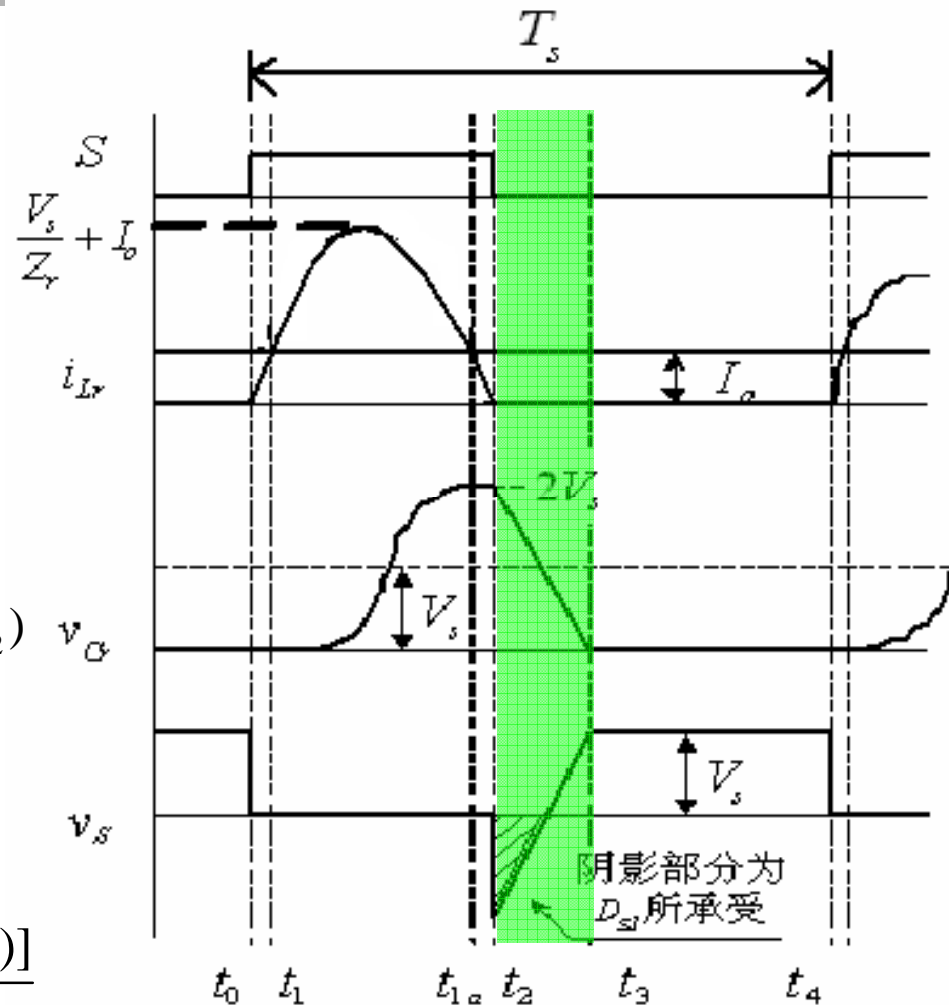
$$T_3 = t_3 - t_2 = \frac{C_r V_{Cr}(t_2)}{I_o} = \frac{C_r V_s [1 - \cos \omega_r (t_2 - t_1)]}{I_o}$$




(a) 半波模式

Stage 3 ends when D starts to conduct

2016/9/3


Stage 4: freewheel (t3,t4)

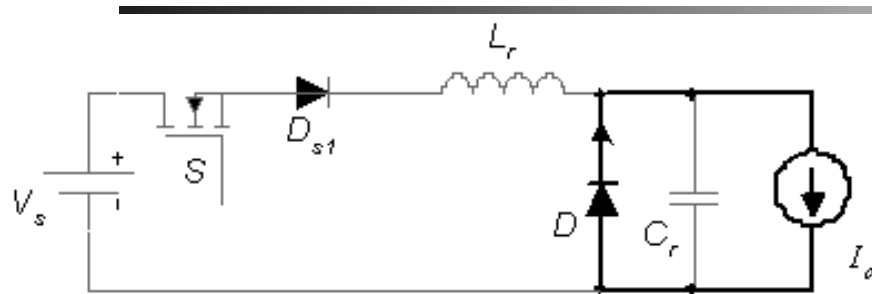

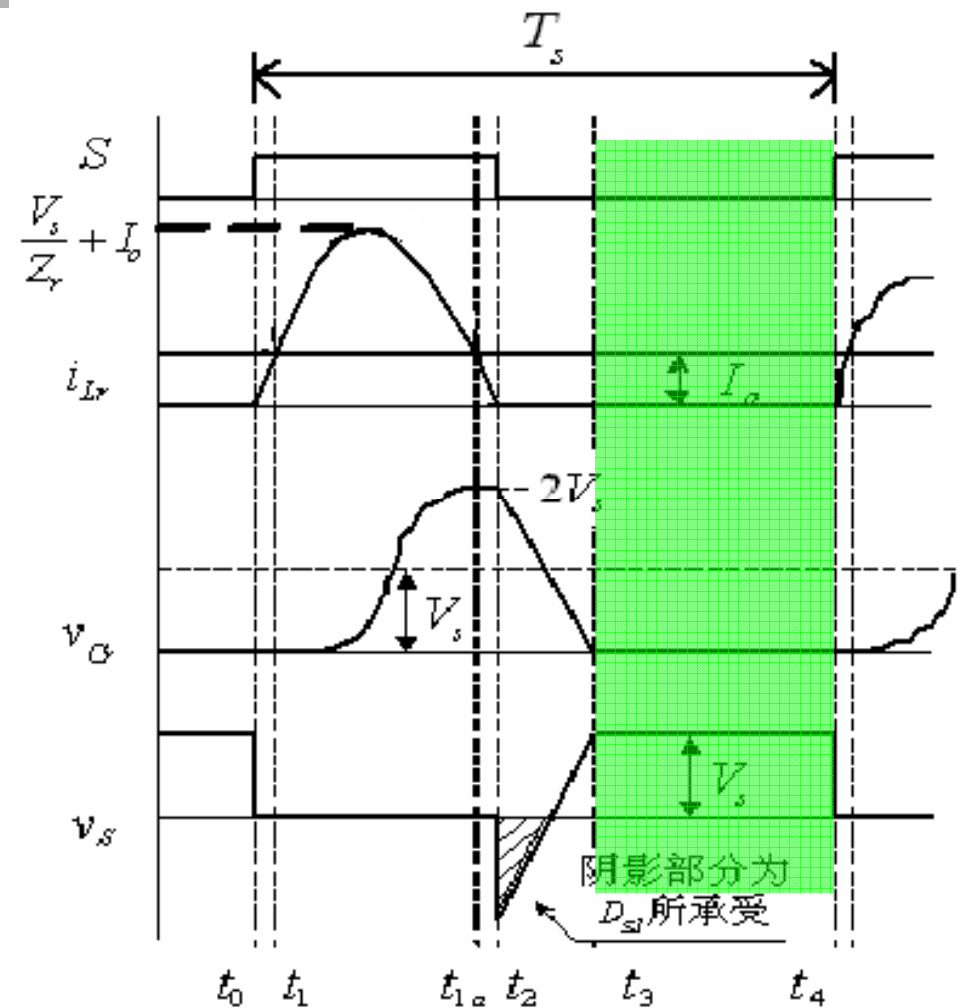(d) $[t_3, t_4]$ 续流阶段


$$T_4 = t_4 - t_3 = T_s - (T_1 + T_2 + T_3)$$

Duration is decided by switching frequency




(a) 半波模式


Summary of the half-wave operation

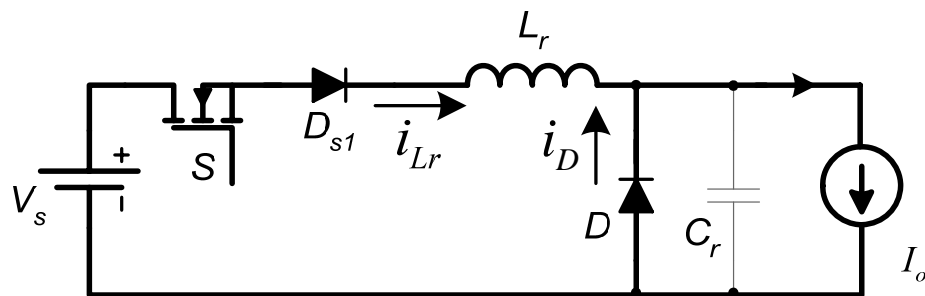


(a) Inductor charging

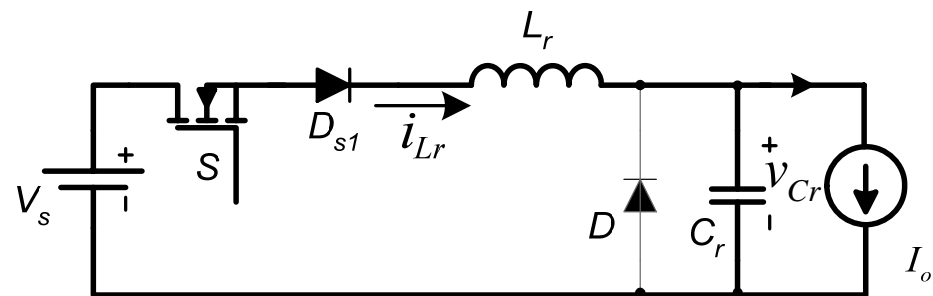

(b) [resonance

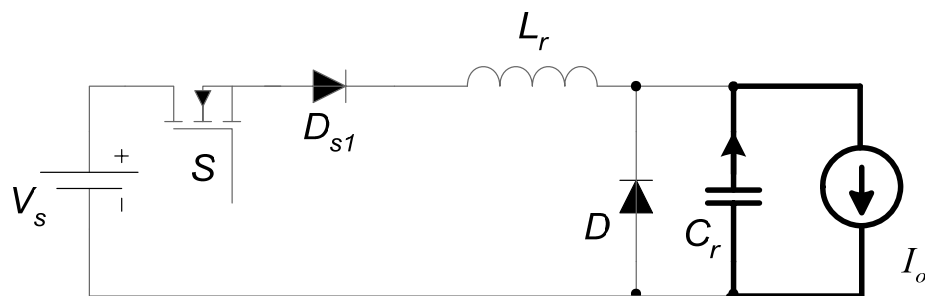


(c) Cap discharging

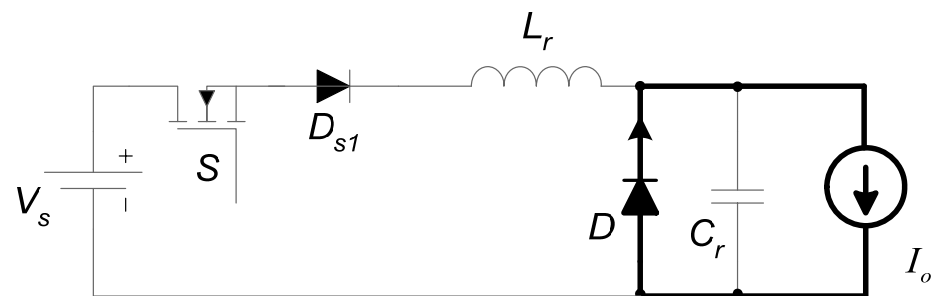


(d) Flywheel :

Full wave mode: Stage 1: inductor charge

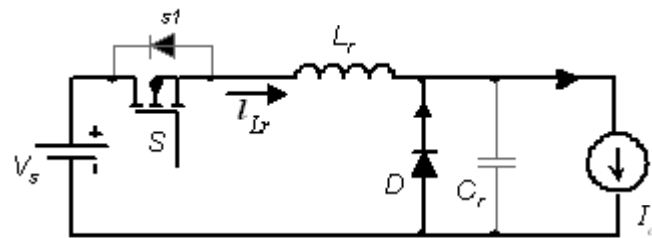


(a) $[t_0, t_1]$ 电感充磁阶段

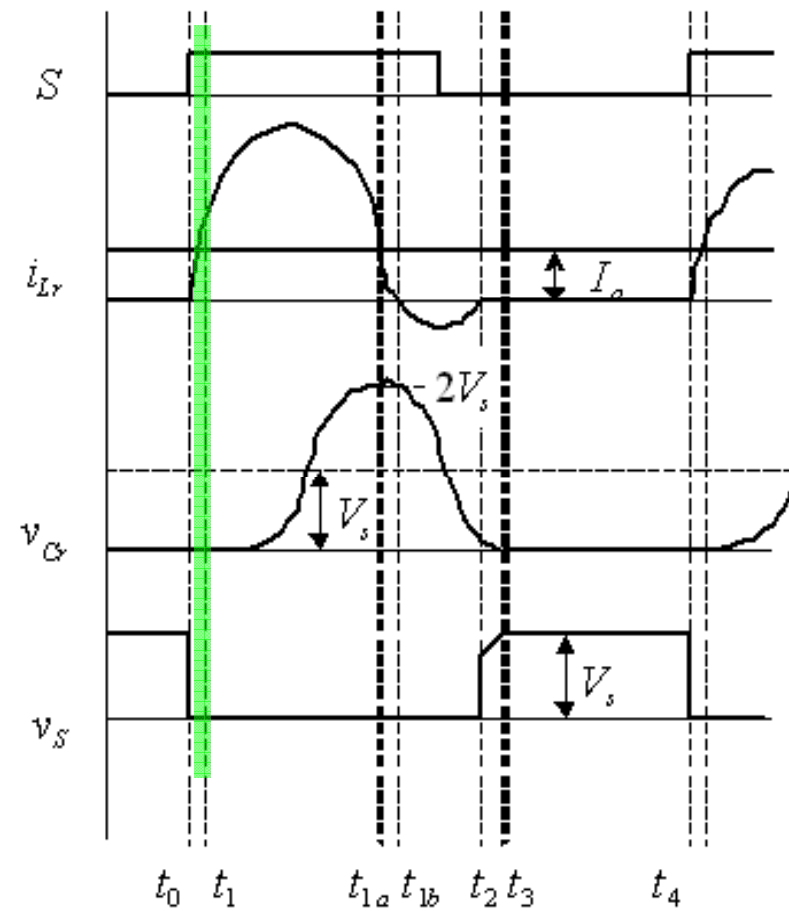


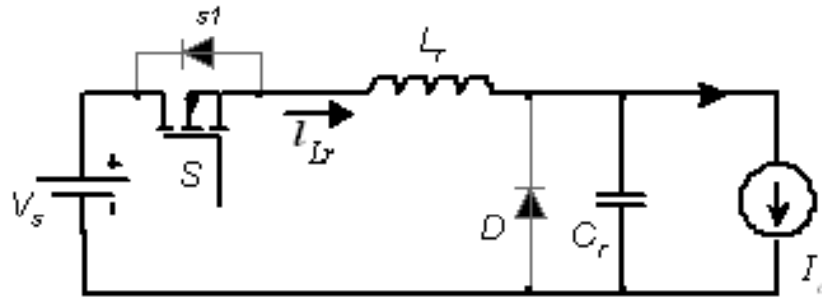(b) 全波模式

Full wave mode: Stage 2(section 1):resonance




(b) $[t_1, t_2]$ 谐振阶段之一

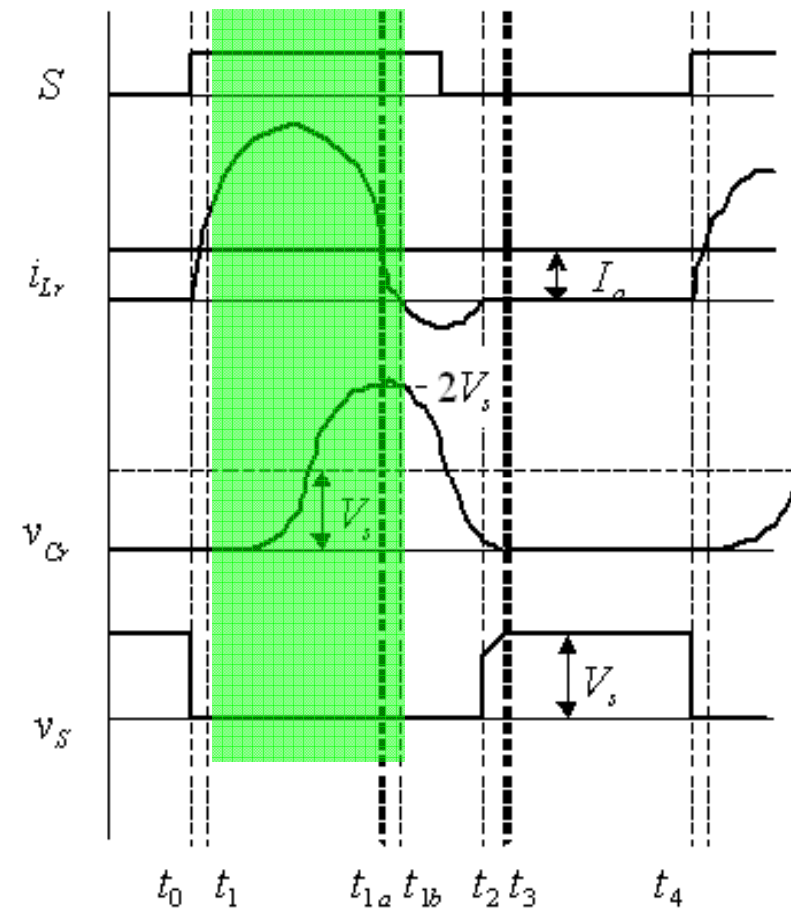

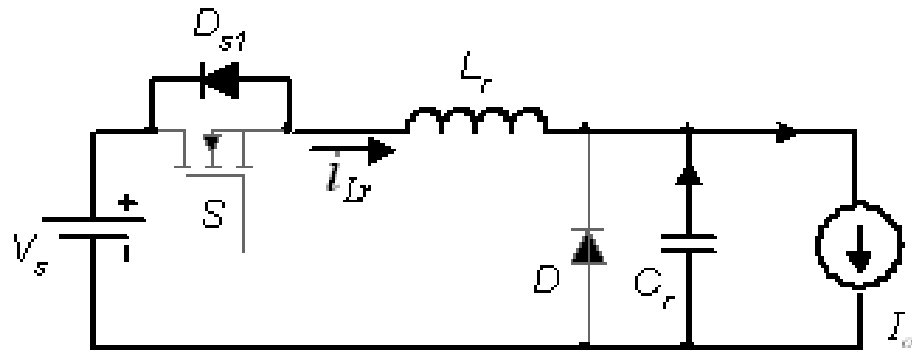(b) 全波模式


Full wave mode: Stage 2(section 2):resonance



(b') $[t_{1b}, t_2]$ 谐振阶段之二



At time t_{1b} i_{Lr} is reversed and resonant through negative half cycle

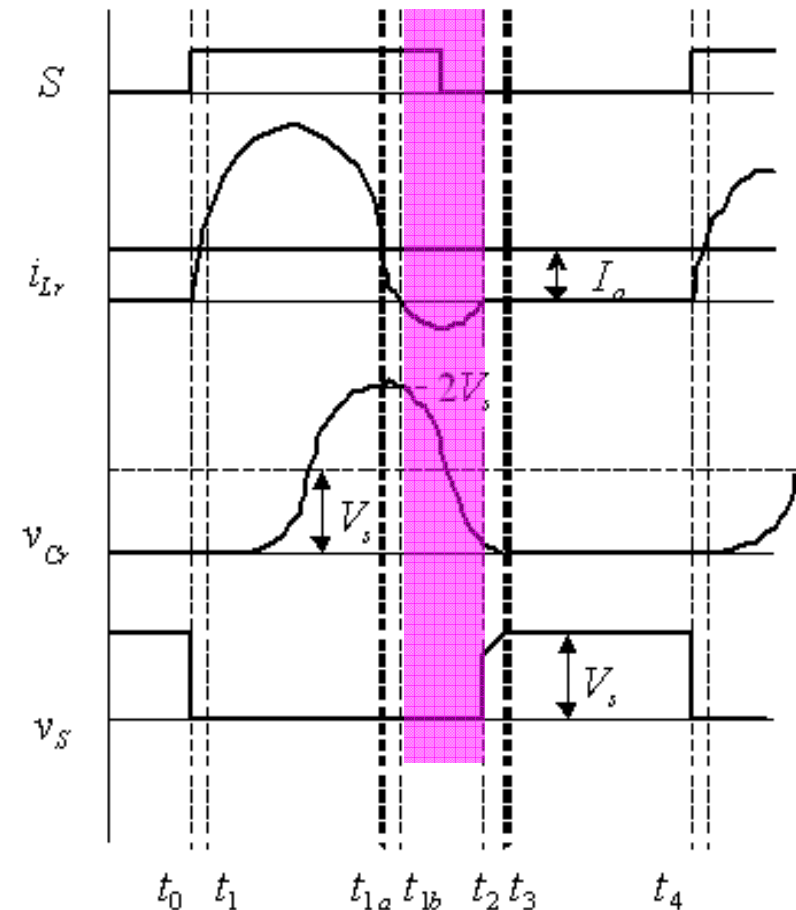During $[t_{1b}, t_2]$, switch S current is zero
It can be turned off with ZCS.



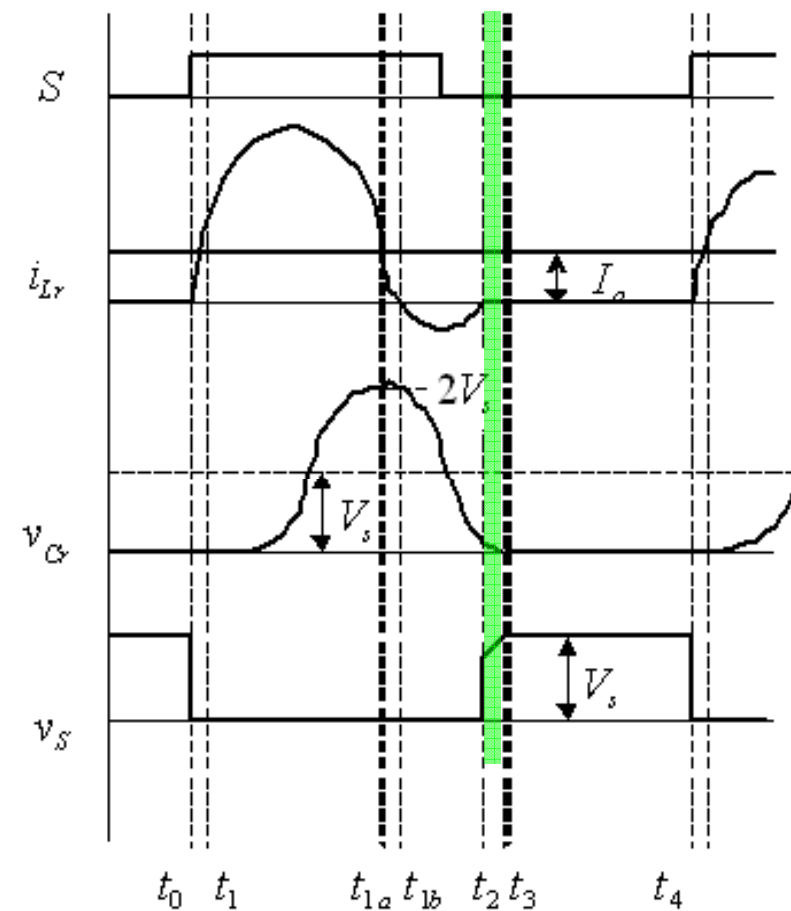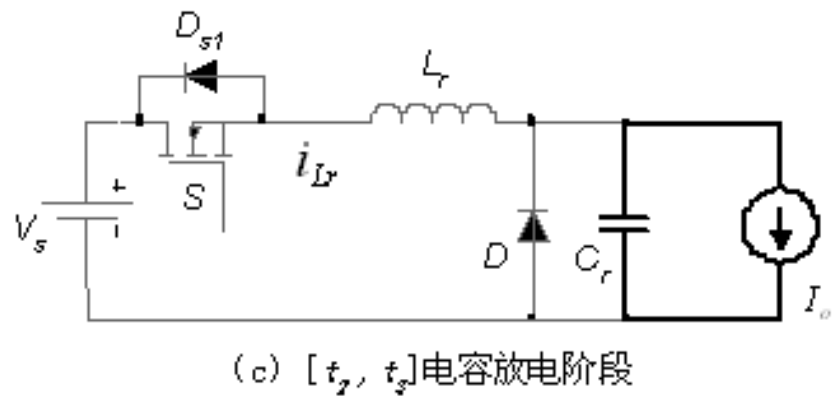
(b) 全波模式

Full wave mode: Stage 3: capacitor discharge




(b) 全波模式

Full wave mode: Stage 4: freewheel

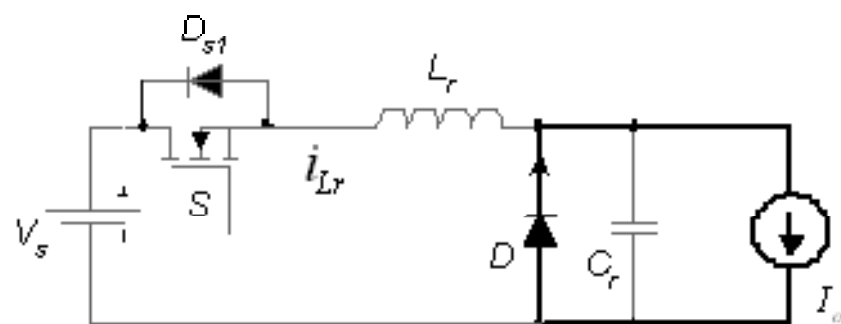


(d) $[t_3, t_4]$ 续流阶段

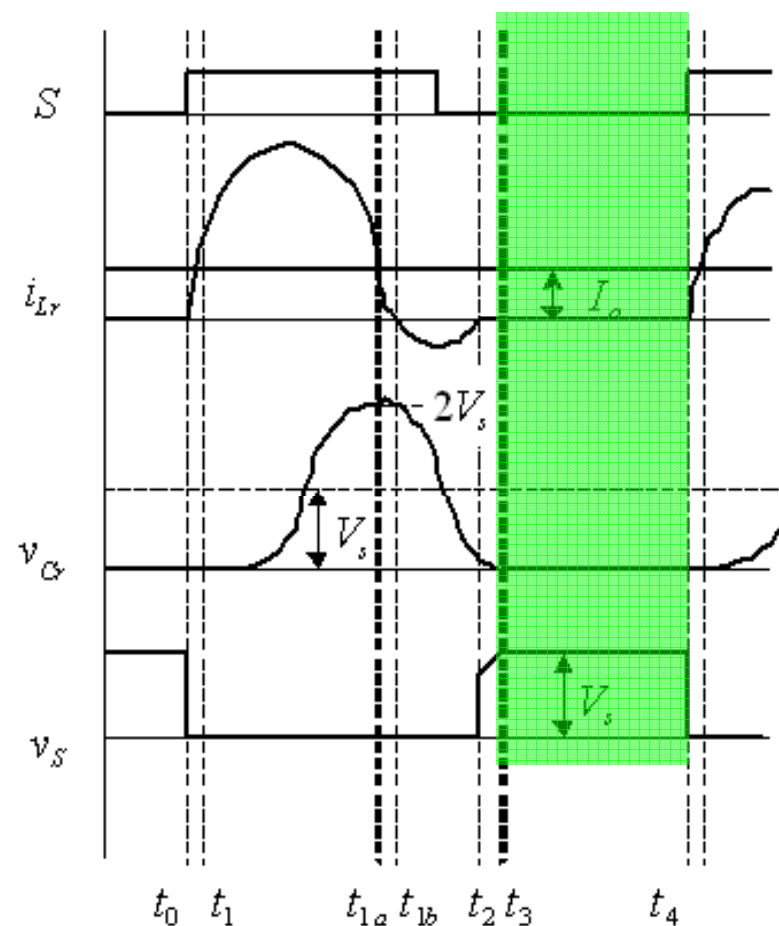


(b) 全波模式


Full-wave operation stages

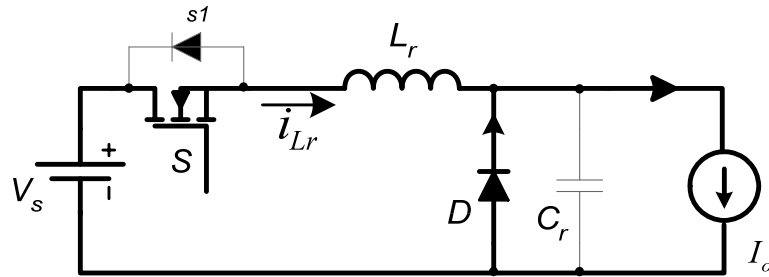


(a) Inductor charging

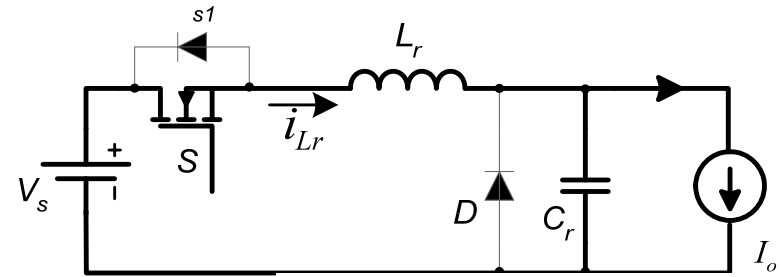


(b) Resonance duration 1

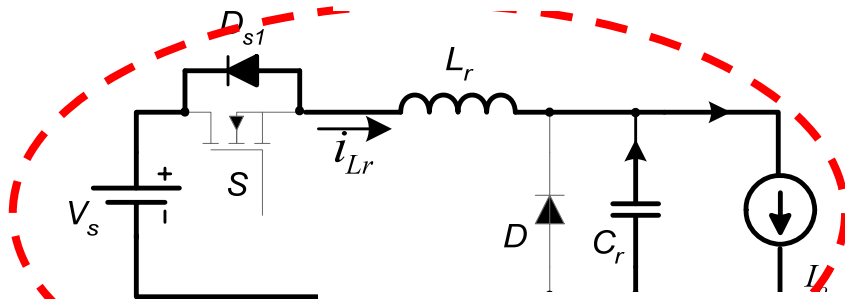

(b') Resonance duration 2

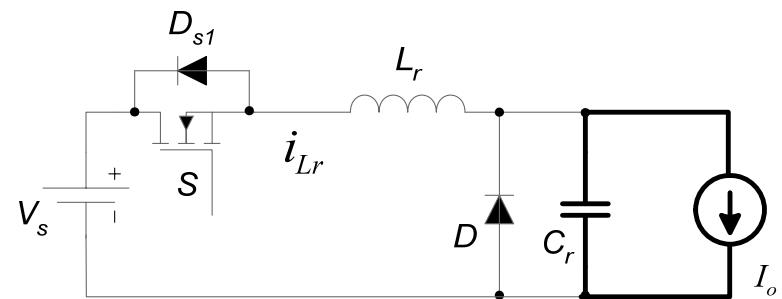

(c) Cap discharging

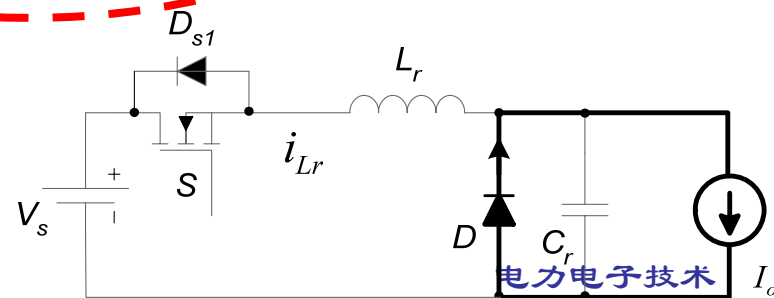


Flywheel

ZCS condition


In stage 2, Inductor current must resonance to zero to realize ZCS.

$$i_{Lr}(t) = I_o + \frac{V_s}{Z_r} \sin \omega_r(t - t_1) \quad \rightarrow \quad \frac{V_s}{Z_r} > I_{o\max}$$

$I_{o\max}$ Maximum load current

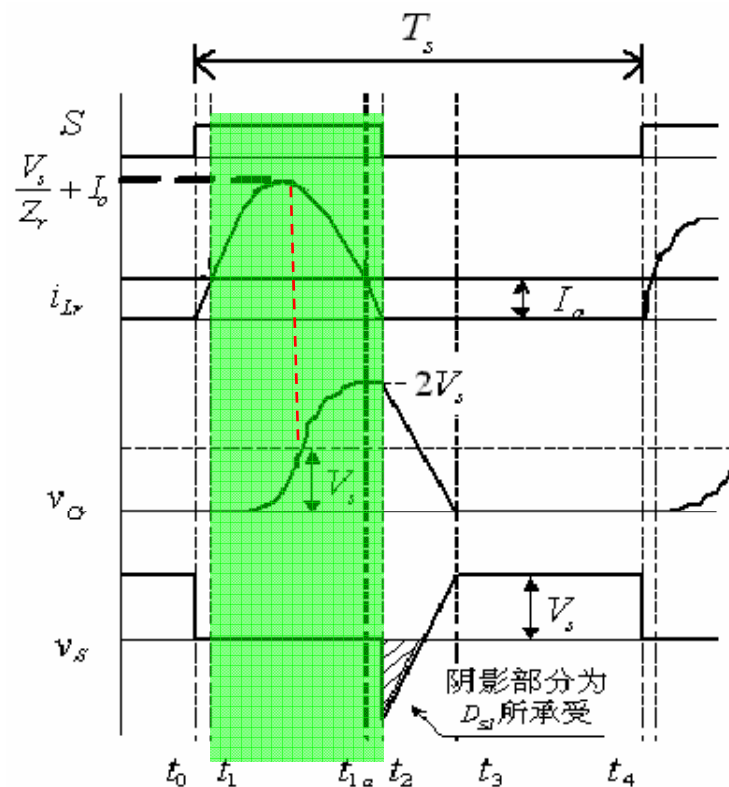

(a) 半波模式

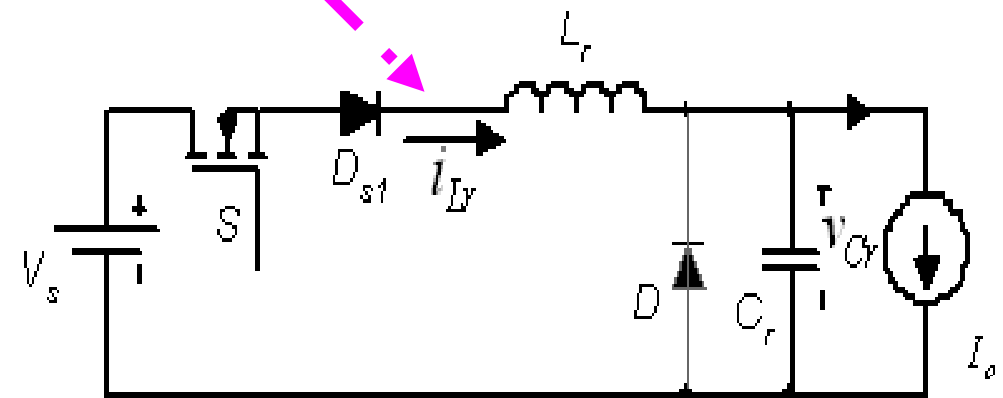

(b) $[t_1, t_2]$ 谐振阶段

DC conversion ratio


Energy drawn from the DC source in every switching cycle:

$$W_s = V_s \int_0^T i_{Lr}(t) dt$$

Energy output to the load

$$W_o = V_o I_o T_s = \frac{V_o I_o}{f_s}$$
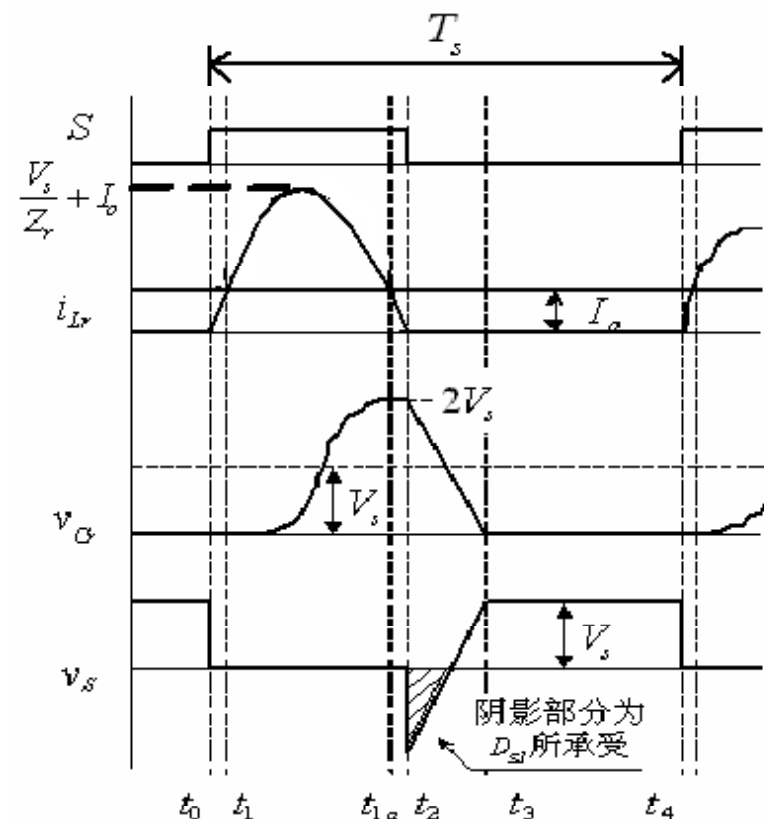
$$\begin{aligned} \int_0^T i_{Lr}(t) dt &= \int_0^{t_1} \frac{V_s t}{L_r} dt + \int_{t_1}^{t_2} \left[I_o + \frac{V_s}{Z_o} \sin \omega_r (t - t_1) \right] dt \\ &= \frac{I_o}{2} t_1 + I_o (t_2 - t_1) + V_s C_r [1 - \cos(\omega_r (t_2 - t_1))] \end{aligned}$$



(a) 半波模式

DC conversion ratio

According to energy conservation law

$$W_s = W_o$$



$$V_o = V_s f_s \left\{ \frac{t_1}{2} + (t_2 - t_1) + \frac{C_r V_s}{I_o} [1 - \cos \omega_r (t_2 - t_1)] \right\}$$


$$V_o = V_s f_s \left[\frac{t_1}{2} + (t_2 - t_1) + (t_3 - t_2) \right]$$

DC conversion ratio $M = \frac{V_o}{V_s} = \frac{f_s}{f_r} f(I_{on})$ where $I_{on} = \frac{Z_r I_o}{V_s}$

Half-wave: $f(I_{on}) = \frac{1}{2\pi} \left[\frac{1}{2} I_{on} + \pi + \sin^{-1}(I_{on}) + \frac{1}{I_{on}} (1 + \text{sign} \sqrt{1 - I_{on}^2}) \right]$

Full-wave: $f(I_{on}) = \frac{1}{2\pi} \left[\frac{1}{2} I_{on} + 2\pi - \sin^{-1}(I_{on}) + \frac{1}{I_{on}} (1 - \text{sign} \sqrt{1 - I_{on}^2}) \right]$

Conversion ratio curves

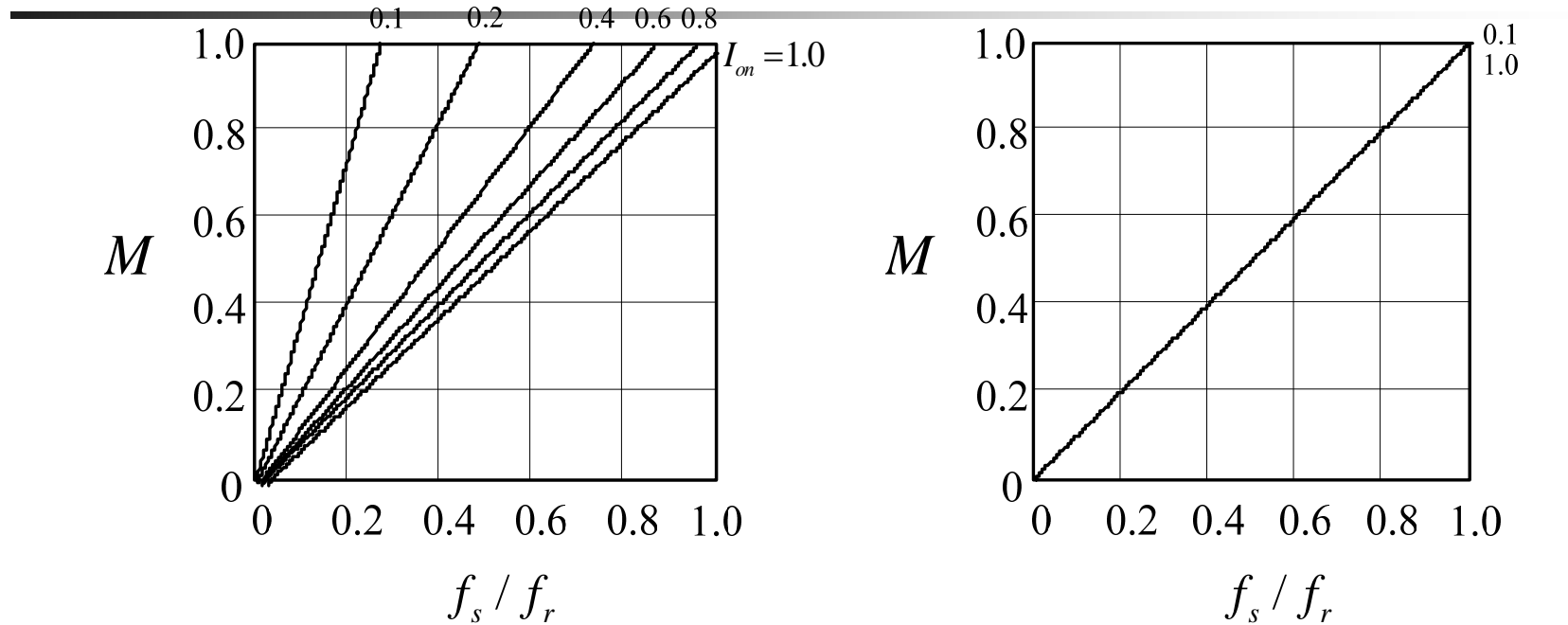

Half wave

Full wave

Half:
$$f(I_{on}) = \frac{1}{2\pi} \left[\frac{1}{2} I_{on} + \pi + \sin^{-1}(I_{on}) + \frac{1}{I_{on}} (1 + \text{sign} \sqrt{1 - I_{on}^2}) \right]$$


Full:
$$f(I_{on}) = \frac{1}{2\pi} \left[\frac{1}{2} I_{on} + 2\pi - \sin^{-1}(I_{on}) + \frac{1}{I_{on}} (1 - \text{sign} \sqrt{1 - I_{on}^2}) \right]$$

Summary of the ZCS QRC converter

-
- Current Resonant switch :full wave and half wave
 - ZCS is realized for the switch
 - ZCS condition is derived. The lighter the load, the better the ZCS condition
 - DC conversion ratio is the function of switching frequency
 - DC conversion ratio: linear for full wave, and nonlinear for half wave
 - The concept can be extended to all DC/DC converters

Zero Voltage quasi resonant converter

ZVS resonant switch

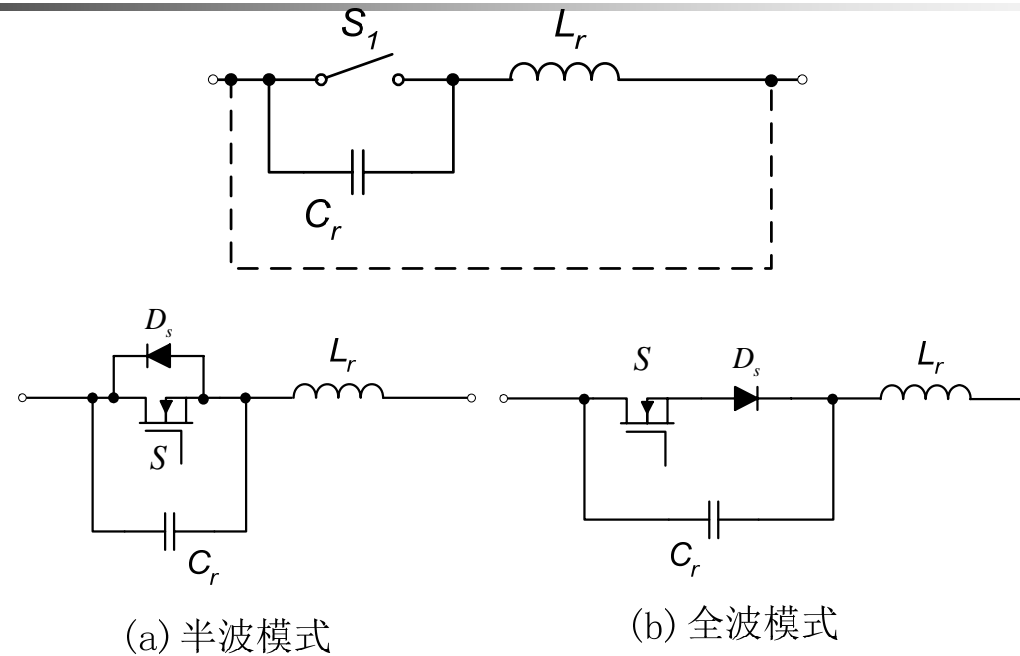


Half wave: Resonant capacitor voltage is one directional


Full wave: Resonant capacitor voltage is bi-directional

Extra diode is inserted in full wave. Conduction loss increased.

Quasi ZVS Boost converter

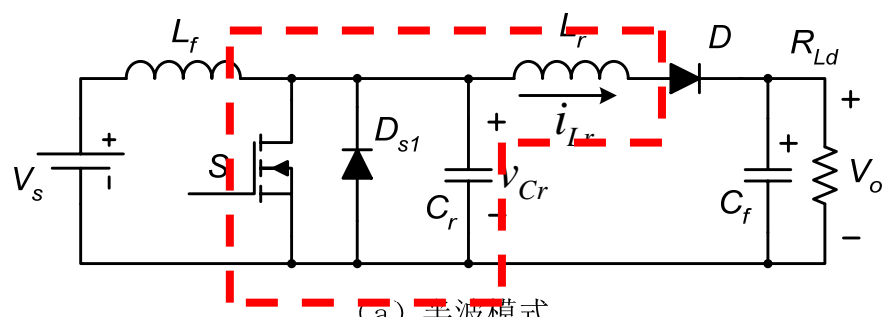

Half wave

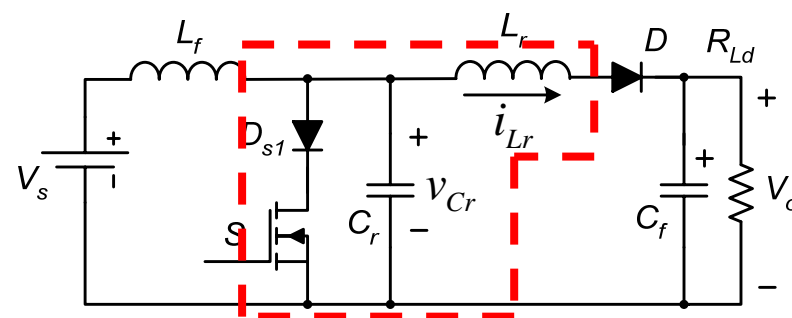


Full wave

Assumption:

- All switches and diodes are ideal
- L and C are ideal
- L_f is larger enough and its current to be seen as the current source
- C_f is larger enough and can be seen as voltage sink

Stage 1: Capacitor Charge (t_0 - t_1)

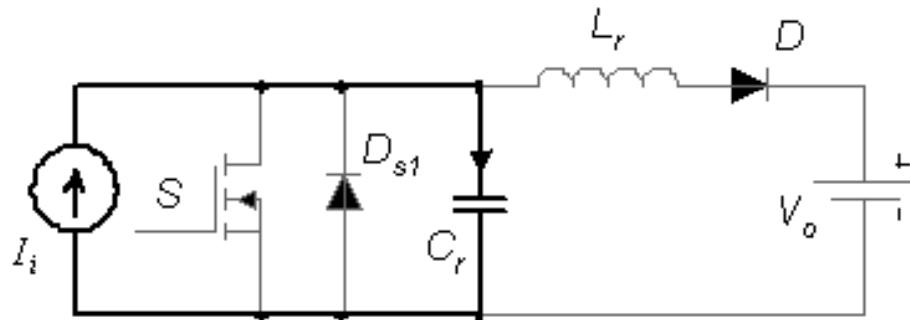


(a) 阶段1(t_0, t_1)电容充电阶段

Voltage on resonant capacitor


$$v_{Cr}(t) = \frac{1}{C_r} \int_0^t I_i dt = \frac{I_i}{C_r} t$$

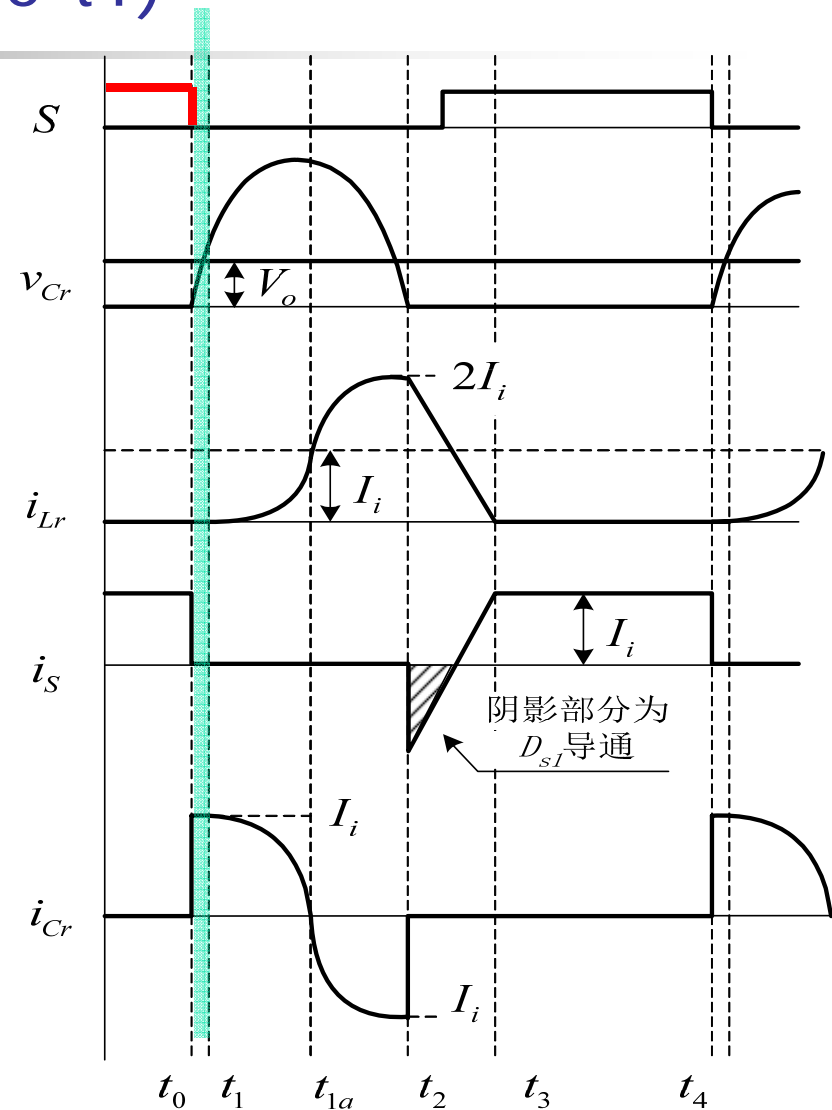Duration: $T_1 = t_1 - t_0 = \frac{C_r V_o}{I_i}$



Stage 1 ends when resonant Cap. Voltage equal to V_o

Stage 2: Resonance (t1-t2)

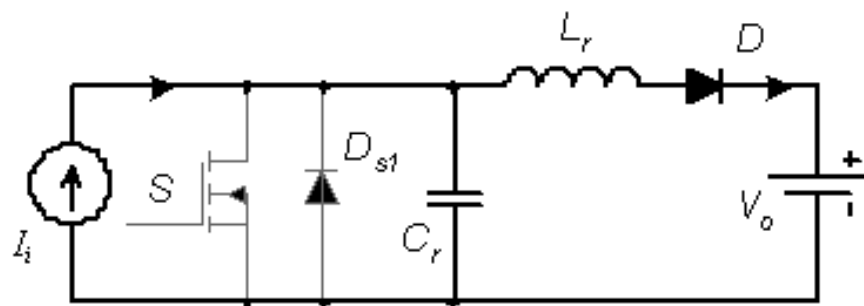


(b) 阶段2(t_1, t_2)谐振阶段

$$\begin{cases} L_r \frac{di_{Lr}}{dt} = v_{Cr} - V_o & \text{KVL law} \\ C_r \frac{dv_{Cr}}{dt} = I_i - i_{Lr} & \text{KCL law} \end{cases}$$

$$i_{Lr}(t) = I_i [1 - \cos \omega_r (t - t_1)]$$

$$v_{Cr}(t) = V_o + I_i Z_r \sin \omega_r (t - t_1)$$

$$\omega_r = 2\pi f_r = \frac{1}{\sqrt{L_r C_r}} \quad Z_r = \sqrt{\frac{L_r}{C_r}}$$

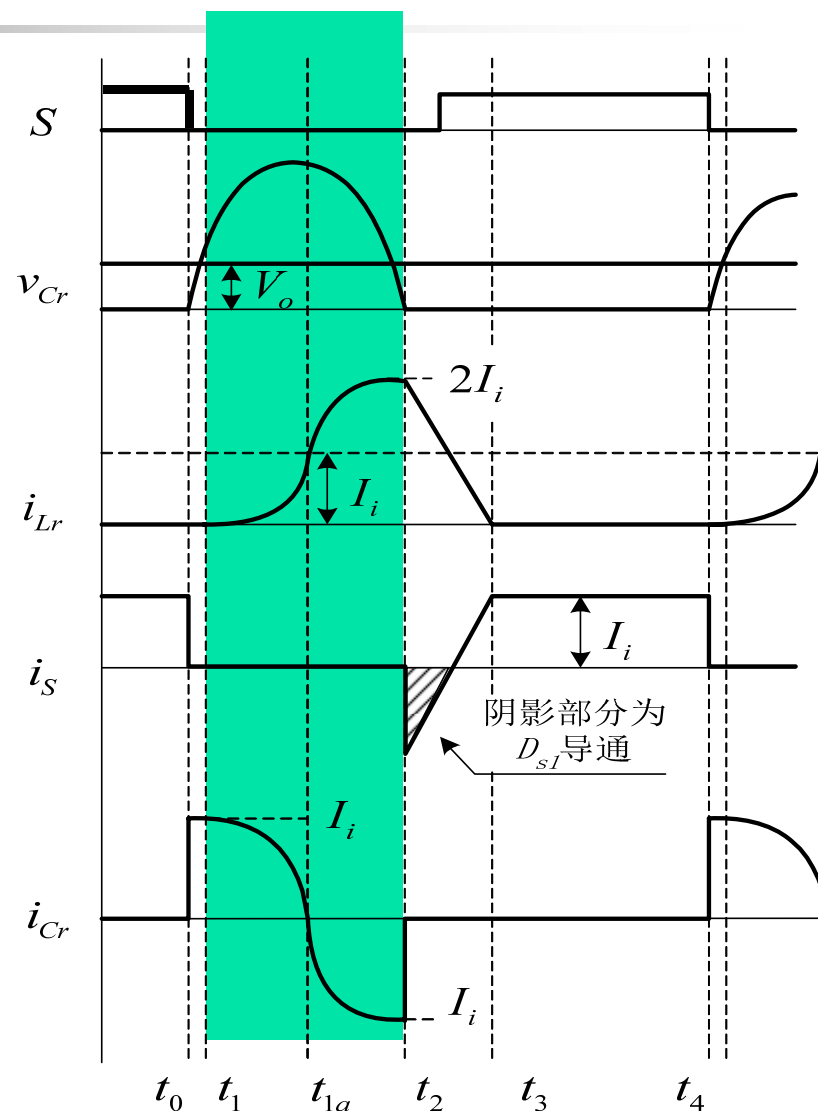

Stage 2: Resonance (cont'd)

$$\omega_r(t_{1a} - t_1) = \frac{\pi}{2}$$

Cap peak voltage $V_{Cr\max} = V_o + I_i Z_r$

$$i_{Lr}(t_{1a}) = I_i$$

$$\omega_r(t - t_1) = \pi$$

Cap voltage resonant to V_o


Ind. Current resonant to $2I_i$

Duration:

$$T_2 = t_2 - t_1 = \frac{1}{\omega_r} \left[\pi + \sin^{-1} \left(\frac{V_o}{I_i Z_r} \right) \right] = \frac{\theta}{\omega_r}$$


$$\pi < \theta < \frac{3}{2}\pi$$
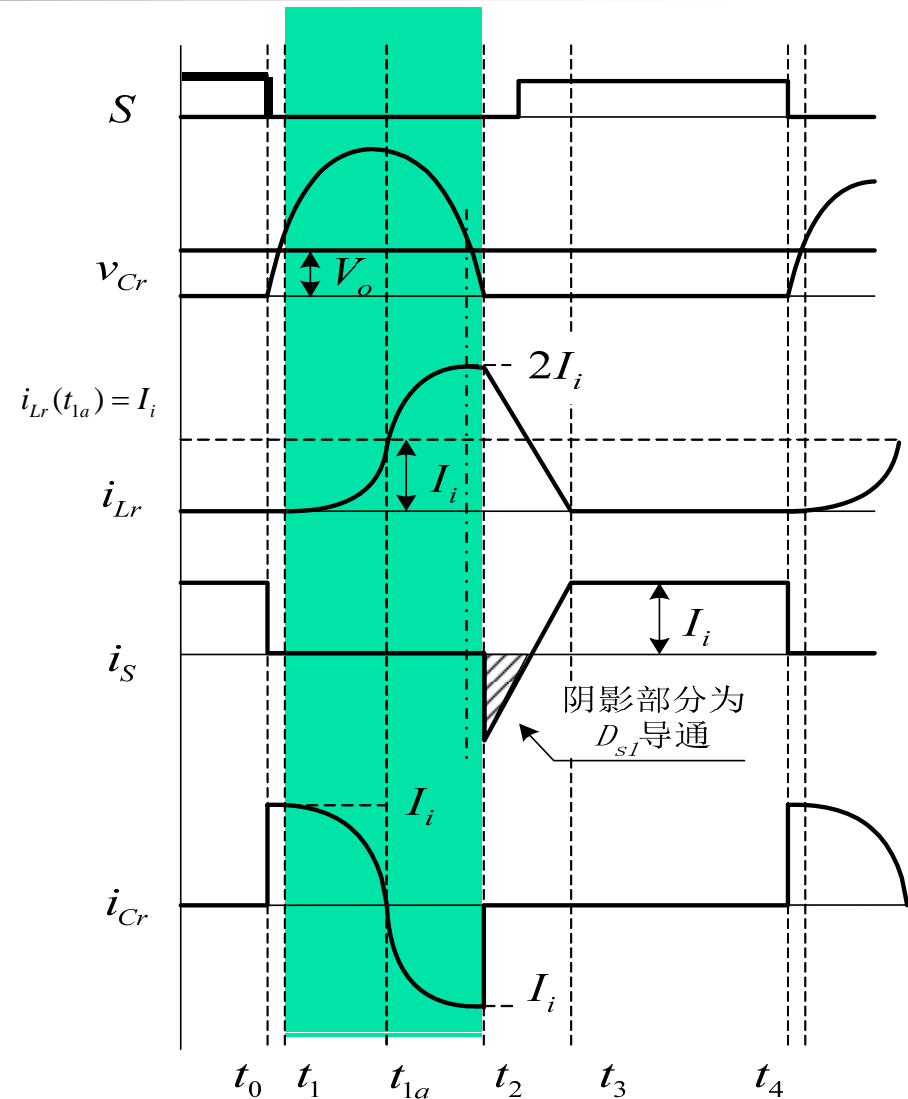
$$I_{Lr2} = i_{Lr}(t_2) = I_i [1 - \cos \omega_r(t_2 - t_1)] = I_i \left[1 + \sqrt{1 - \left(\frac{V_o}{I_i Z_r} \right)^2} \right]$$



Stage 2 ends when cap. voltage resonant to zero

Stage 3: Inductor discharge (t₂-t₃)

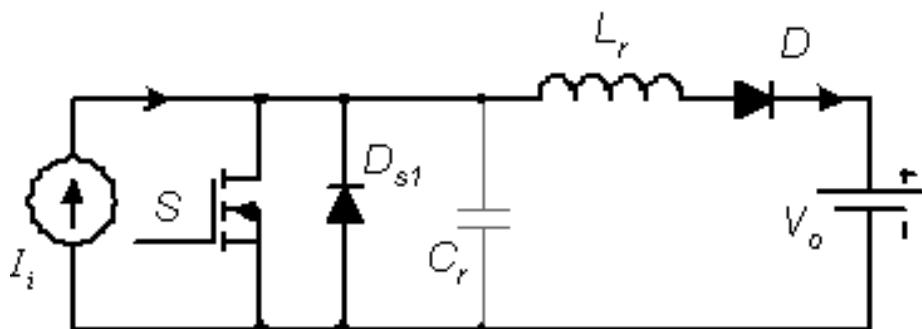


(c) 阶段3(t_2, t_3)电感放电阶段

Inductor current is linearly decreasing


$$i_{Lr}(t) = I_{Lr2} - \int_{t_2}^t \frac{V_o}{L_r} dt = I_{Lr2} - \frac{V_o}{L_r} (t - t_2)$$

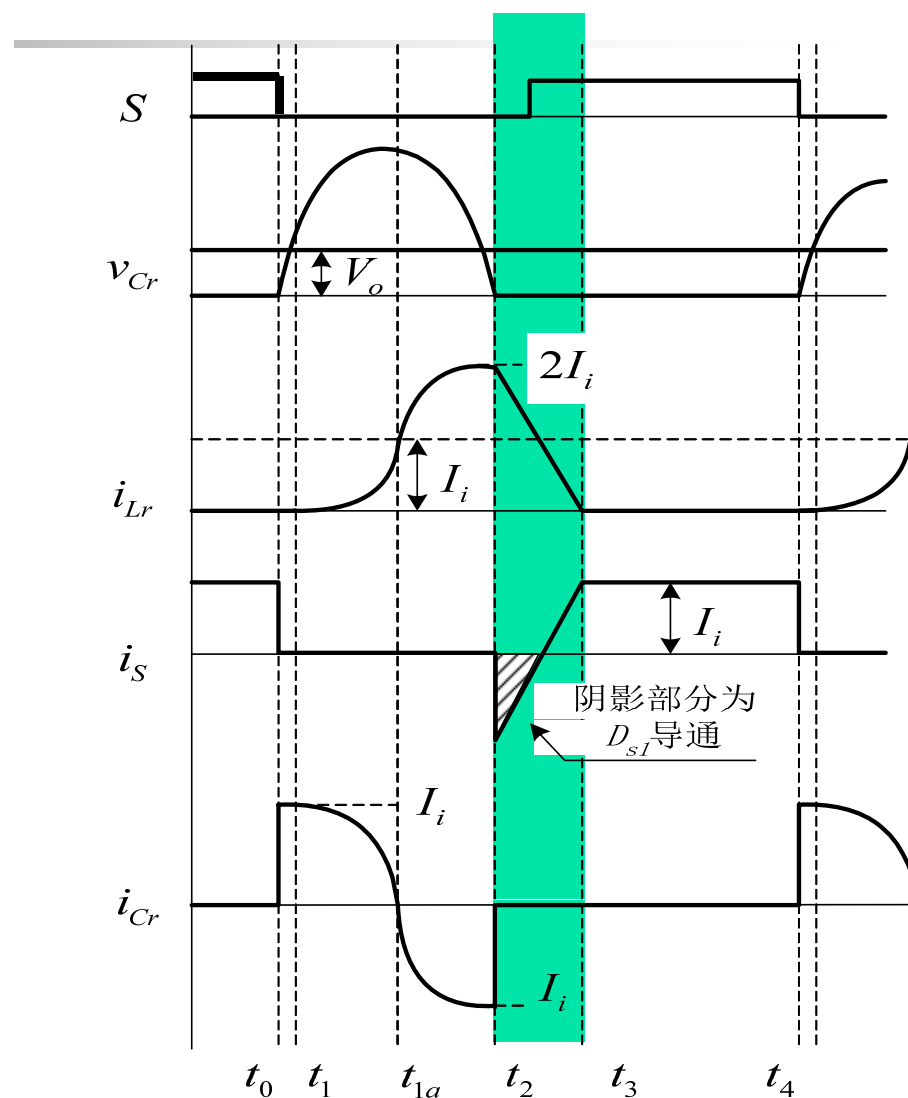Duration: $T_3 = t_3 - t_2 = \frac{L_r I_{Lr}(t_2)}{V_o}$



Switch S may be turned on with ZVS when D_{s1} is conducting


Stage 4: freewheel (t_3 - t_4)

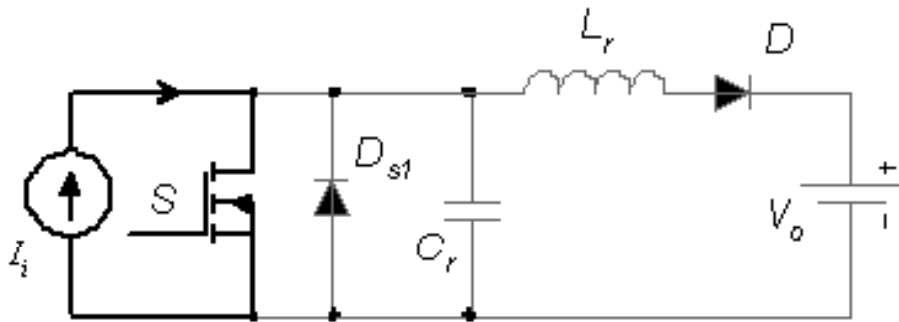


(d) 阶段4(t_3, t_4)续流阶段

Duration decided by switching freq.


$$T_4 = T_s - T_1 - T_2 - T_3$$

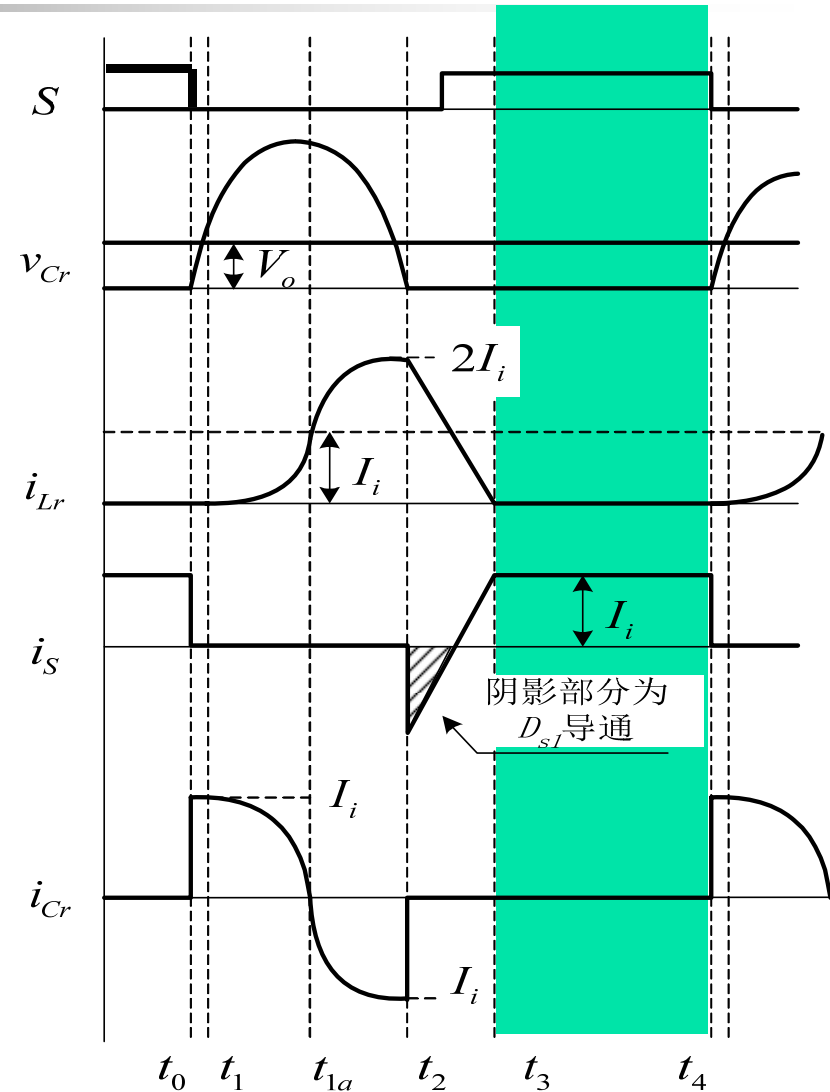


Stages in a cycle

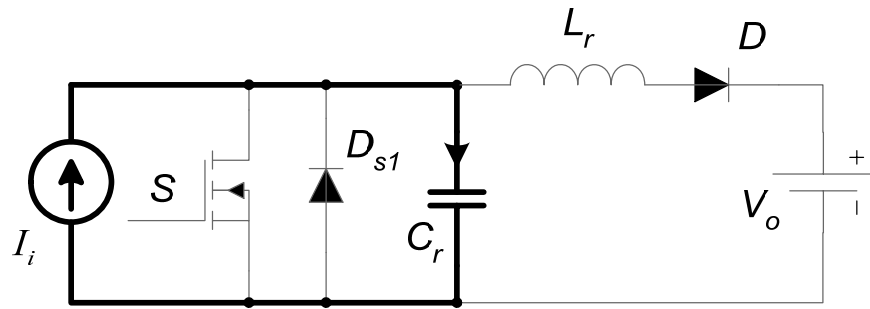


(a) 阶段1(t_0, t_1) 电容充电阶段

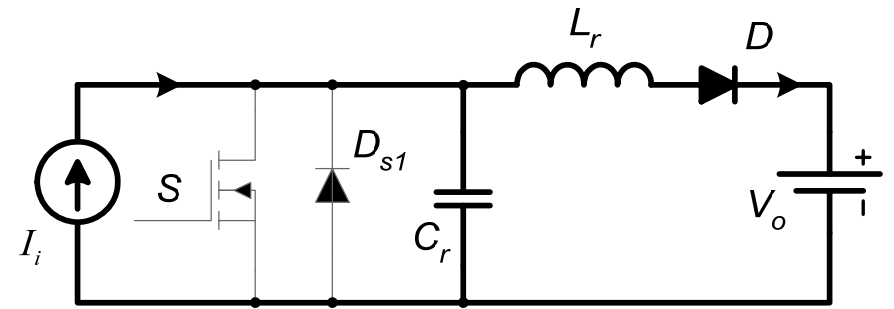

(b) 阶段2(t_1, t_2) 谐振阶段

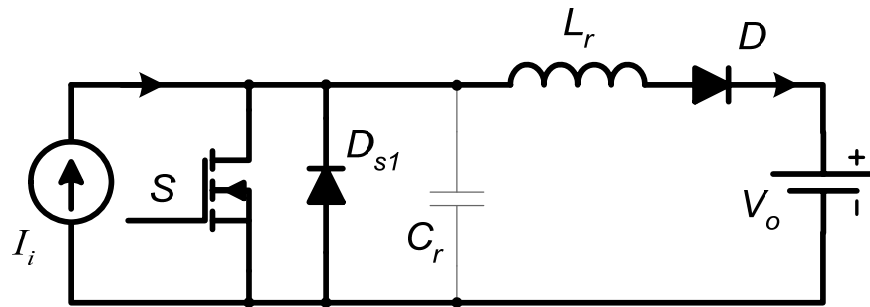

(c) 阶段3(t_2, t_3) 电感放磁阶段

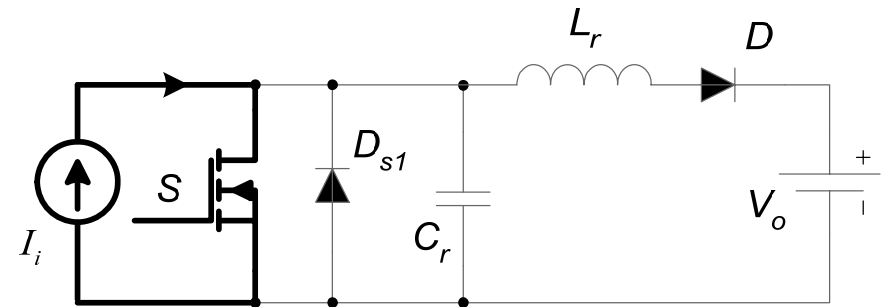

(d) 阶段4(t_3, t_4) 续流阶段

ZVS condition

Resonant cap voltage v_{Cr} must resonance to zero in stage 2


$$v_{Cr}(t) = V_o + I_i Z_r \sin \omega_r (t - t_1)$$

$$I_{i\min} Z_r > V_o \quad \Rightarrow \quad Z_r > \frac{V_o}{I_{i\min}}$$

$I_{i\min}$ Minimum input current

Cap peak voltage $V_{Cr\max} = V_o + I_{i\max} Z_r$

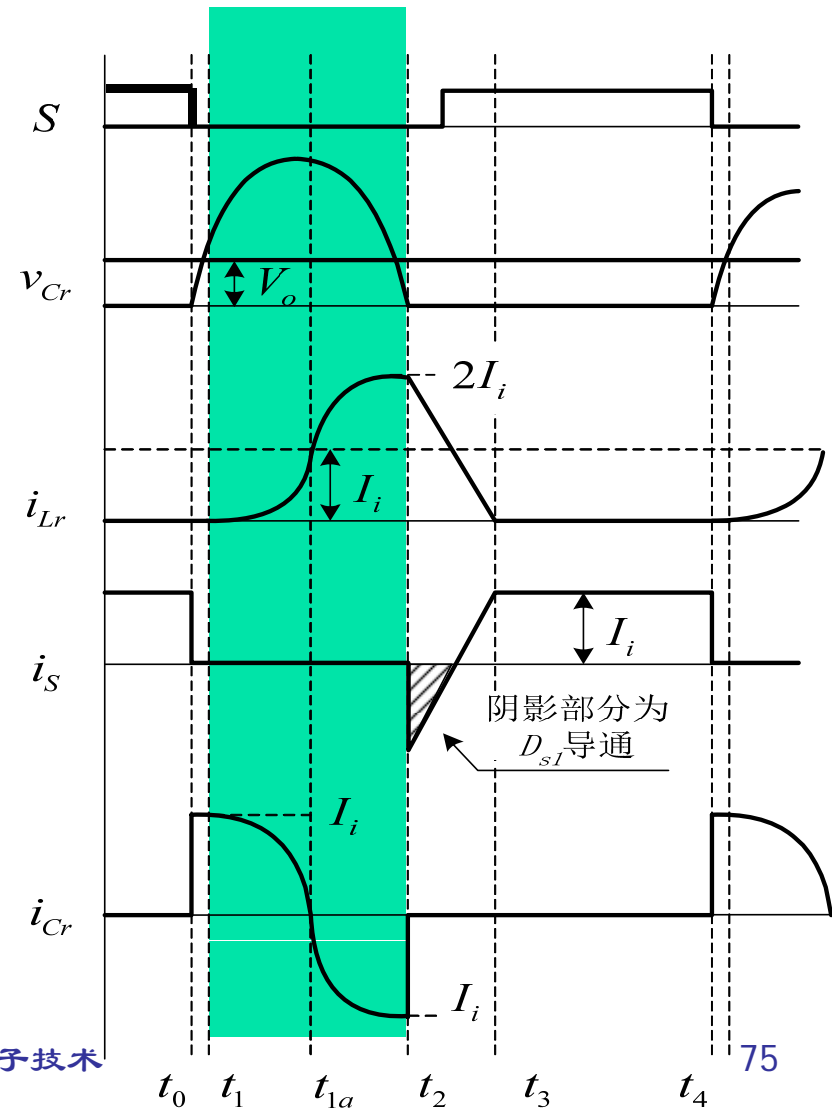Therefore $V_{Cr\max} > V_o \left(1 + \frac{I_{i\max}}{I_{i\min}}\right)$




DC/DC conversion ratio

By energy conservation law, conversion ratio derived


$$M = \frac{V_o}{V_s} = \frac{1}{\frac{f_s}{2\pi f_r} [\pi + \sin^{-1}(\frac{\gamma}{M}) + \frac{\gamma}{2M} + \frac{M}{\gamma} (1 + \sqrt{1 - \frac{\gamma^2}{M^2}})]}$$

Where $\gamma = \frac{R_0}{Z_r}$

DC/DC conversion ratio

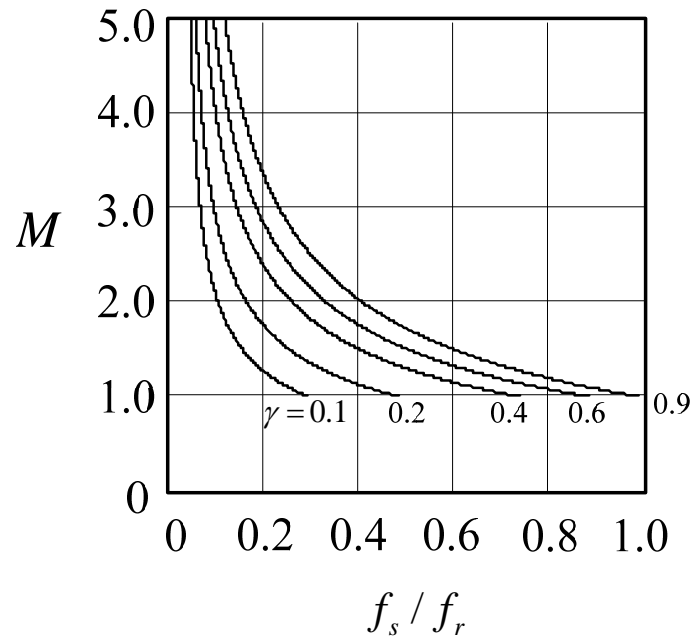

(a) 半波模式

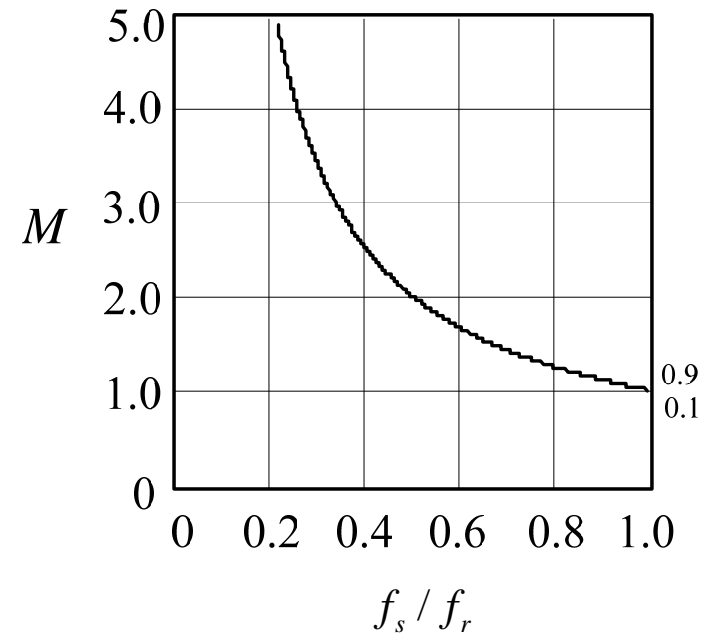

(b) 全波模式

Half wave case: conversion ratio also affected by load

Full wave case: conversion ratio not related to load

Full wave: $M \approx \frac{f_r}{f_s}$

2018/9/3

电力电子技术

77

ZCS vs. ZVS

ZCS QRC:

- Switch is ZCS turn-off
- diode D is zero voltage off, reverse recovery reduced
- Switch turn-on loss and EMI noise

ZVS QRC:

- Switch is ZVS turn-on
- Parasitic resonance between D junction cap and resonant inductor
- Higher voltage stress on switch

$$V_{Cr\max} > V_o \left(1 + \frac{I_{i\max}}{I_{i\min}}\right)$$

QRC vs. PWM converter

QRC:

- switching loss is reduced
- Circuit is simple
- Higher current or voltage stress
- Conduction loss is higher
- Variable frq control cause filter larger ???